



Technical University of Lodz
Institute of Electronics



Electronic Circuits

Marcin Kociolek PhD
Medical Electronics Division
Łódź 2018



General info

Lecturer:
Marcin Kociolek PhD
senior lecturer in w Institute of Electronics LUoT
Contact:
e-mail: kociolek@p.lodz.pl
<http://www.eletel.p.lodz.pl/kociolek>
phone: +48 42 631 26 38
room: 205 B9
Consultation:
please check my calendar:
<http://www.eletel.p.lodz.pl/kociolek/timetable2010.html>

2



General info

2 ECTS credits - 50 ÷ 60 h. of work
(1 ECTS – 25 ÷ 30 h)

Lecture:

15 h

Laboratory:

15 h

Self work:

20 ÷ 30 (during 15 weeks of semester)

3



Final Mark - lecture

- 1) 7 partial test (10 min) each lecture (first one on 2nd meeting)
 - Each test gives 0÷4 credits
 - Final mark is:
 - >19 4
 - >21 4,5
 - >23 5
 - First test can be repeated
 - A student, who will inform me before 8.00 on test day, about his/her absence on the test, has the right to take this test at other time
 - Additional test time will be scheduled in the last meeting of the semester. At this time a Student will be able to retake the first test and/or take missing test. A student will be able to take maximum of 2 tests

4



Final Mark - lecture

- 2) Pirate test (whole material test) two times during exam session + one time during repetition session. Positive mark for number of received credits > half of total number of credits from the test.

Remarks:

- Tests results will be published on my webpage in 5 work days after the test
- Works will be available for review during my consultation hours only for 5 days after publication of results.

Laboratory:

Mark for the report and work during laboratories.

5



Lecture Plan

1. Operational Amplifiers
2. Noise in active circuits
3. Analog multipliers
4. Power amplifiers integrated circuits
5. Band pass amplifiers integrated circuits
6. Active analog filters with continuous and discrete time
7. Phase-locked loop and its applications
8. Detectors of amplitude, frequency and phase
9. Programmable analog circuits and their applications
10. Application specific integrated circuits
11. Digital to analog and analog to digital converters

6



Laboratory

Laboratory: 15h (L215, B9)

- Linear distortion
- Nonlinear distortion
- Broadband amplifier
- Power amplifier
- ...

7



Warning !

Slides shown during lectures do not cover all knowledge needed for passing all tests. Knowledge is passed during the lecture.

It is very wise to make notes from the lecture. It is also worth of effort to read publications which covers presented topics.

8



Lecture Plan

1. Noise in active circuits
2. Analog multipliers
3. Power amplifiers integrated circuits
4. Band pass amplifiers integrated circuits
5. Active analog filters with continuous and discrete time
6. Phase-locked loop and its applications
7. Detectors of amplitude, frequency and phase
8. Digital to analog and analog to digital converters

9




Operational Amplifier (OPAMP) circuits

operational amplifier:

- DC amplifier
- High voltage gain
- Symmetrical (differential) input
- Asymmetrical output

Applications:

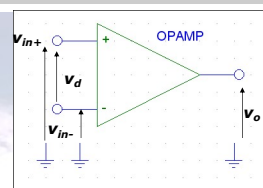- Linear an nonlinear operations
- Usually works with high negative gain



$$v_o = A_{vd}(v_{in+} - v_{in-}) = A_{vd}v_d$$



10





Operational Amplifier (OPAMP) circuits

Ideal opamp:

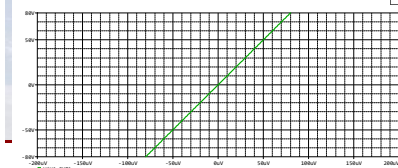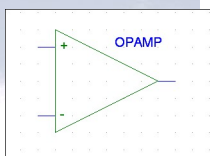- Infinite input impedance
- Zero output resistance
- Infinite voltage gain
- No limitation of output voltage
- Infinite bandwidth
- Output voltage unrelated to the sum of input voltages



Operational Amplifier (OPAMP) circuits

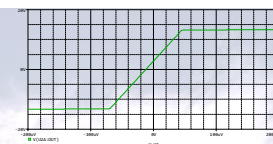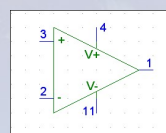

$$v_{out} = A_{vd}(v_{in+} - v_{in-}) + A_{vd}(v_{in+} + v_{in-}) + v_{noise} + V_{offset}$$

$$A_{vd} = \frac{\Delta V_o}{\Delta V_d} \Big|_{U_c = const}$$

$$A_{vc} = \frac{\Delta V_o}{\Delta V_c} \Big|_{U_c = const}$$

$$TC = \frac{A_{vd}}{A_{vc}}$$

$$CMRR = 20 \log \frac{A_{vd}}{A_{vc}}$$

12



Operational Amplifier (OPAMP) parameters

Name	unit	uA741
Gain ($A_{vd,min}$)	V/mV	25
Common mode rejection ratio (CMRR)	DB	80
Input current I_{IN}	nA	500
Wejściowy prąd niezrównoważenia I_N	nA	200
Wejściowe napięcie niezrównoważenia U_N	mV	6
Współczynnik temperaturowy napięcia niezrównoważenia	$\mu V/^\circ C$	30
Współczynnik zmian wejściowego napięcia niezrównoważenia od zmian napięcia zasilania (SVRR)	$\mu V/V$	30

13




Operational Amplifier (OPAMP) parameters

Name	unit	uA741
Input resistance (R_{in})	$M\Omega$	2
Output resistance (R_o)	Ω	75
Bandwidth (f_t lub f_T)	MHz	1
Slew rate (SR)	V/ μs	0,6
Maximum input differential voltage (V_{IND})	V	± 30
Maximum common input voltage (V_{INC})	V	± 15
Supply voltage	V	-15,+15
Power dissipated (P)	mW	50
Operation temperature range (t_{min} , t_{max})	$^\circ C$	0,+70



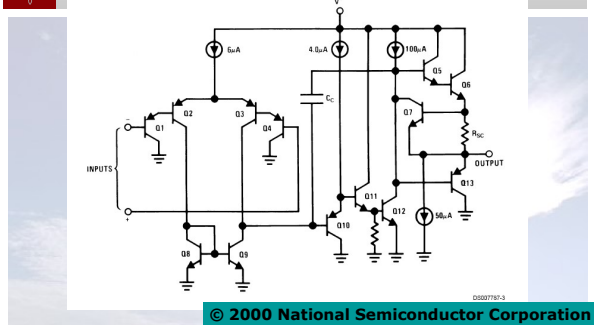Operational Amplifier (OPAMP) example (LM358)




© 2000 National Semiconductor Corporation

15



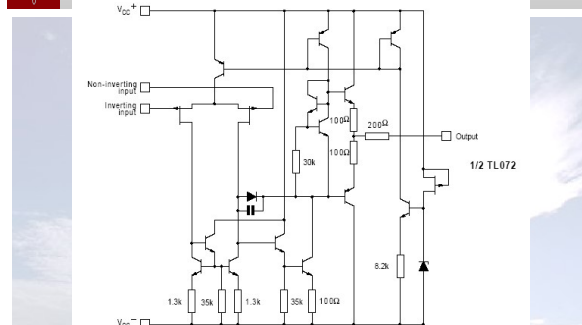Operational Amplifier (OPAMP) example (TL072)




© 2001 STMicroelectronics

16



Inverting amplifier

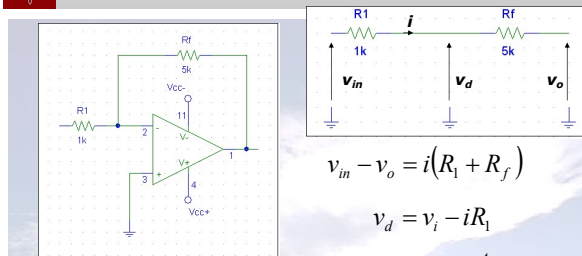

$$v_{in} - v_o = i(R_1 + R_f)$$

$$v_d = v_i - iR_1$$

$$v_o = -v_d A$$

17



Inverting amplifier

$$v_o = -v_d A$$

$$v_{in} - v_o = i(R_1 + R_f)$$

$$v_d = -v_o \frac{1}{A}$$

$$i = (v_{in} - v_o) \frac{1}{R_1 + R_f}$$

$$v_d = v_{in} - iR_1$$

$$-v_o \frac{1}{A} = v_{in} - (v_{in} - v_o) \frac{R_1}{R_1 + R_f}$$

$$-v_o \frac{1}{A} = v_{in} - v_{in} \frac{R_1}{R_1 + R_f} + v_o \frac{R_1}{R_1 + R_f}$$

18



Inverting amplifier

$$-v_o \frac{1}{A} = v_{in} - v_{in} \frac{R_1}{R_1 + R_f} + v_o \frac{R_1}{R_1 + R_f}$$

$$-v_o \frac{1}{A} - v_o \frac{R_1}{R_1 + R_f} = v_{in} - v_{in} \frac{R_1}{R_1 + R_f}$$

$$-v_o \left(\frac{1}{A} + \frac{R_1}{R_1 + R_f} \right) = v_{in} \left(1 - \frac{R_1}{R_1 + R_f} \right)$$

$$\frac{v_o}{v_{in}} = - \frac{1 - \frac{R_1}{R_1 + R_f}}{\frac{1}{A} + \frac{R_1}{R_1 + R_f}}$$

19



Inverting amplifier

$$\frac{v_o}{v_{in}} = - \frac{1 - \frac{R_1}{R_1 + R_f}}{\frac{1}{A} + \frac{R_1}{R_1 + R_f}} = - \frac{\frac{R_1 + R_f - R_1}{R_1 + R_f}}{\frac{1}{A} + \frac{R_1}{R_1 + R_f}} = - \frac{R_1 + R_f - R_1}{\frac{A(R_1 + R_f)}{R_1 + R_f} + \frac{R_1}{R_1 + R_f}}$$

$$\frac{v_o}{v_{in}} = - \frac{R_f}{R_1 + R_f} \frac{A(R_1 + R_f)}{R_1 + R_f + AR_1} = - \frac{AR_f}{R_1 + R_f + AR_1}$$

$$\frac{v_o}{v_{in}} = - \frac{AR_f}{R_1 + R_f + AR_1} = - \frac{R_f}{R_1} \frac{AR_1}{R_1 + R_f + AR_1}$$

20



Inverting amplifier

$$\frac{v_o}{v_{in}} = - \frac{AR_f}{R_1 + R_f + AR_1} = - \frac{R_f}{R_1} \frac{AR_1}{R_1 + R_f + AR_1}$$

$$\frac{v_o}{v_{in}} = - \frac{R_f}{R_1} \frac{1}{\frac{1}{A} + \frac{R_f}{AR_1} + 1} = - \frac{R_f}{R_1} \frac{1}{\frac{R_1 + R_f}{AR_1} + 1}$$

$$\frac{v_o}{v_{in}} = - \frac{R_f}{R_1} \frac{1}{1 + \frac{1}{A\beta_v}}$$

$$\beta_v = \frac{R_1}{R_1 + R_f}$$

21



Inverting amplifier

$$\frac{v_o}{v_{in}} = - \frac{R_f}{R_1} \frac{1}{1 + \frac{1}{A\beta_v}}$$

$$\beta_v = \frac{R_1}{R_1 + R_f}$$

$$A\beta_v > 1000$$


$$A_{vf} = - \frac{R_f}{R_1}$$

$$A_{vf} = - \frac{Z_f}{Z_i}$$

22



Inverting amplifier

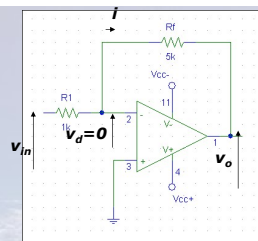

$$v_d = 0$$

$$i_{in-} = 0$$

$$v_{in} = iR_1 \quad i = \frac{v_{in}}{R_1}$$

$$v_o = -iR_f$$


$$v_o = -v_{in} \frac{R_f}{R_1}$$

$$\frac{v_o}{v_{in}} = - \frac{R_f}{R_1} \quad A_{vf} = - \frac{R_f}{R_1}$$

23



Inverting amplifier

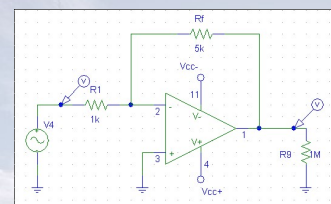

24




Inverting amplifier transfer characteristic



25




Inverting amplifier time plots

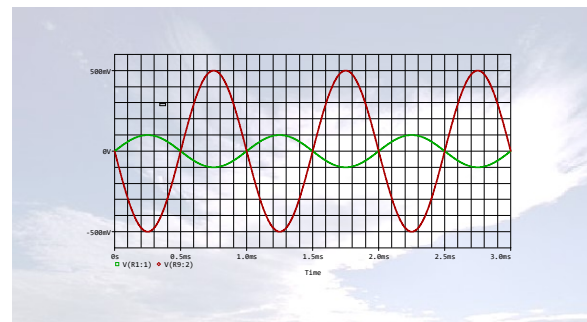

26




Inverting amplifier frequency response

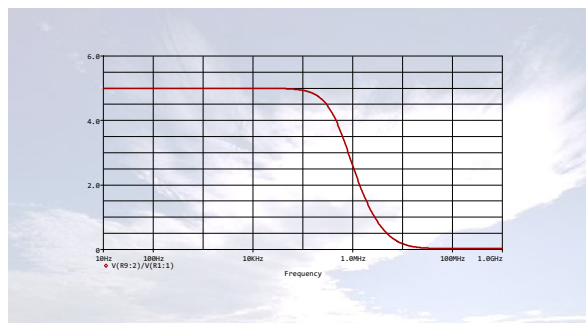

27




Inverting amplifier frequency response

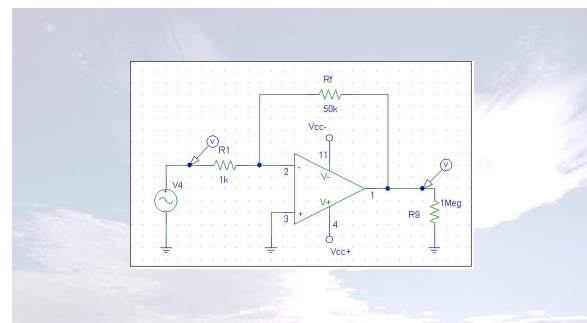

28




Inverting amplifier frequency response

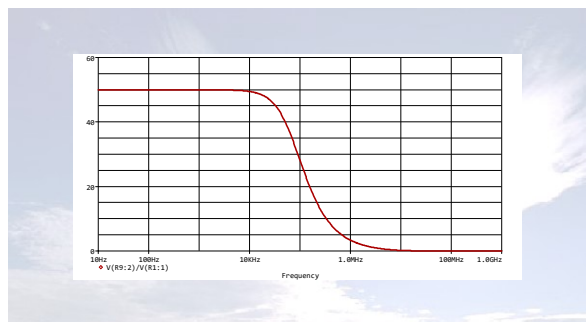

29




Inverting amplifier frequency response

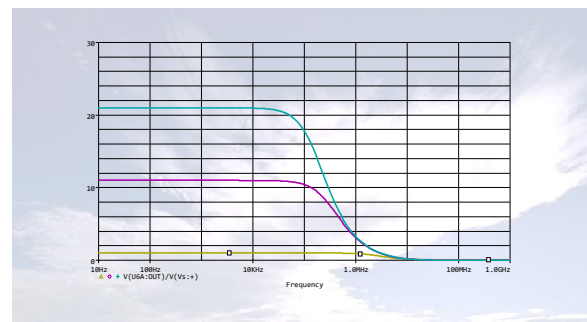

30




Inverting amplifier frequency response

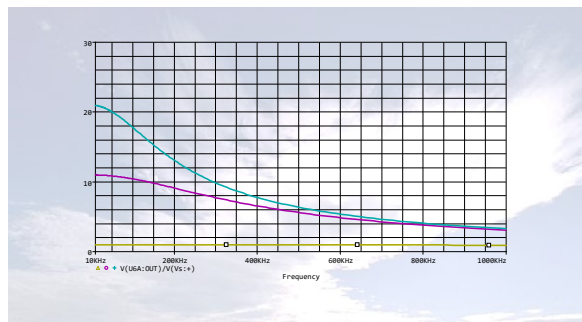

31



Noninverting amplifier

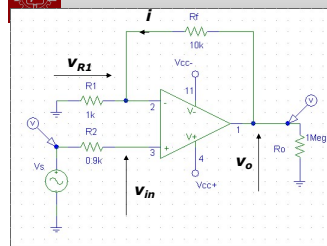


$$v_d = 0$$

$$i_{in+} = i_{in-} = 0$$

32



Noninverting amplifier

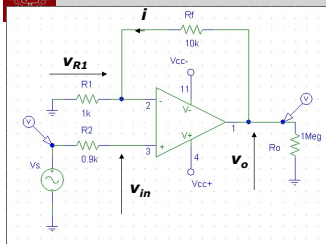

$$v_d = 0$$

$$i_{in+} = i_{in-} = 0$$

$$v_{in} = iR_1 \quad i = \frac{v_{in}}{R_1}$$

$$v_o = i(R_f + R_1)$$


$$v_o = \frac{v_{in}}{R_1} (R_f + R_1)$$

$$A_{vf} = \frac{v_o}{v_{in}} = \frac{R_f}{R_1} + 1$$

33



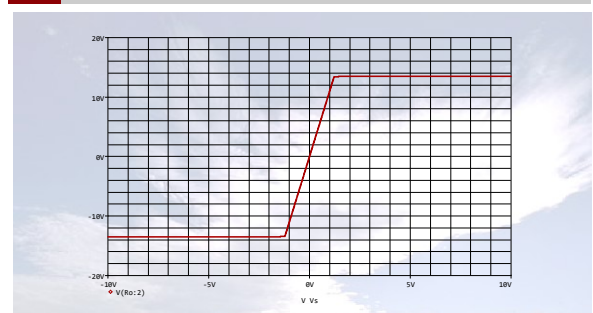
Noninverting amplifier transfer characteristic



34




Noninverting amplifier

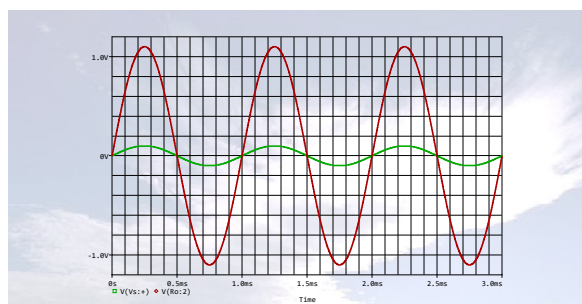

35



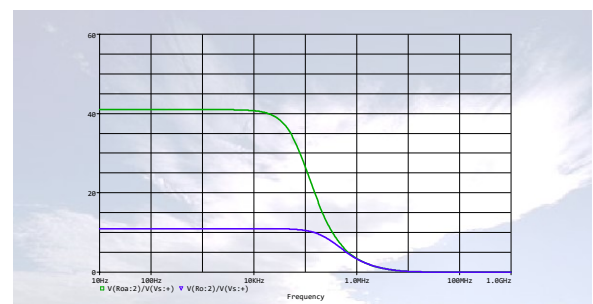
Noninverting amplifier frequency response



36




Voltage follower

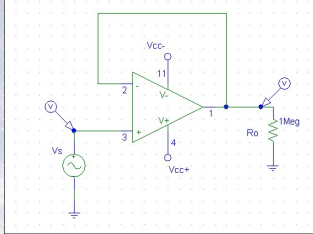

37



Differential amplifier

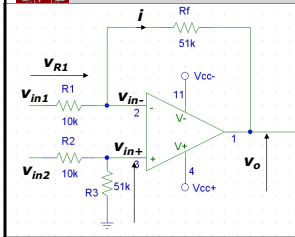

$$v_d = 0$$

$$i_{in+} = i_{in-} = 0$$

$$v_{in+} = v_{in2} \frac{R_2}{R_2 + R_3}$$

$$i = (v_{in1} - v_o) \frac{1}{R_1 + R_f}$$

$$v_{in-} = v_{in1} - iR_1$$

$$v_{in-} = v_{in1} - (v_{in1} - v_o) \frac{R_1}{R_1 + R_f}$$

38



Differential amplifier

$$v_{in-} = v_{in1} - v_{in1} \frac{R_1}{R_1 + R_f} + v_o \frac{R_1}{R_1 + R_f}$$


$$v_{in-} = v_{in1} \left(1 - \frac{R_1}{R_1 + R_f} \right) + v_o \frac{R_1}{R_1 + R_f}$$

$$v_{in-} = v_{in1} \frac{R_f}{R_1 + R_f} + v_o \frac{R_1}{R_1 + R_f}$$

39



Differential amplifier

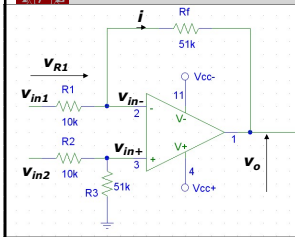

$$v_d = 0$$

$$v_{in+} = v_{in-}$$

$$v_{in+} = v_{in2} \frac{R_2}{R_2 + R_3}$$

$$v_{in-} = v_{in1} \frac{R_f}{R_1 + R_f} + v_o \frac{R_1}{R_1 + R_f}$$

$$v_{in2} \frac{R_2}{R_2 + R_3} = v_{in1} \frac{R_f}{R_1 + R_f} + v_o \frac{R_1}{R_1 + R_f}$$

40



Differential amplifier

$$v_{in2} \frac{R_2}{R_2 + R_3} = v_{in1} \frac{R_f}{R_1 + R_f} + v_o \frac{R_1}{R_1 + R_f}$$

$$v_o \frac{R_1}{R_1 + R_f} = v_{in2} \frac{R_2}{R_2 + R_3} - v_{in1} \frac{R_f}{R_1 + R_f}$$


$$\frac{R_1}{R_f} = \frac{R_2}{R_3}$$

$$v_o = \frac{R_f}{R_1} (v_{in2} - v_{in1})$$

41




Differential amplifier

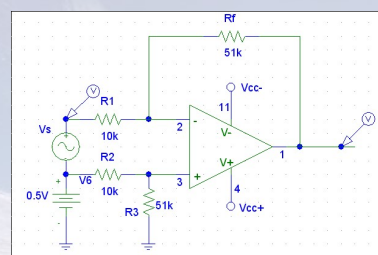

42




Differential amplifier

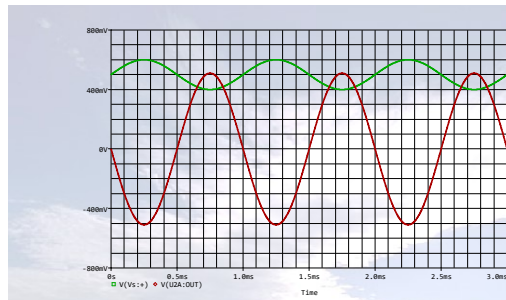

43




Differential amplifier

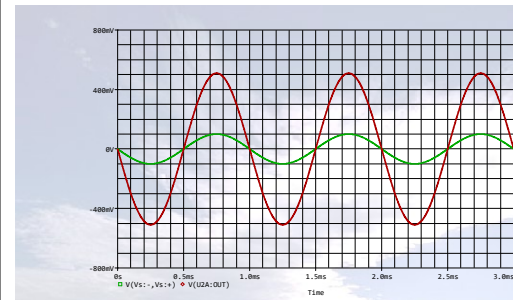

44



Differential amplifier

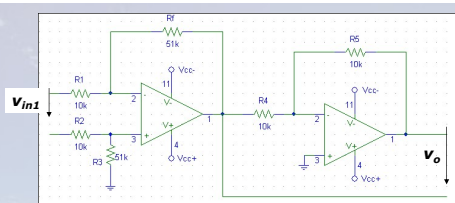


$$v_o = 2 \frac{R_f}{R_1} (v_{in2} - v_{in1})$$

$$v_o = 2 \frac{R_f}{R_1} v_{in1}$$

45




Differential amplifier

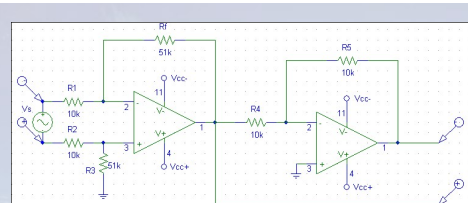

46




Differential amplifier

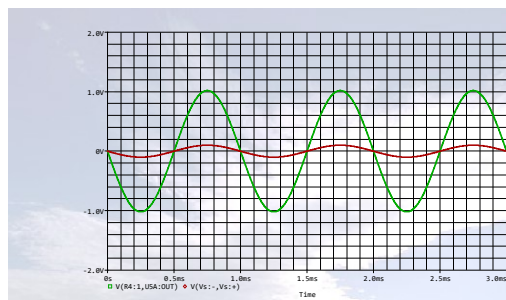

47



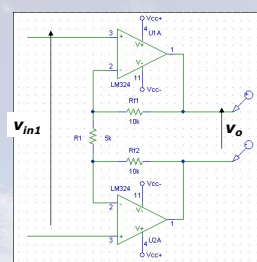Differential amplifier with very high input resistance




$$v_o = \left(1 + 2 \frac{R_f}{R_1} \right) v_{in2}$$

48



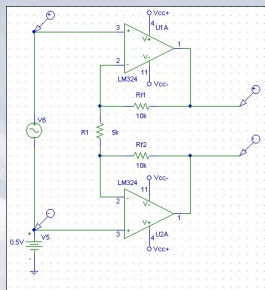
Differential amplifier with very high input resistance



49



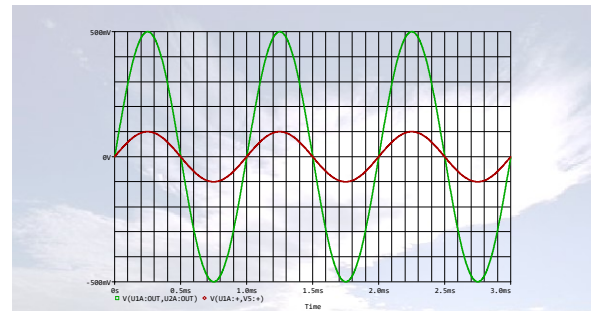
Differential amplifier with very high input resistance



50



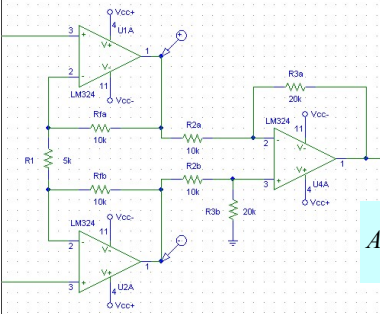Differential amplifier with very high input resistance




$$A_{vf} = - \left(1 + 2 \frac{R_f}{R_1} \right) \frac{R_3}{R_2}$$

51



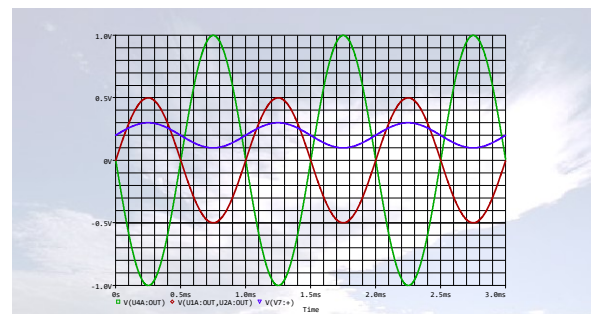
Differential amplifier with very high input resistance



52



Instrumentation amplifier

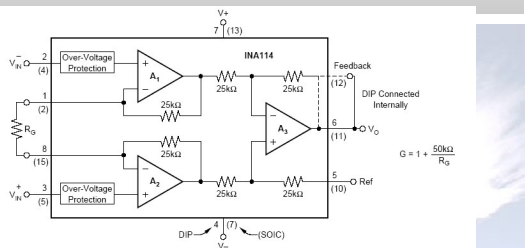


©1992 Burr-Brown Corporation

53



Instrumentation amplifier

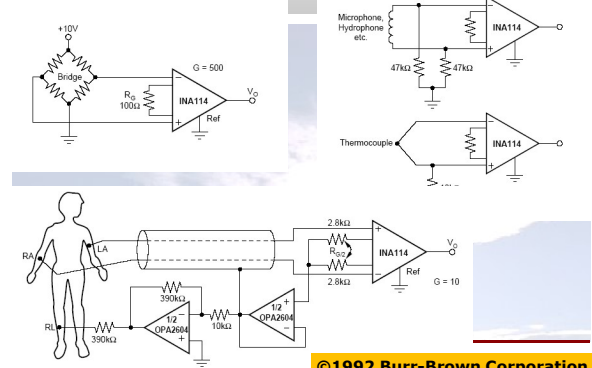

©1992 Burr-Brown Corporation

Summing amplifier

$$i = \frac{u_{in1}}{R_1} + \frac{u_{in2}}{R_2} + \frac{u_{in3}}{R_3}$$

$$u_o = -u_{in1} \frac{R_f}{R_1} - u_{in2} \frac{R_f}{R_2} - u_{in3} \frac{R_f}{R_3}$$

Thanks to the virtual shortcircuit to the ground inputs are separated

Current to voltage transducer

$$v_o = -i_{in} R_f$$

Voltage to current transducer

$$i_L = \frac{v_{in} - V_{cc-}}{R_e}$$

Differentiating amplifier

$$i(t) = C \frac{\partial v_{in}(t)}{\partial t}$$

$$v_o(t) = -i(t) R_f$$

$$v_o(t) = -C R_f \frac{\partial v_{in}(t)}{\partial t}$$

Differentiating amplifier

Integrating amplifier

$$i = \frac{v_{in}}{R_1}$$

$$i = -C \frac{\partial v_o}{\partial t}$$

$$C \frac{\partial v_o(t)}{\partial t} = -\frac{v_{in}(t)}{R_1}$$


$$\frac{\partial v_o(t)}{\partial t} = -\frac{v_{in}(t)}{C R_1}$$

$$\frac{\partial v_o(t)}{\partial t} = -\frac{v_{in}(t)}{C R_1}$$

$$v_o(t) = -\frac{1}{C R_1} \int v_{in}(t) dt$$




Integrating amplifier

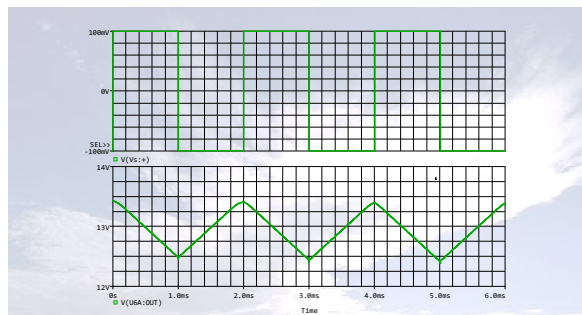

61




Wzmacniacz całkujący

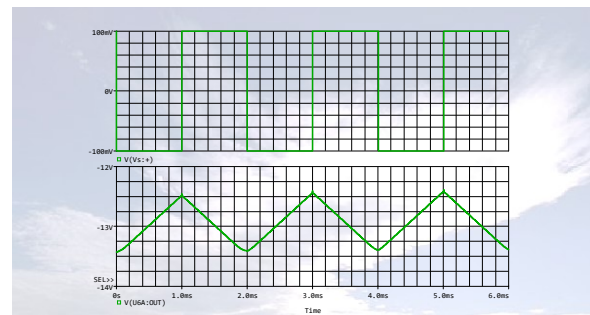

62




Integrating amplifier

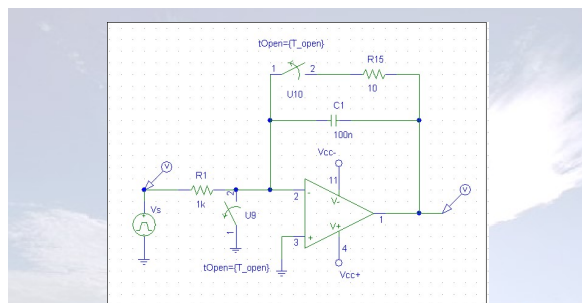

63




Integrating amplifier

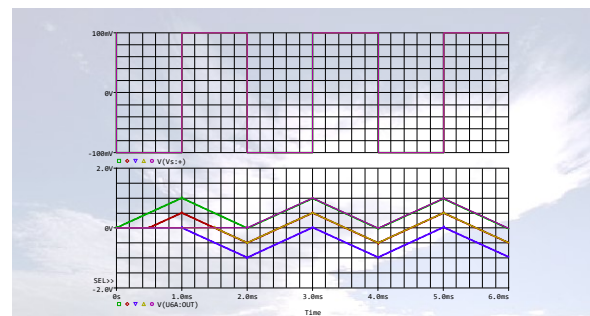

64




Integrating amplifier

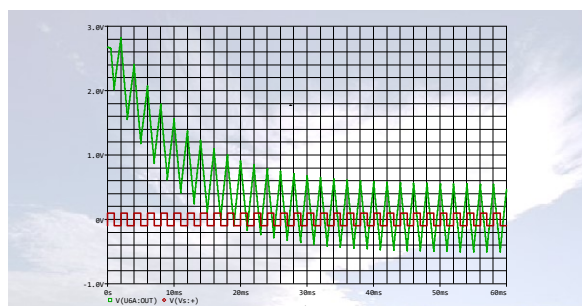

65




Integrating amplifier

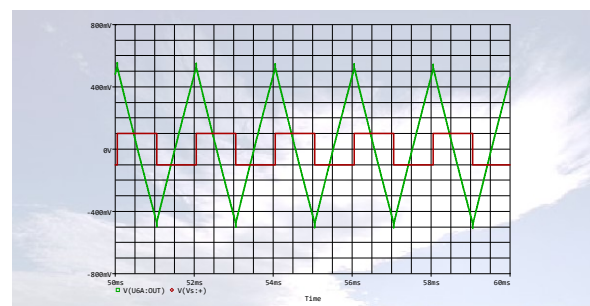

66




Integrating amplifier

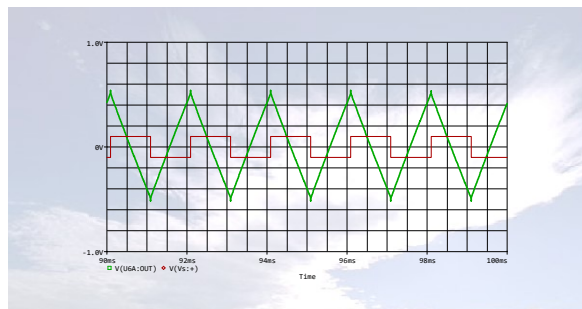

67




Integrating amplifier

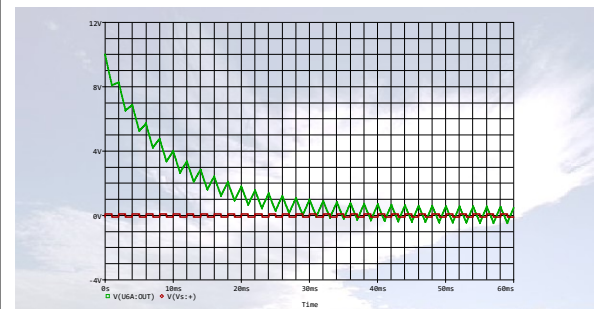

68




Integrating amplifier

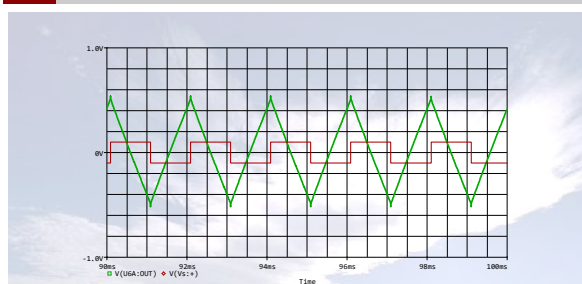

69




Impulse response

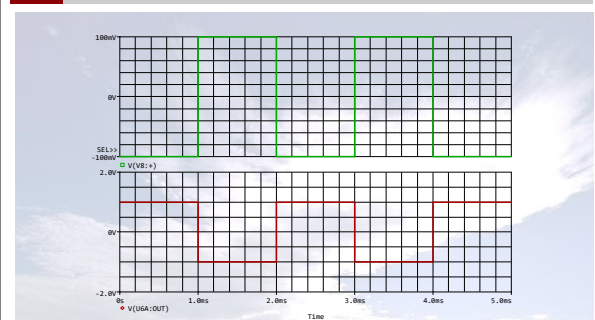

70




Impulse response

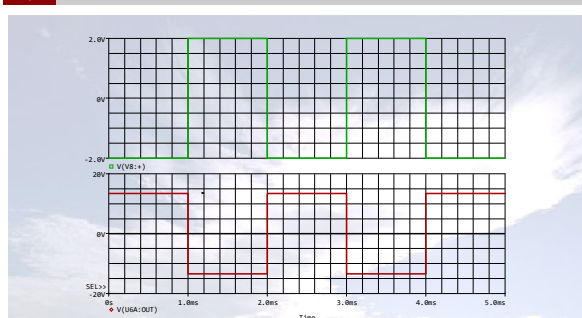

71




Impulse response

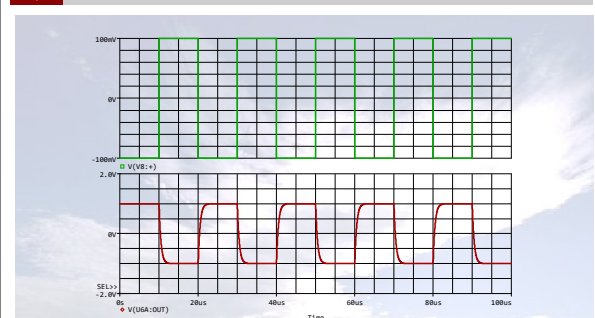

72




Impulse response

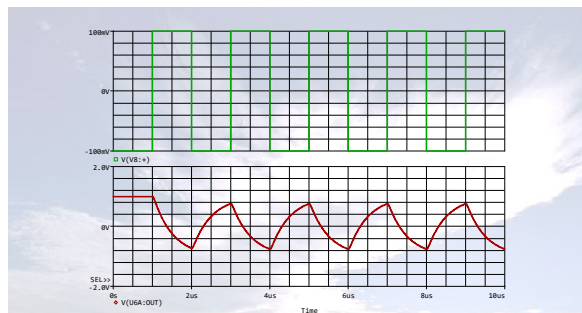

73




Impulse response

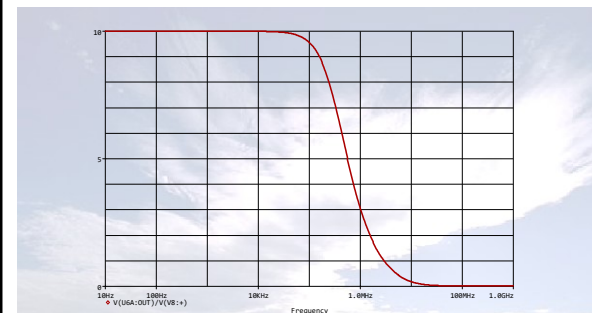

74



Impulse response

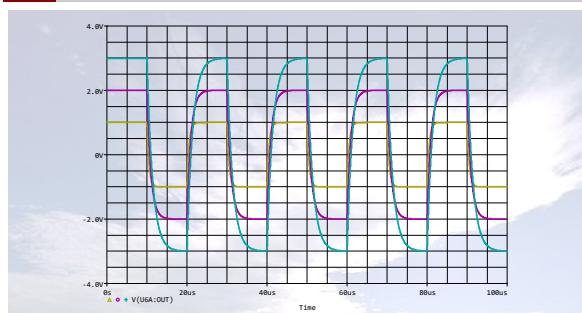


75



Opamp with open feedback loop-comparator

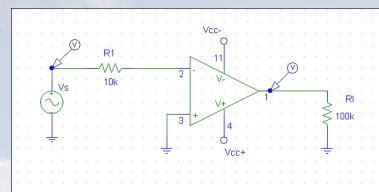
Non regenerative detector of zero crossing



76



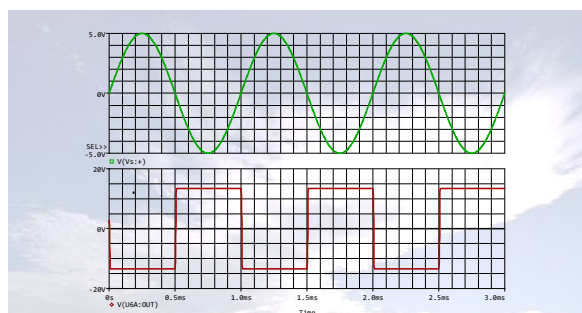
Non regenerative detector of zero crossing



77



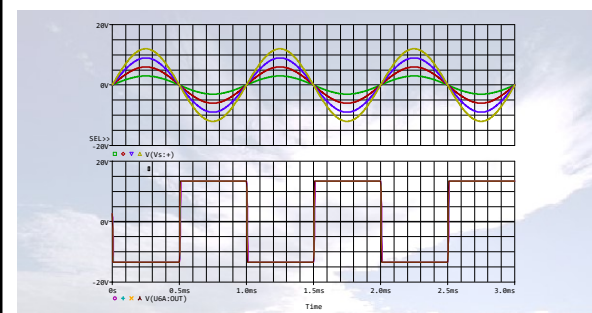
Non regenerative detector of zero crossing



78




Non regenerative amplitude discriminator

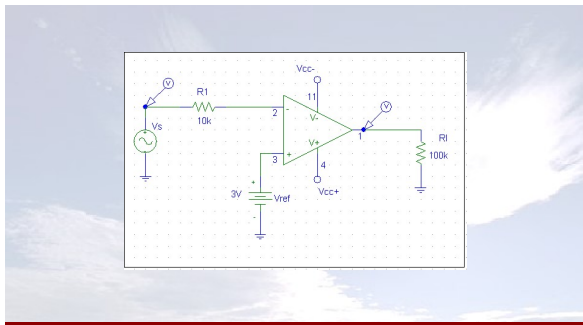

79




Non regenerative amplitude discriminator

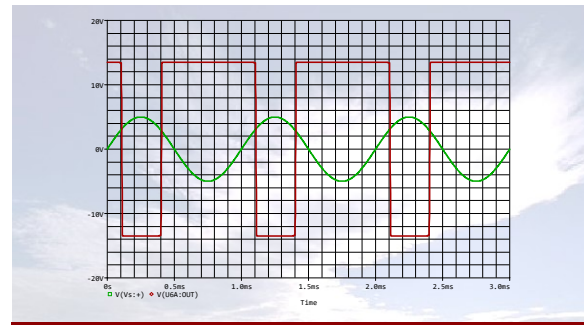

80




Non regenerative amplitude discriminator

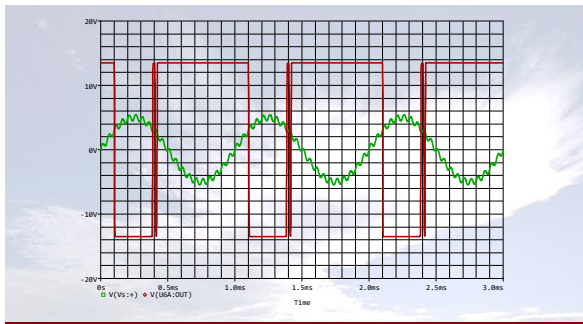

81




Regenerative amplitude discriminator

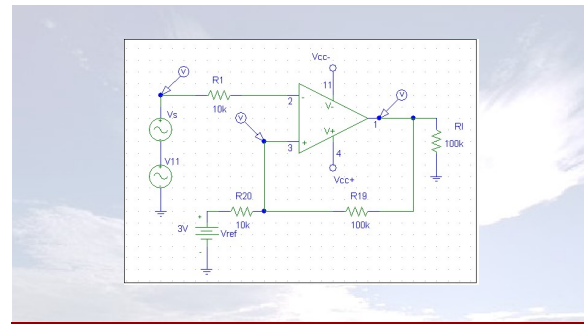

82




Regenerative amplitude discriminator

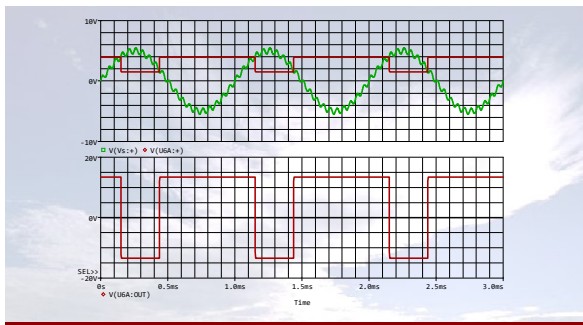

83




Regenerative amplitude discriminator

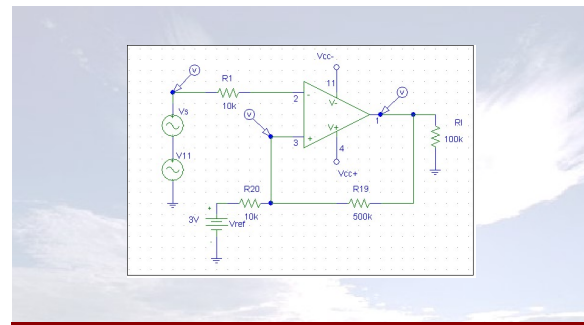

84




Regenerative amplitude discriminator

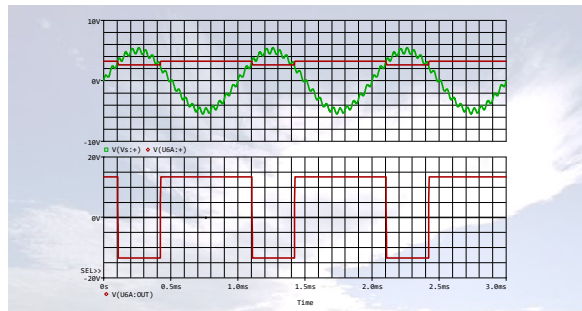

85




Regenerative amplitude discriminator

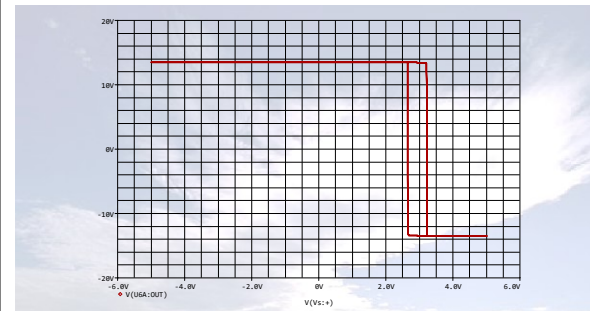

86




Regenerative amplitude discriminator

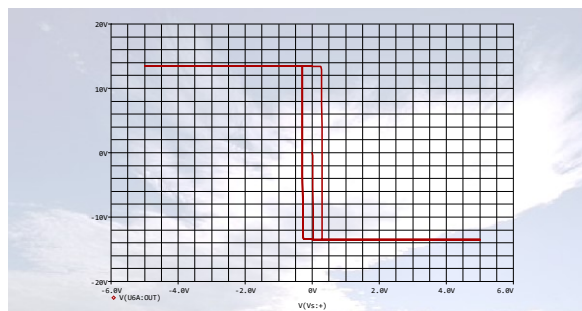

87




Regenerative amplitude discriminator

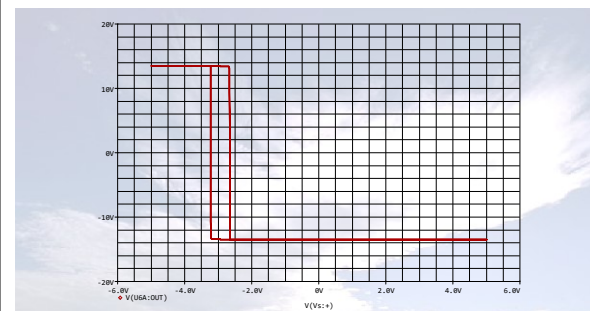

88




Regenerative amplitude discriminator

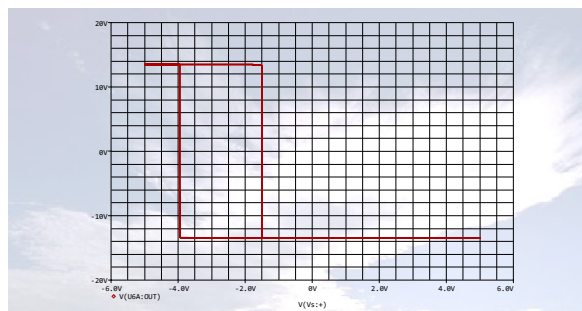

89




Regenerative amplitude discriminator

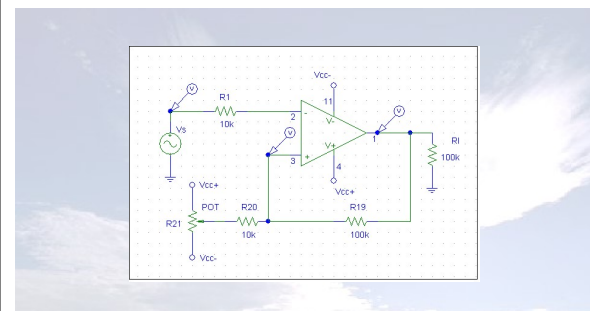

90



Regenerative amplitude discriminator

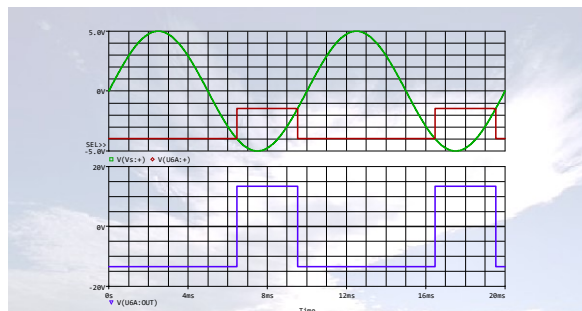

91



Noise in active circuits

Literature:

Józef Boksa, Analogowe układy elektroniczne, BTC, Warszawa 2007

Waldemar Nawrocki, Krzysztof Arnold, Krzysztof Lange, Układy Elektroniczne, Wydawnictwo Politechniki Poznańskiej, Poznań 1999

Stanisław Kuta, Wykład układy Elektroniczne, szумы w układach elektronicznych, AGH

<http://student.agh.edu.pl/~mborowka/UE/wyklad/R1.17.ppt>

Fabrizio Bonani, Giovanni Ghione, Noise in Semiconductor Devices: Modeling and Simulation Springer (Kindle Edition - 6 Sep 2001)

92



Noise in active circuits

Noise
Interference
Distortion

93



Noise in active circuits

Noise:

a random fluctuation in an electrical signal, a characteristic of all electronic circuits

Interference:

an unwanted external signal causing improper operation of electronic device. e.g. cross-talk, deliberate jamming or other unwanted electromagnetic interference from specific transmitters

Distortion:

unwanted (very often predictable) alteration of signal waveform introduced by electronic device. Distortion is caused by properties of device.

94



Noise in active circuits

Noise is an unwanted perturbation to a wanted signal; it is called noise as a generalization of the audible noise heard when listening to a weak radio transmission

Noise can block, distort, change or interfere with the meaning of a message in human, animal and electronic communication.

Electronic noise is a random fluctuation in an electrical signal, a characteristic of all electronic circuits.

[http://en.wikipedia.org/wiki/Noise_\(electronics\)](http://en.wikipedia.org/wiki/Noise_(electronics))
<http://en.wikipedia.org/wiki/Noise>

95



Noise in active circuits

Noise Types:

- thermal,
- shot,
- flicker - $1/f$,
- burst,
- magnetic,
- ionic,
- avalanche,
- generation recombination,
- ...

96



Thermal Noise

Main source of distortions in electronic circuits.

Johnson–Nyquist noise (sometimes thermal, Johnson or Nyquist noise) is unavoidable, and generated by the random thermal motion of charge carriers (usually electrons), inside an electrical conductor, which happens regardless of any applied voltage.

Predicted by A. Einstein w 1907r

First observed by J. B. Johnson from Bell Labs in 1928

Explained by H Nyquist from Bell Labs

97



Thermal Noise

Voltage variance RMS (root mean square) per hertz of bandwidth, is given by:

$$\bar{v} = \sqrt{4k_B TR \Delta f} \quad \text{Johnson-Nyquist equation}$$

where:

R – resistance [Ω]

Δf – noise frequency band [Hz],

k_B – Boltzman's constant = $1,38 \times 10^{-23}$ [J/K]

T - temperature [K].


Power of thermal noise

$$P = \frac{\left(\frac{\bar{v}}{2}\right)^2}{R} = k_B T \Delta f$$

98



Thermal Noise

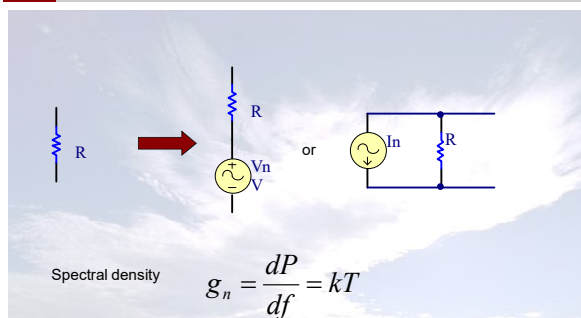

99



Thermal Noise

Main properties of thermal noise:

- Present in all resistive elements,
- Caused by thermal excitation of electrons,
- Spectral density is constant in very wide bandwidth (0 - 10^{13} Hz),
- Power is proportional to the bandwidth

100



Shot noise

Shot noise in electronic devices consists of unavoidable random statistical fluctuations of the electric current through a potential barrier.

Random fluctuations are inherent when current flows through e.g. p-n junction, as the current is a flow of discrete charges (electrons).

Noise is caused by discrete nature of mater.

http://en.wikipedia.org/wiki/Shot_noise

101



Shot noise

RMS of current fluctuations is given:

$$I_{sn} = \sqrt{2eI\Delta f} \quad \text{Schottky equation:}$$

where:

e – elementary charge $1,6 \times 10^{-19}$ [C],

I – average current thru device [A],

Δf – noise bandwidth [Hz]

102



Shot noise

Main properties of the shot noise:

- Refers mainly to the p-n junctions,
- Is caused by quantum nature of current,
- Spectrum is equally spaced in frequency,
- Shot noise measurements allow for calculation of element charge

103



Flicker noise 1/f (low frequency noise)

It occurs in almost all electronic devices, and results from a variety of effects, though always related to a direct current. In electronic devices, it is a low-frequency phenomenon, as the higher frequencies are overshadowed by white noise from other sources.

The cause of flicker noise occurrence is not yet explained. 2 hypothesizes:

- Conductivity fluctuations on the junction between 2 different materials in electronic elements (this can explain why such noise exist in various elements)
- Result of few different physical actions among them the dominating is generation and recombination of electric charges in defects of semiconductor crystal structure


104



Flicker noise 1/f (low frequency noise)

Spectral density :

$$S(f) = k \frac{1}{f^\alpha}$$

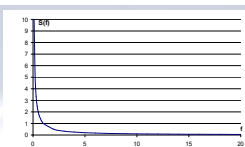

α coefficient is usually close to 1 (range 0,7 – 2).

when :

$\alpha = 1$ noise is called pink

$\alpha = 2$ noise is called red

105



Burst Noise


Burst noise consists of sudden step-like transitions between two or more levels.

No single source of popcorn noise is theorized to explain all occurrences.

The most commonly invoked cause is the random trapping and release of charge carriers at thin film interfaces or at defect sites in bulk semiconductor crystal.

Properties:

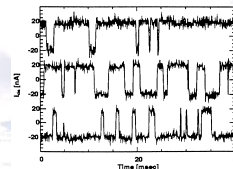
- Impulse time from ms to tens of s
- Frequency < 1Hz
- Amplitude 10 to 100 times higher than amplitude of thermal noise



106



Noise parameters

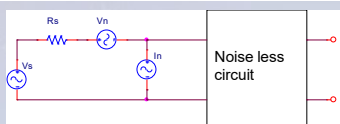

$$SNR = \frac{P_s}{P_n}$$

$$SNR_{out} = SNR_{in} \quad \text{For noiseless circuit}$$


$$SNR_{out} = F \times SNR_{in} \quad \text{For real circuit}$$

where: F noise coefficient $F > 1$

107



Noise parameters

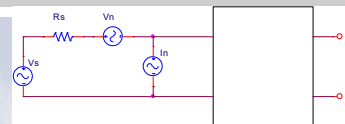

$$V_{n_total}^2 = V_n^2 + R_s^2 I_n^2 + V_{ns}^2 + 2c V_n I_n R_s$$

where:

V_{n_total} – total noise voltage taken to the input of circuit

V_{ns} – noise voltage generated by signal source


c – correlation coefficient between V_n and I_n

For $c = 0$:

$$V_{n_total}^2 = V_n^2 + R_s^2 I_n^2 + V_{ns}^2$$

108

Noise coefficient

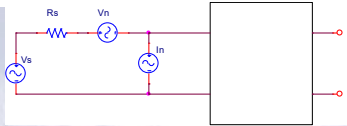

$$F = \frac{V_{n_total}^2}{V_{ns}^2} = \frac{V_n^2 + R_s^2 I_n^2 + V_{ns}^2}{V_{ns}^2}$$

$$F[dB] = 10 \log_{10} \frac{V_n^2 + R_s^2 I_n^2 + V_{ns}^2}{V_{ns}^2}$$

109

Passive elements noises

Resistor:

- Thermal noise
- Flicker noise (1/f) caused by flow of the current thru non uniform grainy structure of resistive material

Capacitor

- Very small thermal noise (can be neglected)
- Flicker noise (1/f)
- Capacitance filters out all noise sources connected in parallel to it


Inductor

- Thermal noise
- Barkhausen noise (in inductors with core) caused by magnetic field fluctuations in the core

110

Diode noises


- Thermal noise
- Shot noise

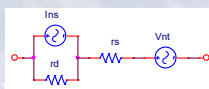

111

BJT noise

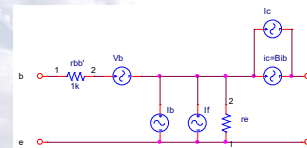- thermal noise of base region resistance
- shot noise of base current
- shot noise of collector current
- flicker noise



112

Noise in integrated circuits

- http://www.national.com/analog/power/ldo#low_noise
- <http://www.national.com/ds/LM/LM340.pdf>
- <http://focus.ti.com/lit/ds/symlink/ina114.pdf>

113

Lecture Plan

1. Noise in active circuits
2. **Analog multipliers**
3. Power amplifiers integrated circuits
4. Band pass amplifiers integrated circuits
5. Active analog filters with continuous and discrete time
6. Phase-locked loop and its applications
7. Detectors of amplitude, frequency and phase
8. Programmable analog circuits and their applications
9. Application specific integrated circuits
10. Digital to analog and analog to digital converters

114



Analog multiplier


Literature:

U. Tietze, Ch. Shenck, Electronics circuits, design and applications, Springer-Verlag, 2001

115




Analog multiplier

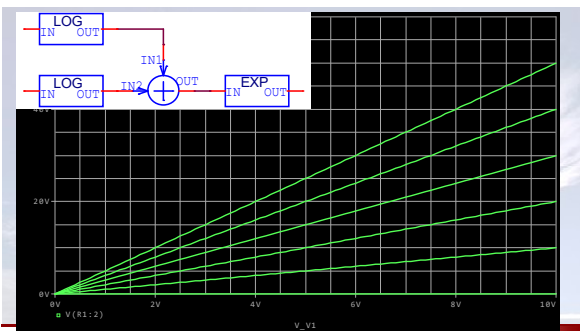

116




Analog multiplier

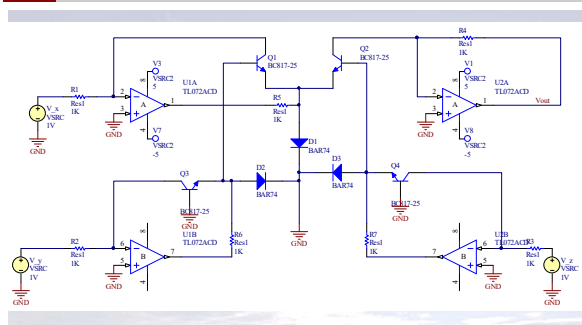

117




Analog multiplier

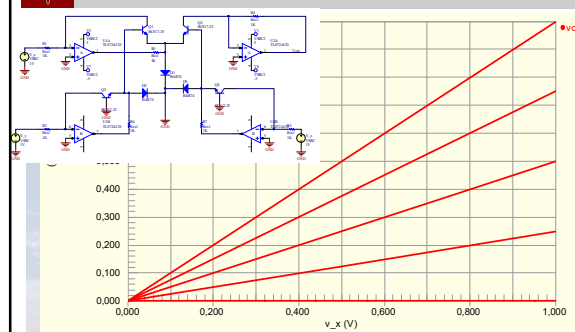

118



Analog multiplier (two-quadrant)

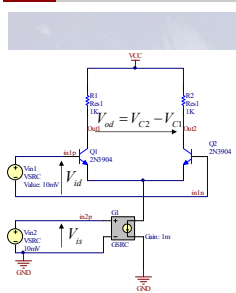

$$V_{C1} = V_{CC} - I_{C1}R_1$$

$$V_{od} = R(I_{C1} - I_{C2}) = R\Delta I_C$$

$$i_E = I_{ES} \left[\exp\left(\frac{v_{BE}}{V_T}\right) - 1 \right]$$

$$I_{C1} = \frac{I_{EE}}{1 + \exp(-V_{id}/V_T)}$$


$$I_{C2} = \frac{I_{EE}}{1 + \exp(V_{id}/V_T)}$$

$$V_{od} = RI_s \tanh(V_{id}/2V_T)$$







119



Analog multiplier (two-quadrant)

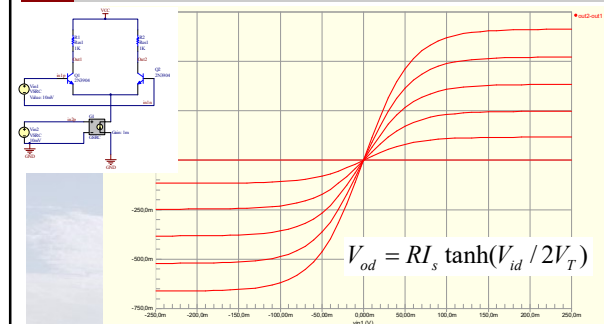


120

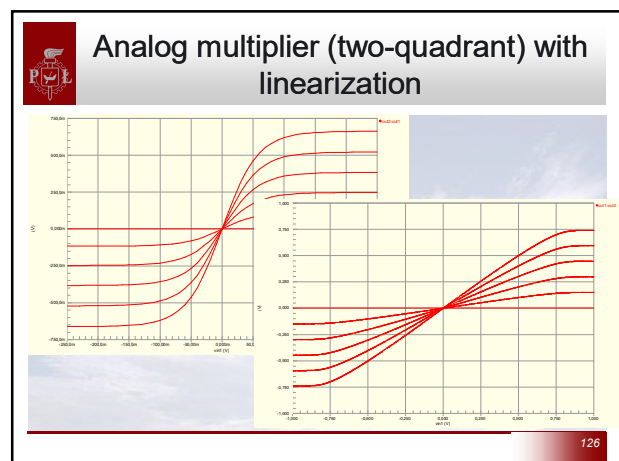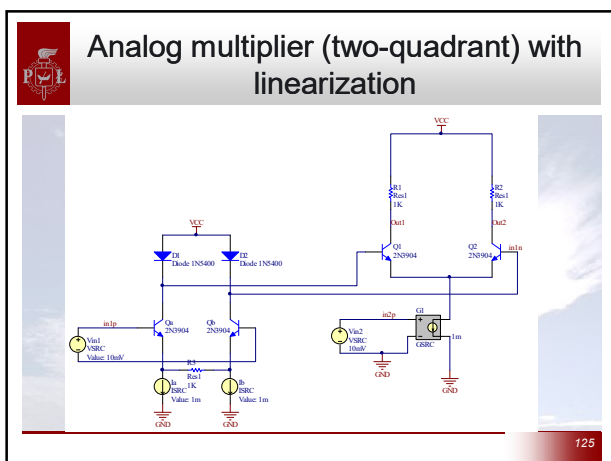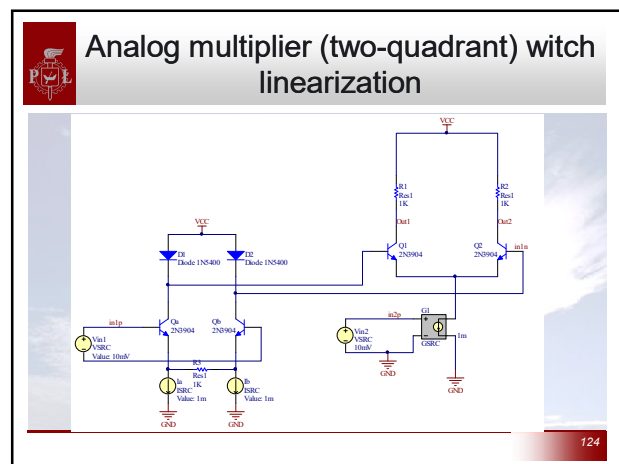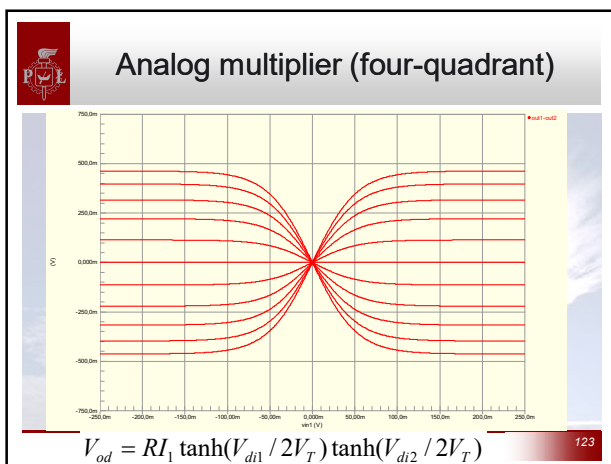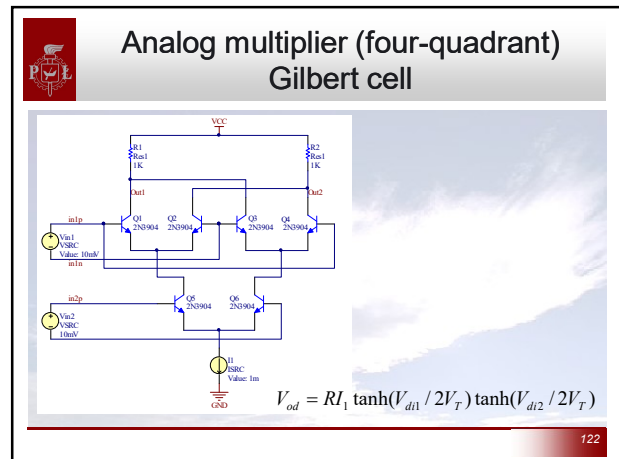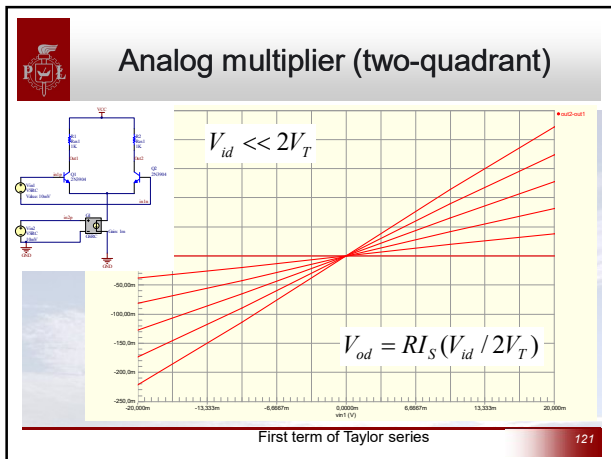



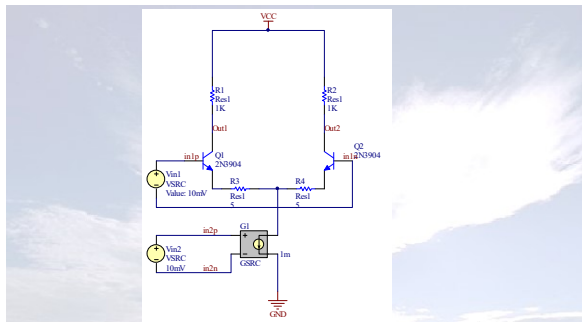
Analog multiplier (two-quadrant) with linearization



127



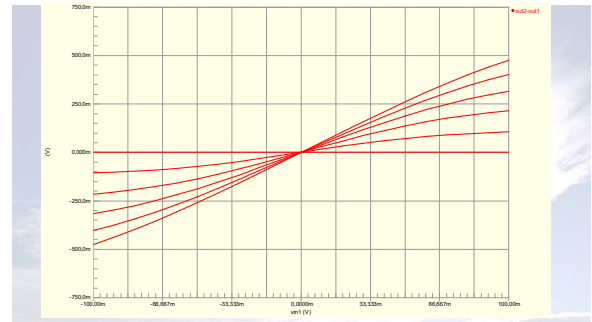
Analog multiplier (two-quadrant) with linearization



128



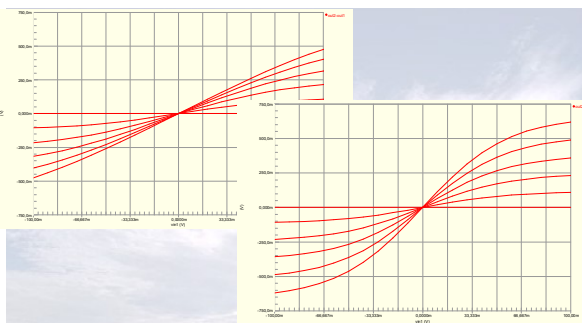
Analog multiplier (two-quadrant) with linearization



129



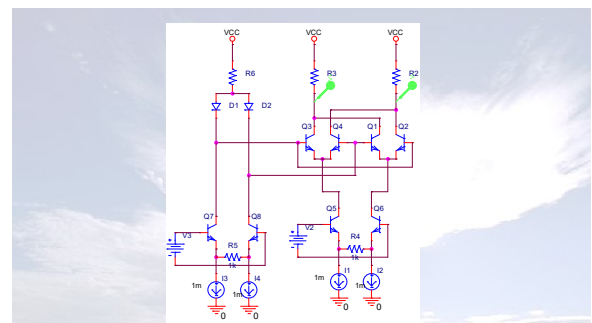
Analog multiplier (four-quadrant) with linearization



130



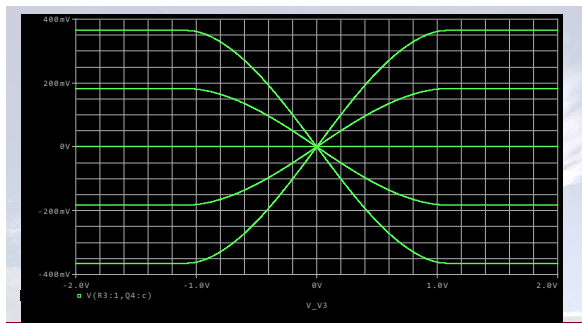
Analog multiplier (four-quadrant) with linearization



131



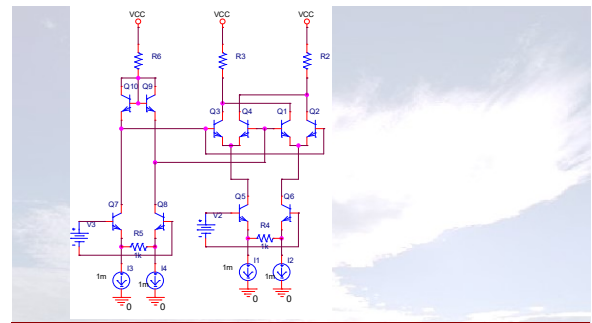
Analog multiplier (four-quadrant) with linearization



132



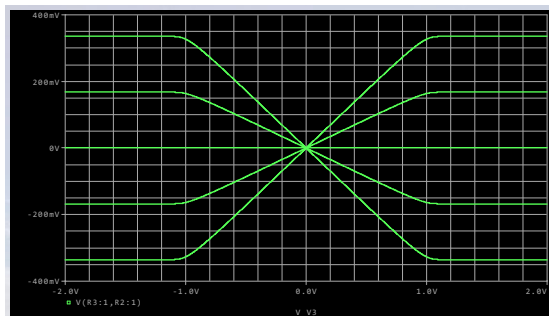Układ mnożący różnicowy (cztero ćwiartkowy) z linearyzacją



133



Analog multiplier application

- Amplitude modulation
- Amplitude detection
- Phase detection
- Frequency detection
- Frequency conversion

134



Analog multiplier application

- AD532
- ADL5391

135



Lecture Plan

1. Noise in active circuits
2. **Power amplifiers integrated circuits**
3. Band pass amplifiers integrated circuits
4. Active analog filters with continuous and discrete time
5. Analog multipliers
6. Phase-locked loop and its applications
7. Detectors of amplitude, frequency and phase
8. Programmable analog circuits and their applications
9. Application specific integrated circuits
10. Digital to analog and analog to digital converters

136



Power amplifiers integrated circuits

Literature:

Józef Boksa, Analogowe układy elektroniczne, BTC, Warszawa 2007
 Zbigniew Nosal, Jerzy Baranowski, Układy Analogowe Liniowe, Wydawnictwa Naukowo Techniczne Warszawa 2003
 Douglas Self, Audio Power Amplifier Design Handbook, Elsevier 2006
 G. Randy Slone, High-Power Audio Amplifier Construction Manual McGraw-Hill 1999

137



Power amplifiers integrated circuits

1. Main issues
2. Classes of power amplifiers
3. Examples of power amplifiers integrated circuits

138



Power Amplifier

- an electronic circuit which main purpose is to deliver required power to the load.
- the last amplifier in a transmission chain (the output stage)
- the amplifier stage that typically requires most attention to power efficiency.

139



Power Amplifiers

- Power not delivered to the load produces heat.
- Large signal amplitudes make nonlinear distortion
- Small signal models do not apply

140



Power amplifier parameters

- Power gain (power dissipated on load to the input power ratio)
- Output power (given in watts by given magnitude of input signal)
- Bandwidth
- Efficiency coefficient (given in percents)
- Total Harmonic Distortion (nonlinear distortion coefficient)

141



Power supplies and Efficiency

$$P_i + P_s = P_o + P_d \leftarrow \text{energy conservation law}$$

P_i – input power

P_s – power taken from power supply

P_o – output power

P_d – power dissipated in circuit


$$\eta = \frac{P_o}{P_s} \cdot 100\% \leftarrow \text{efficiency}$$

Why the power efficiency is so important?

142




Amplitude distortions

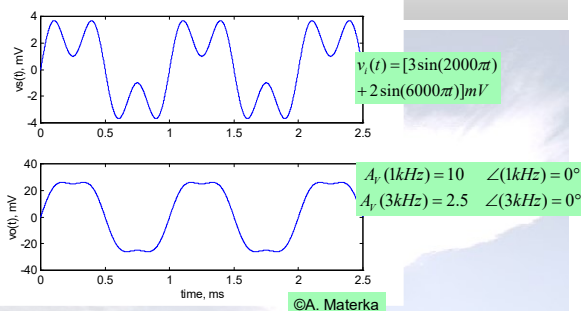

143



Phase distortions

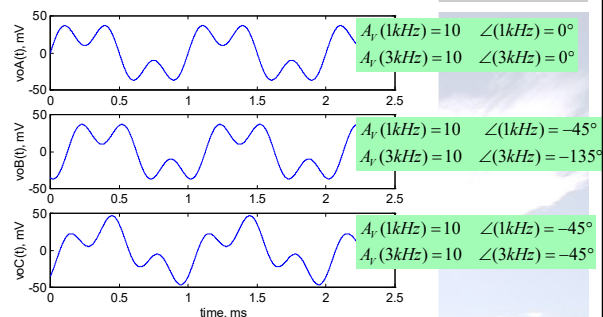

144



Phase distortions

Input signal is the sum of two signals:

1. frequency = 1 kHz; amplitude = 2V
2. frequency = 3 kHz; amplitude = 1V

MatLab simulation:

m-file: PhaseDistortion.m

300 samples

Sampling frequency = 100 kHz



145



Phase distortions

$$A_r(1\text{kHz}) = 4 \quad \angle(1\text{kHz}) = 0^\circ$$
$$A_r(3\text{kHz}) = 4 \quad \angle(3\text{kHz}) = 0^\circ$$
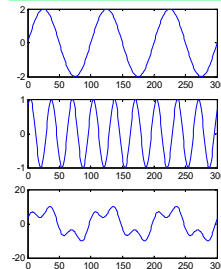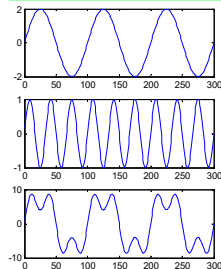
$$A_r(1\text{kHz}) = 4 \quad \angle(1\text{kHz}) = 0^\circ$$
$$A_r(3\text{kHz}) = 4 \quad \angle(3\text{kHz}) = 45^\circ$$





146



Phase distortions

$$A_r(1\text{kHz}) = 4 \quad \angle(1\text{kHz}) = 0^\circ$$
$$A_r(3\text{kHz}) = 4 \quad \angle(3\text{kHz}) = 0^\circ$$
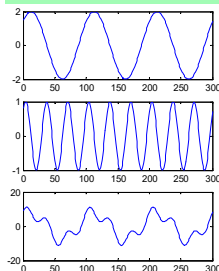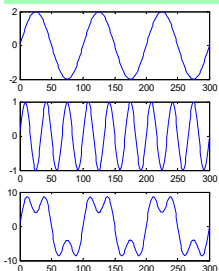
$$A_r(1\text{kHz}) = 4 \quad \angle(1\text{kHz}) = 45^\circ$$
$$A_r(3\text{kHz}) = 4 \quad \angle(3\text{kHz}) = 45^\circ$$





147



Phase distortions

$$A_r(1\text{kHz}) = 4 \quad \angle(1\text{kHz}) = 0^\circ$$
$$A_r(3\text{kHz}) = 4 \quad \angle(3\text{kHz}) = 0^\circ$$
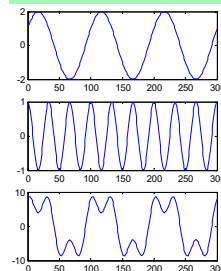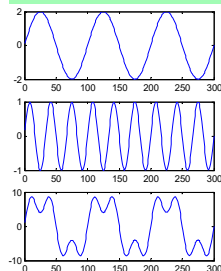
$$A_r(1\text{kHz}) = 4 \quad \angle(1\text{kHz}) = 30^\circ$$
$$A_r(3\text{kHz}) = 4 \quad \angle(3\text{kHz}) = 90^\circ$$





148



Phase distortions

$$A_r(1\text{kHz}) = 4 \quad \angle(1\text{kHz}) = 0^\circ$$
$$A_r(3\text{kHz}) = 4 \quad \angle(3\text{kHz}) = 0^\circ$$
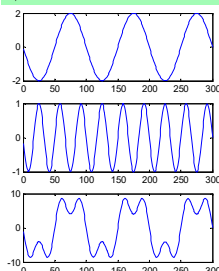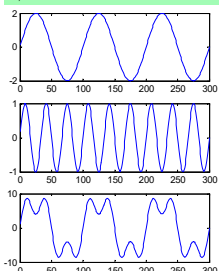
$$A_r(1\text{kHz}) = 4 \quad \angle(1\text{kHz}) = 180^\circ$$
$$A_r(3\text{kHz}) = 4 \quad \angle(3\text{kHz}) = 180^\circ$$





149



Phase distortions

$$A_r(1\text{kHz}) = 4 \quad \angle(1\text{kHz}) = 0^\circ$$
$$A_r(3\text{kHz}) = 4 \quad \angle(3\text{kHz}) = 0^\circ$$
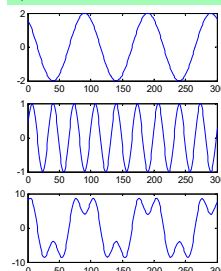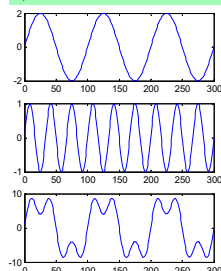
$$A_r(1\text{kHz}) = 4 \quad \angle(1\text{kHz}) = 125^\circ$$
$$A_r(3\text{kHz}) = 4 \quad \angle(3\text{kHz}) = 15^\circ$$



150



Linear Distortion – Conclusions

To avoid linear distortion two conditions should be met:

1. Amplitude condition – gain should be constant in the useful band of signal

$$A(f) = \text{const dla } f \in (f_L, f_H);$$


2. Phase condition – phase should be equal to 0, equal to 180° or proportional to the frequency in the useful band of signal

$$\varphi(f) = 0^\circ, \varphi(f) = 180^\circ, \varphi(f) = k \cdot f \text{ dla } f \in (f_L, f_H)$$

151




Linear distortions

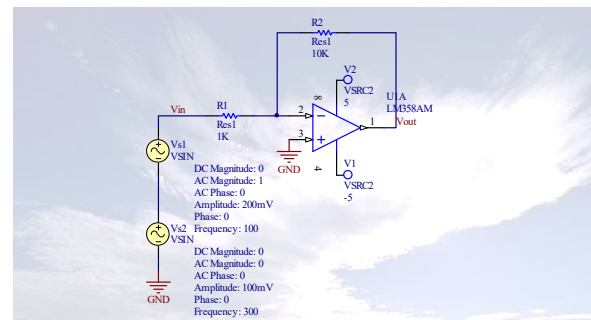


152




Linear distortions

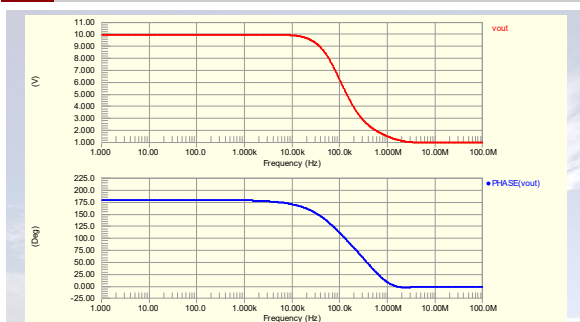


Linear distortions

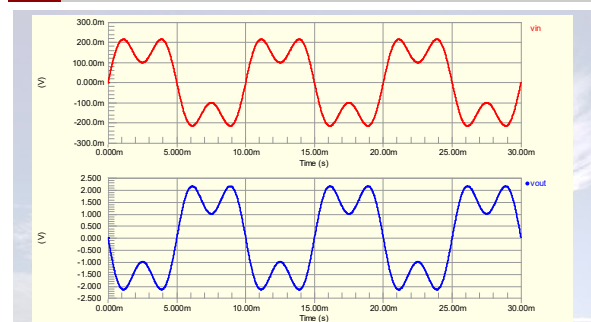







Linear distortions






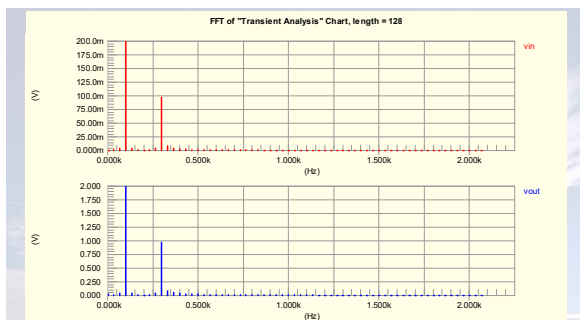


Linear distortions

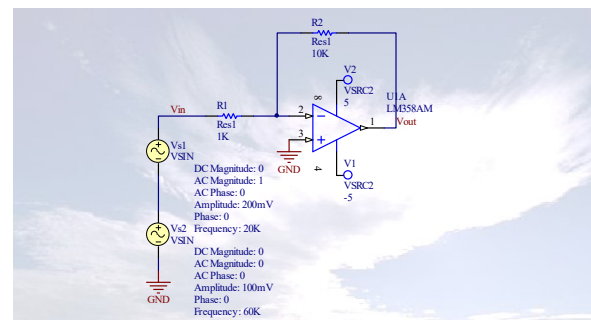


156

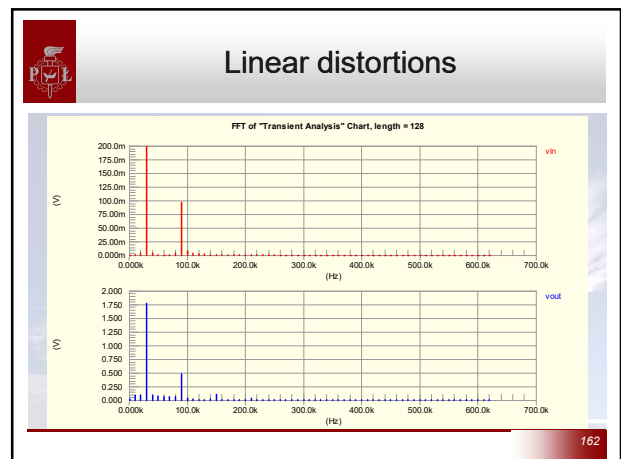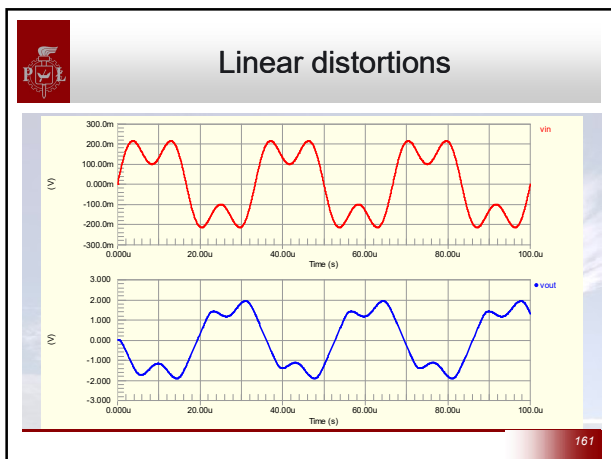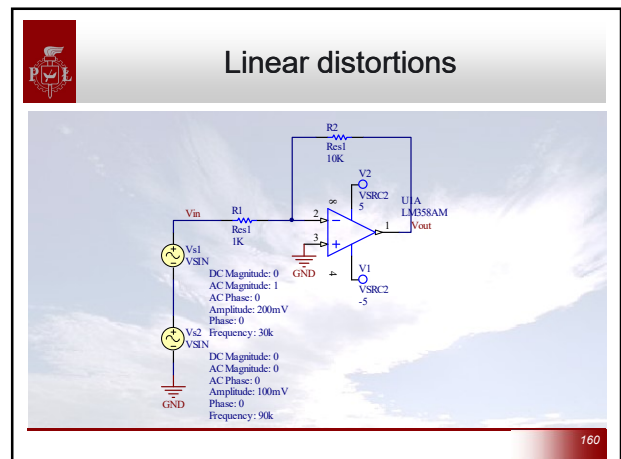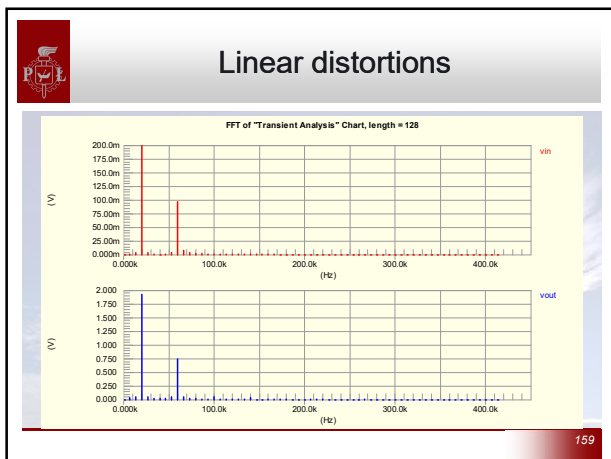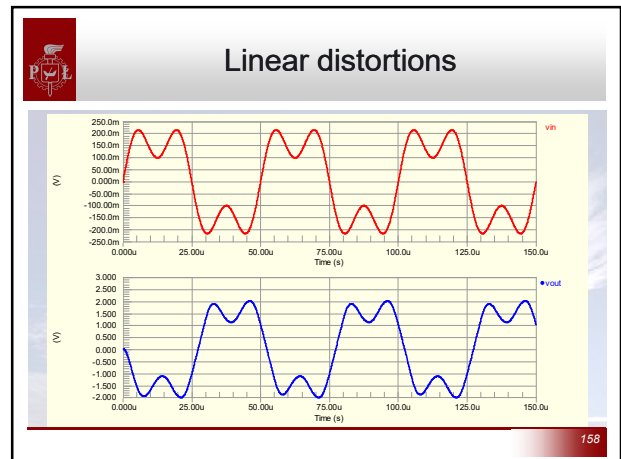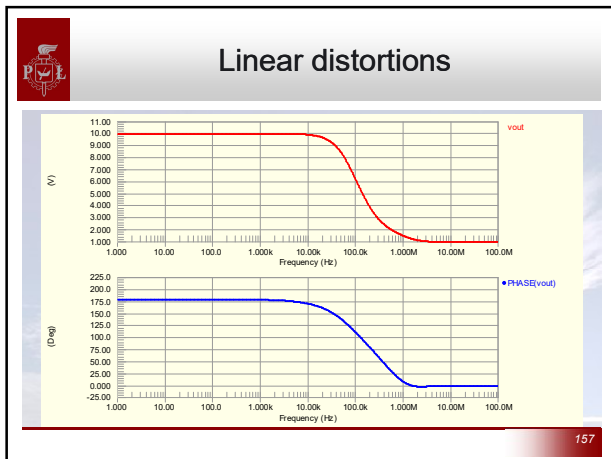

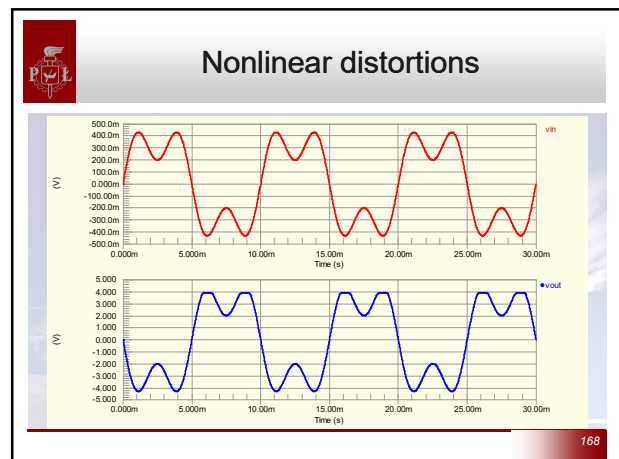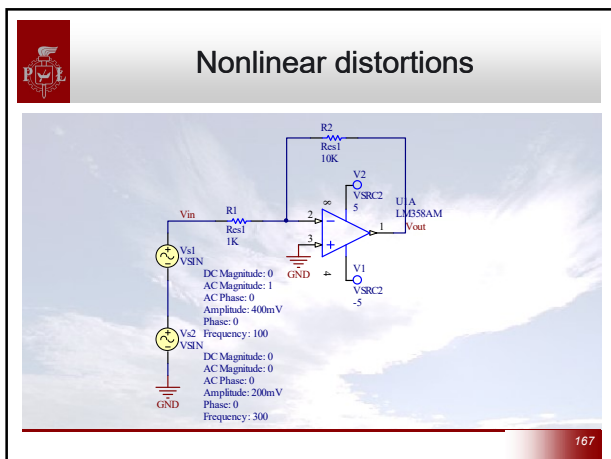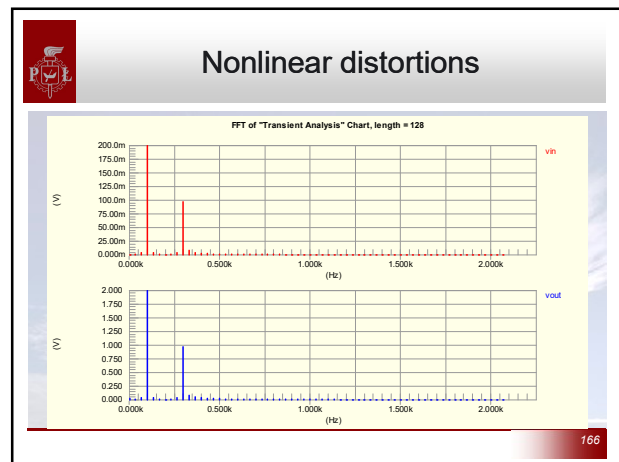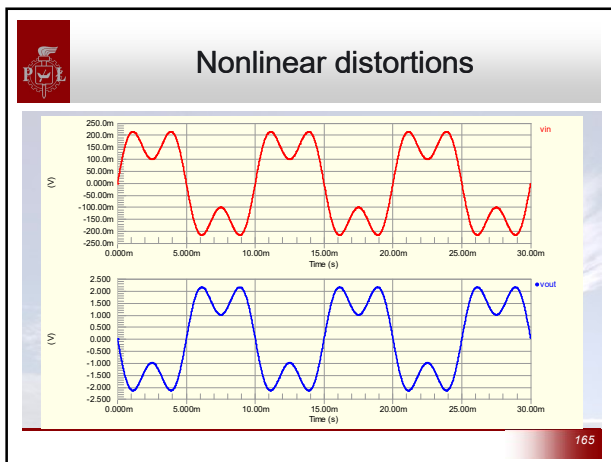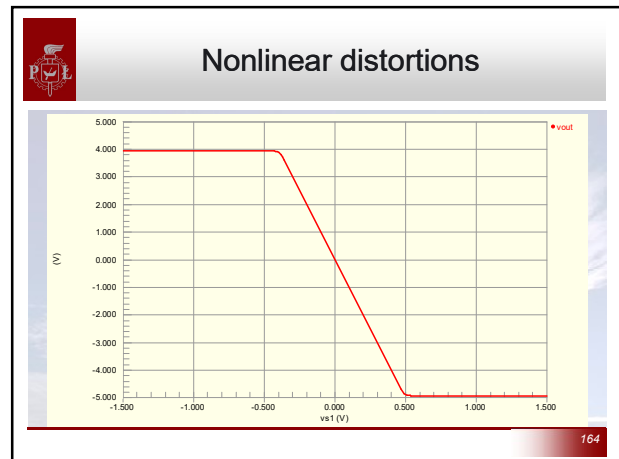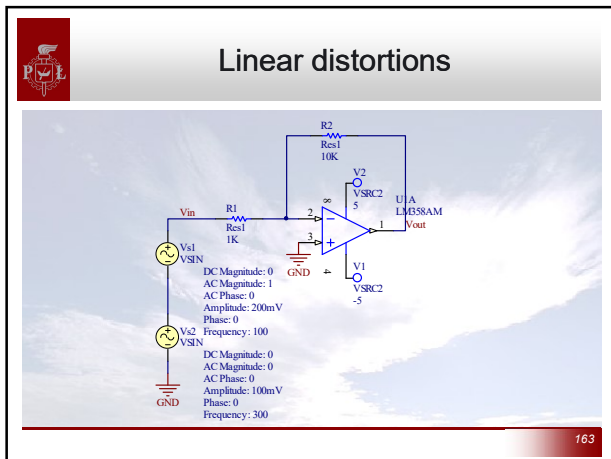




Nonlinear distortions

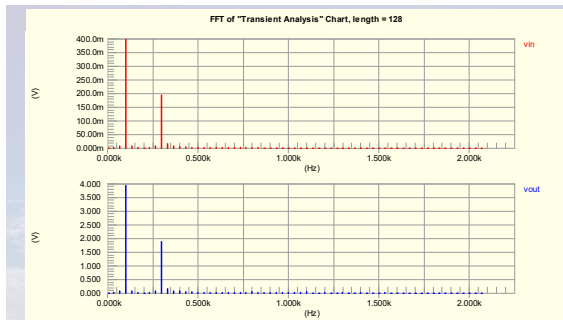

169




Nonlinear distortions

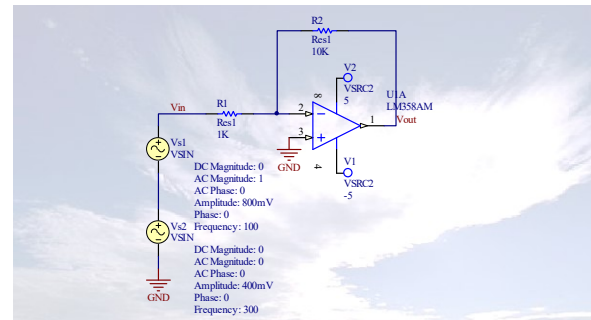

170




Nonlinear distortions

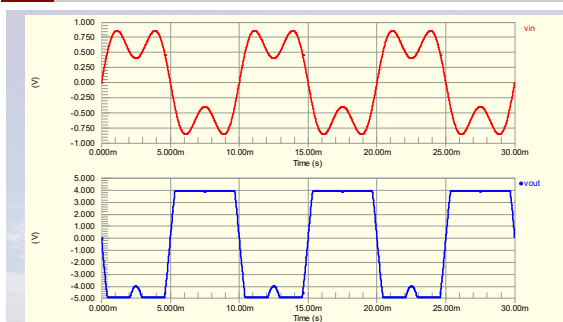

171




Nonlinear distortions

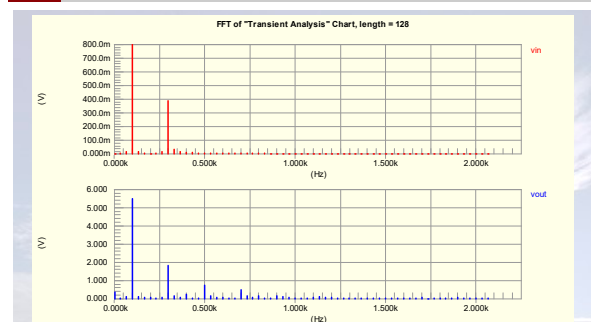

172




Nonlinear distortions

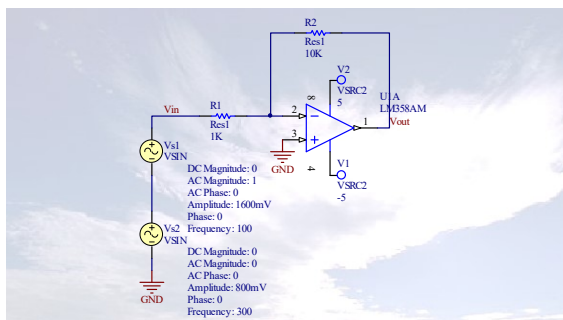


173



Nonlinear distortions

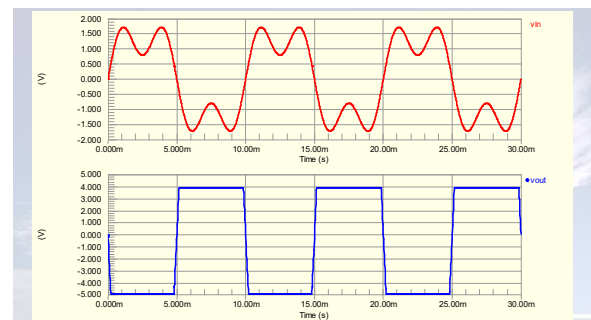

174

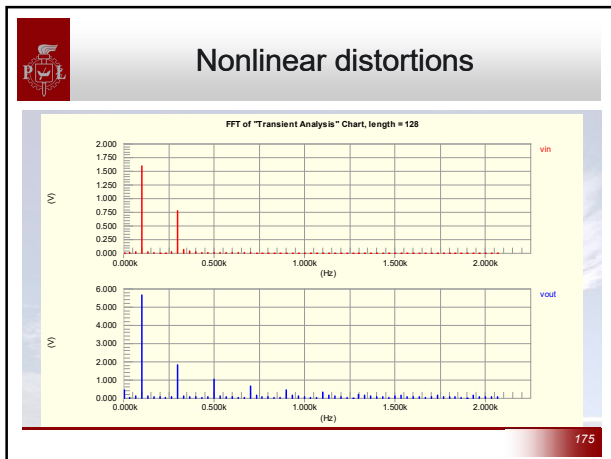

Nonlinear distortions

Nonlinear distortions cause in output signal occurrence of **harmonics** not present in input signal

Total Harmonic Distortion

Effective value of voltage for higher harmonics to the fundamental ratio measured for sine wave input signal

$$THD = \frac{\sqrt{\sum_{k=2}^n V_k^2}}{V_1}$$

where:
 V_1 - effective value of voltage for fundamental
 V_k - effective value of voltage for k harmonic

$$THD + N = \frac{\sqrt{V_n^2 + \sum_{k=2}^n V_k^2}}{V_1}$$

where:
 V_n - effective value of voltage for noise

- ### THD in audio systems
- 10% (-20dB) – clearly sensed distortion (improper for audio systems)
 - 1% (-40dB) – acceptable distortion level in simple audio systems, can be sensed in hifi for listeners with trained musical hearing
 - 0,1% (-60dB) – widely accepted distortion level skipping high end HiFi systems
 - 0,01% (-80dB) – distortion level representative for high end HiFi systems, accepted by audiophiles
 - 0,001% (-100dB) – distortion level beyond possibilities of audio systems.
 - 0,0001% (-120dB) – level comparable with state of art measurement techniques

Decibel notation

Absolute values


$A_{vdB} = 20 \log |A_v| \text{ dB}$ Voltage gain







$A_{idB} = 20 \log |A_i| \text{ dB}$ Current gain







$G_{dB} = 10 \log G \text{ dB}$ Power gain $G = A_i^2 \frac{R_o}{R_i}$







$A_v = 100$	40 dB,	$G = 100$	20 dB,
$A_v = 10$	20 dB,	$G = 10$	10 dB,
$A_v = 1$	0 dB,	$G = 1$	0 dB,
$A_v = 0.1$	-20 dB,	$G = 0.1$	-10 dB,



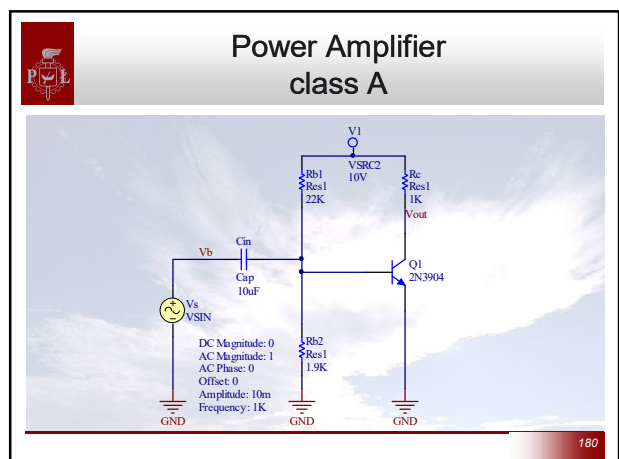
$G_{dB} = A_{vdB} \Leftrightarrow R_L = R_i$



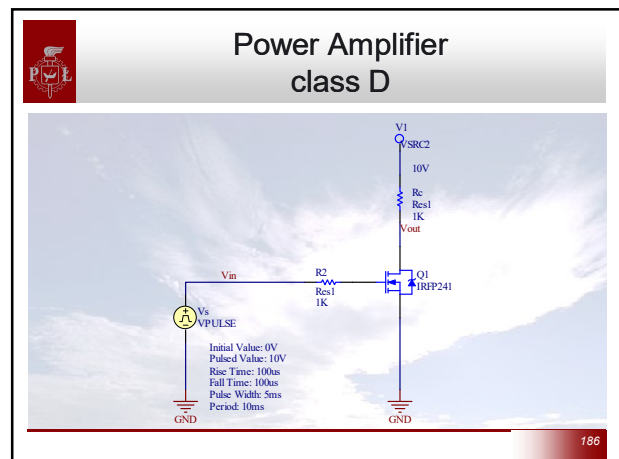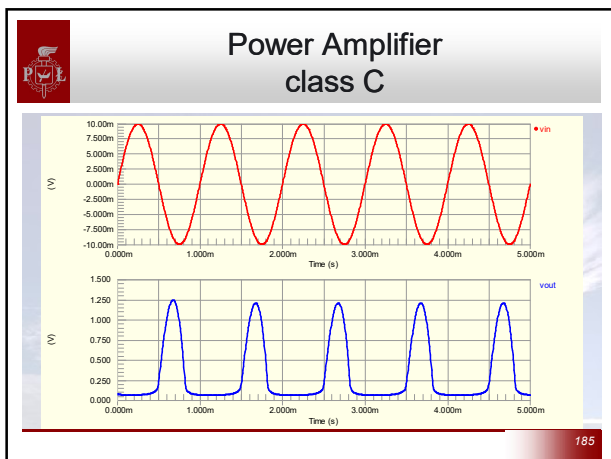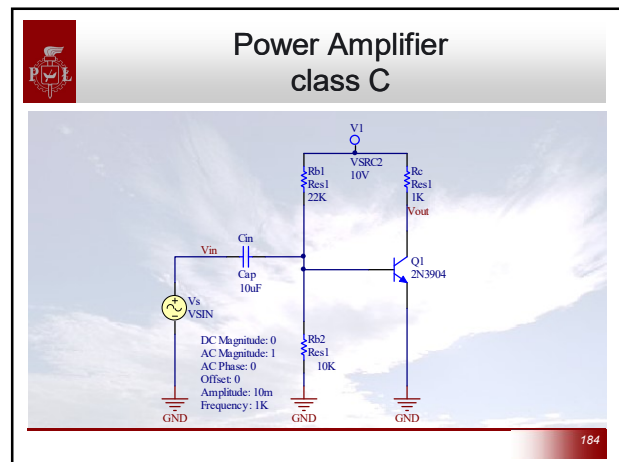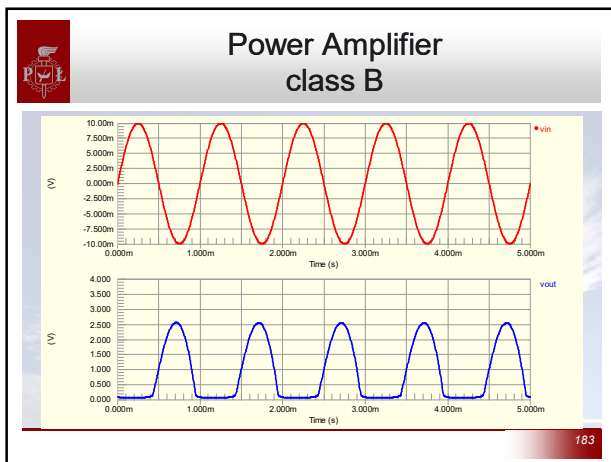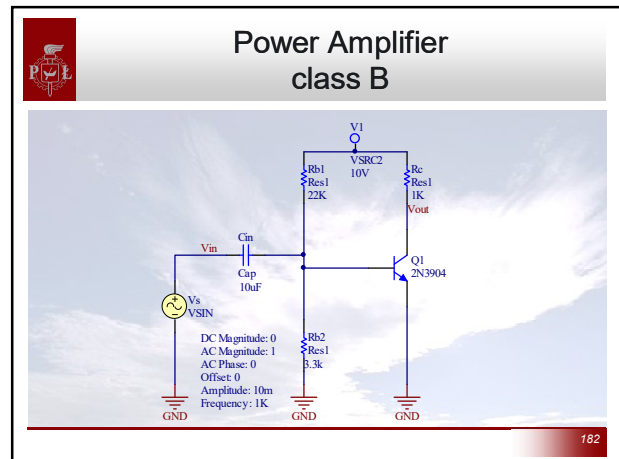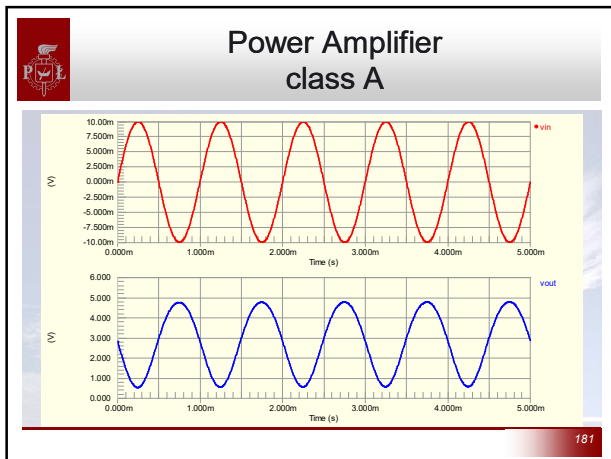

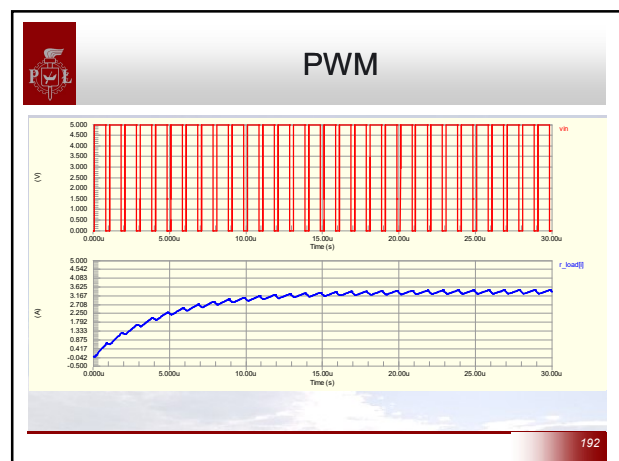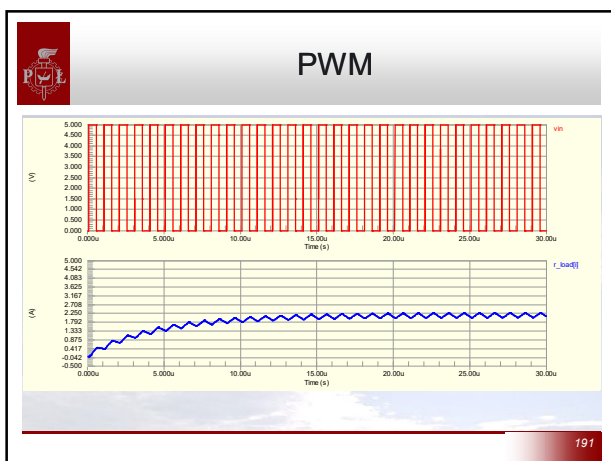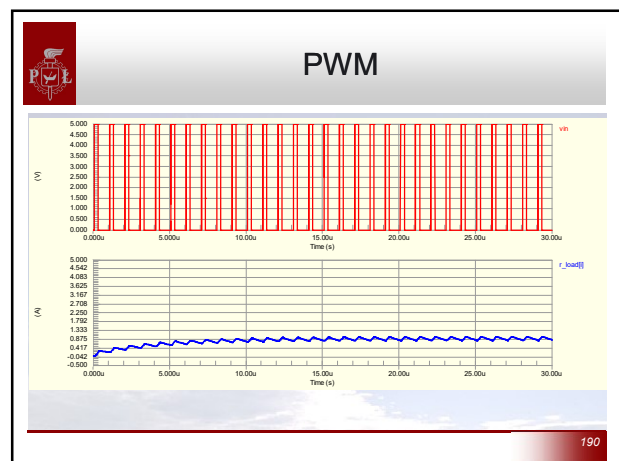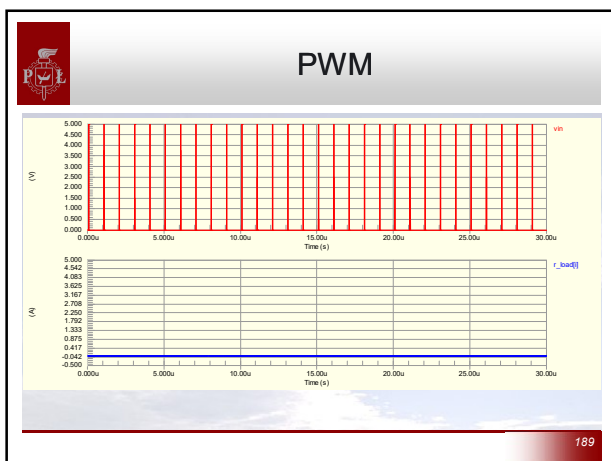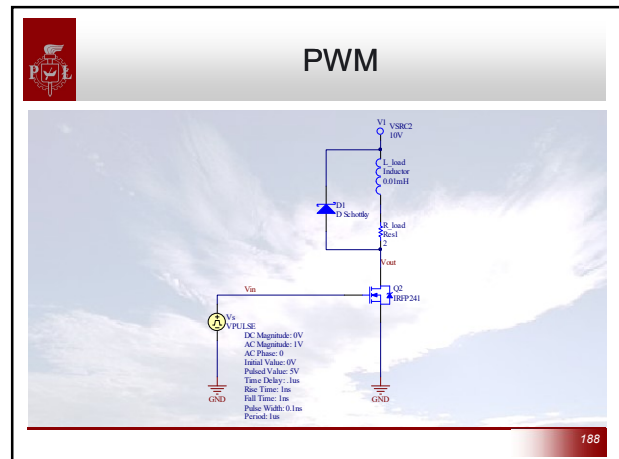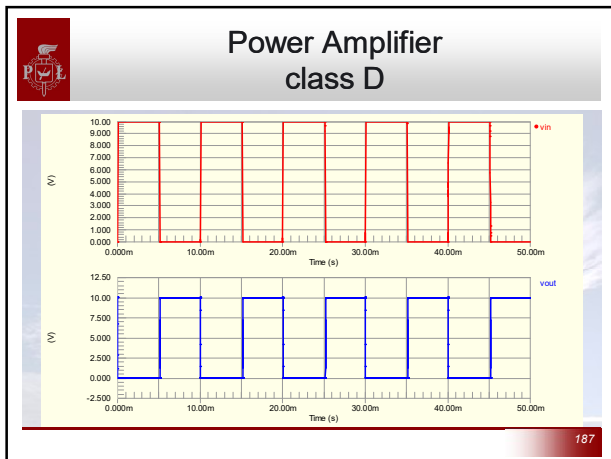

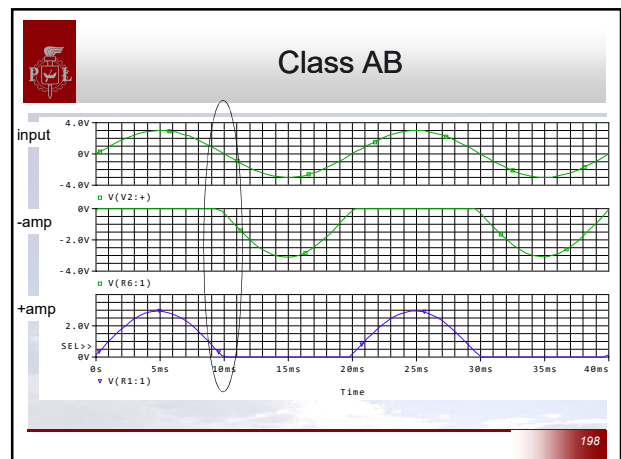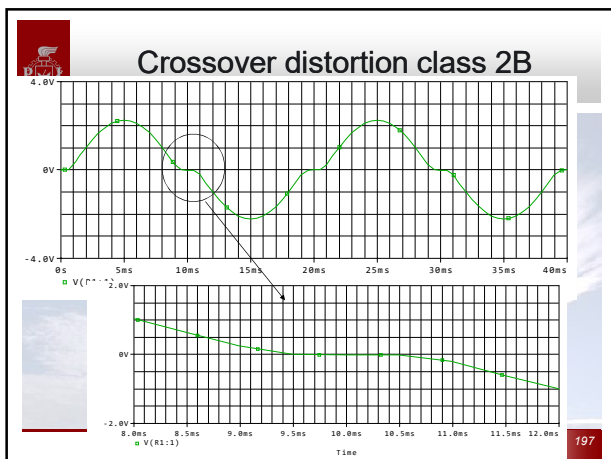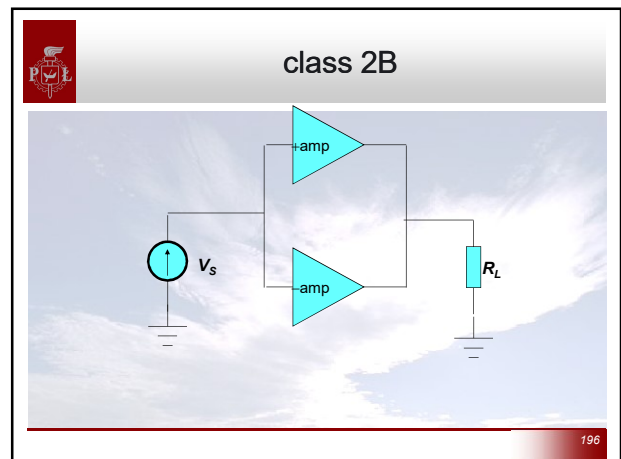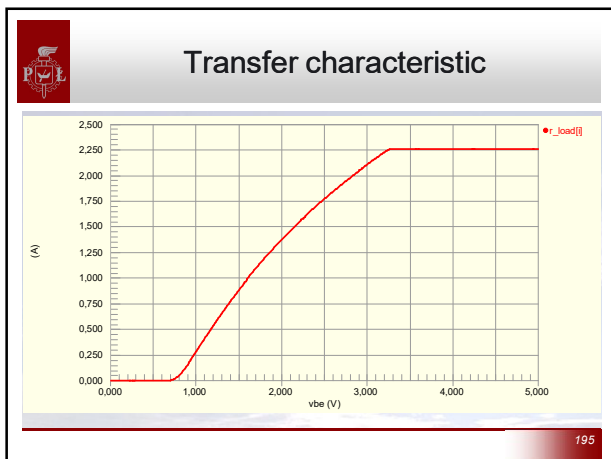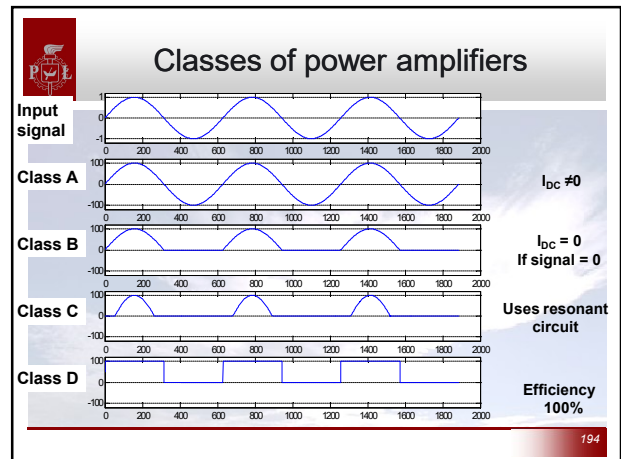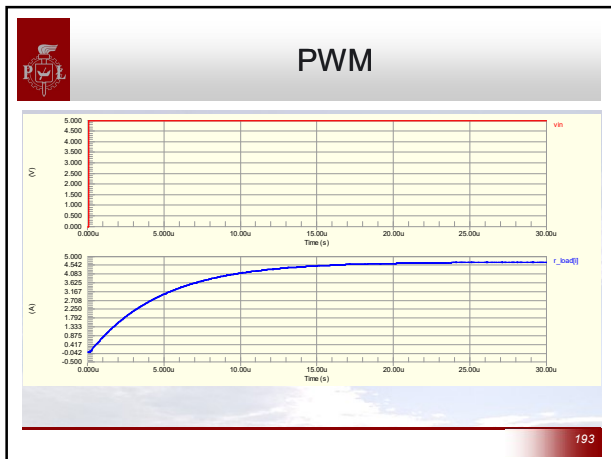

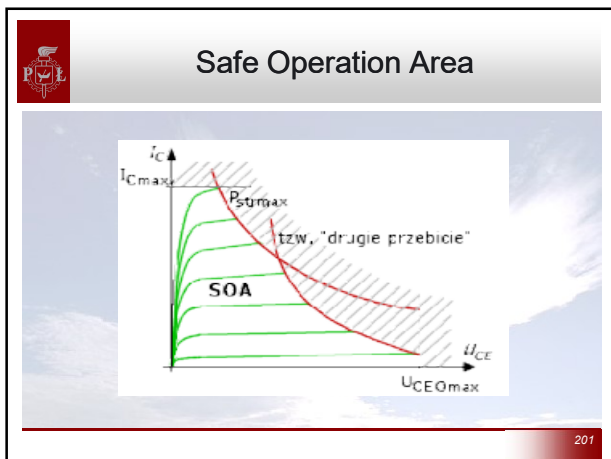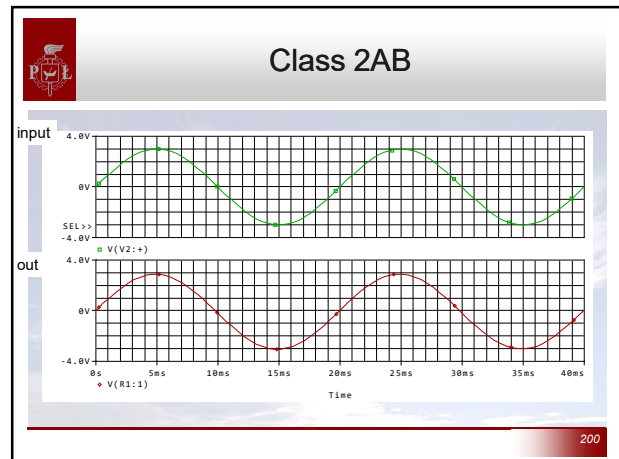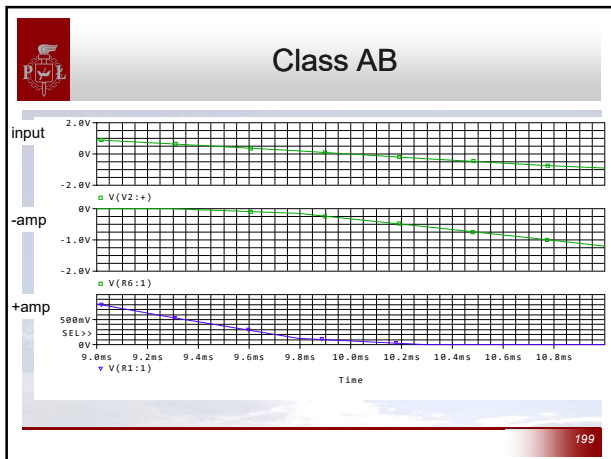

- ### Układy scalone wzmacniaczy mocy.
- LM380 2.5W Audio Power Amplifier
 - TDA7052 1 W BTL mono audio amplifier
 - LM4780 Overture™ Audio Power Amplifier Series Stereo 60W, Mono 120W Audio Power Amplifier with Mute
 - TDA8920B 2 x 100 W class-D power amplifier
 - Class D Audio Amplifier Design International amplifier <http://www.irf.com/product-info/audio/classdtutorial.pdf>
- 202

- ### Lecture Plan
1. Noise in active circuits
 2. Power amplifiers integrated circuits.
 3. **Broadband and impulse amplifiers integrated circuits**
 4. Active analog filters with continuous and discrete time
 5. Analog multipliers
 6. Detectors of amplitude, frequency and phase
 7. Phase-locked loop and its applications
 8. Programmable analog circuits and their applications.
 9. Application specific integrated circuits.
 10. Digital integrated circuits.
- 203

- ### Broadband and impulse amplifiers integrated circuits
- Literature:
- Józef Boksa, Analogowe układy elektroniczne, BTC, Warszawa 2007
- Waldemar Nawrocki, Krzysztof Arnold, Krzysztof Lange, Układy Elektroniczne, Wydawnictwo Politechniki Poznańskiej, Poznań 1999
- Zbigniew Nosal, Jerzy Baranowski, Układy Analogowe Liniowe, Wydawnictwa Naukowo Techniczne Warszawa 2003
- 204



Broadband and impulse amplifiers integrated circuits

1. Introduction
2. Relations between frequency characteristic and impulse response of linear circuits
3. Examples of broadband amplifiers integrated circuits

205



Band pass amplifiers integrated circuits

Very large bandwidth

$$(f_h - f_l) > \text{MHz}$$

$$\frac{f_h}{f_l} > 10$$


Example of applications:

- CRT TV receivers (30Hz - 6MHz)
- oscilloscopes (DC - few GHz)
- Radar equipment (> 20 GHz)
- Fiber optic telecommunication (100kHz – 25GHz)

206




Impulse response of amplifiers

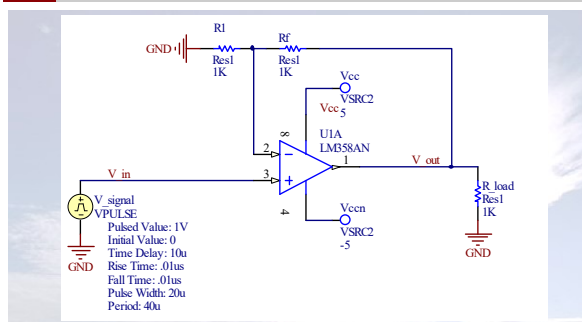

207




Impulse response of amplifiers

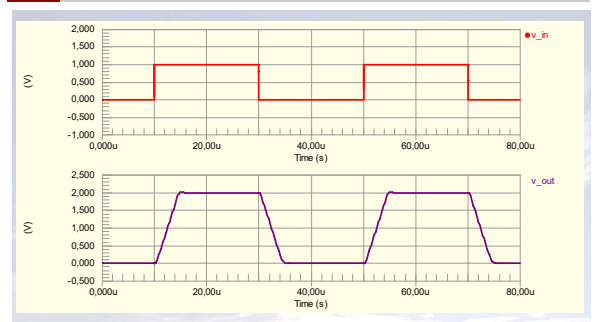

208




Impulse response of amplifiers

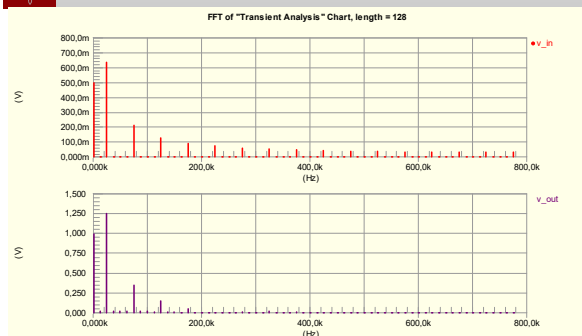







209















Impulse response of amplifiers


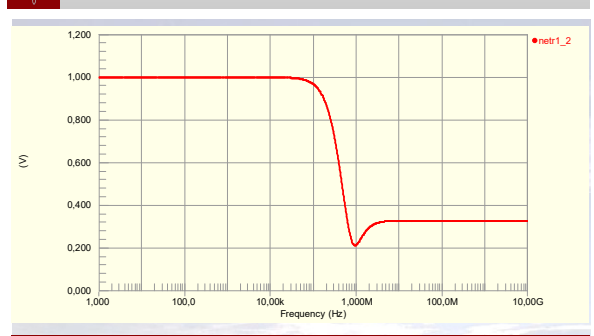


210

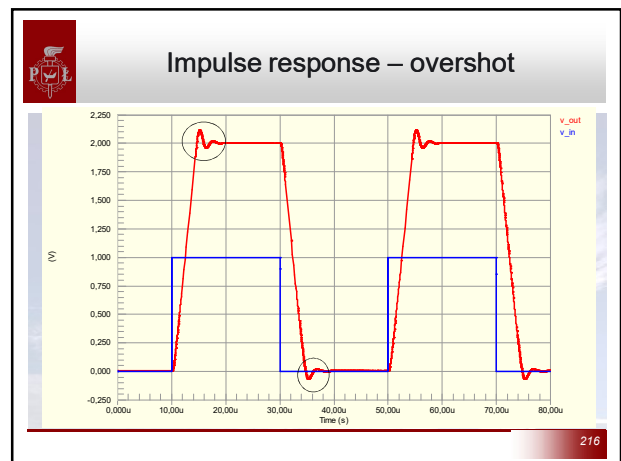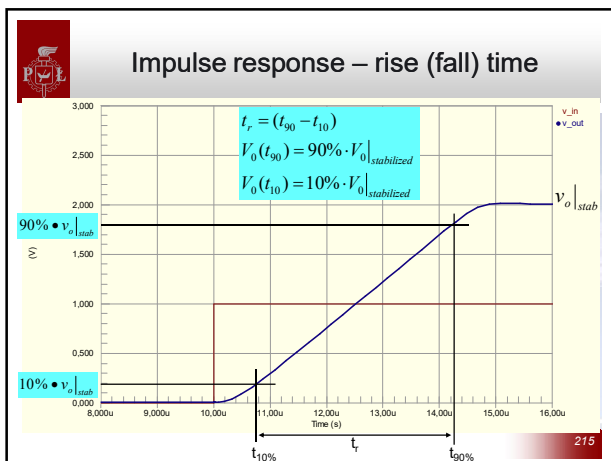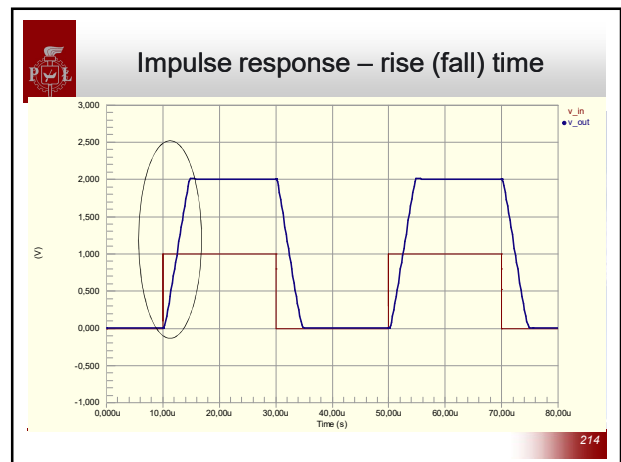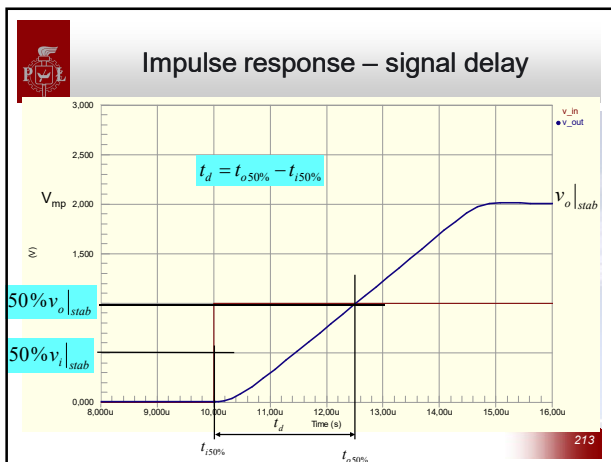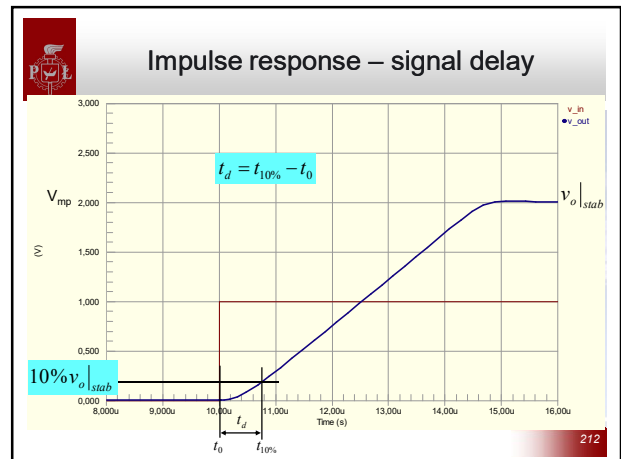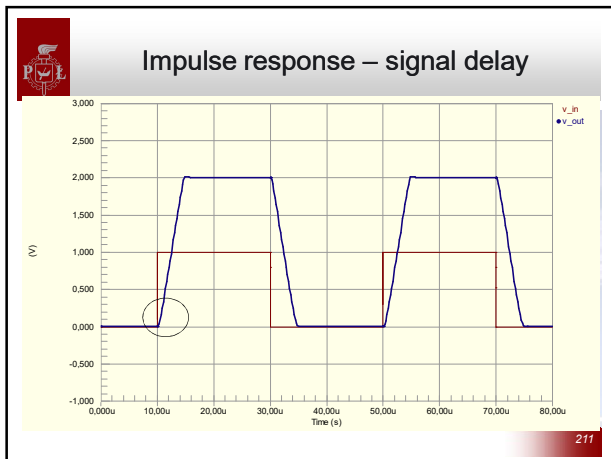

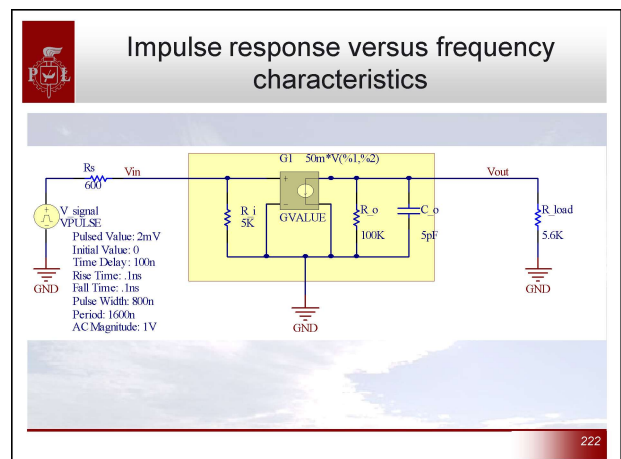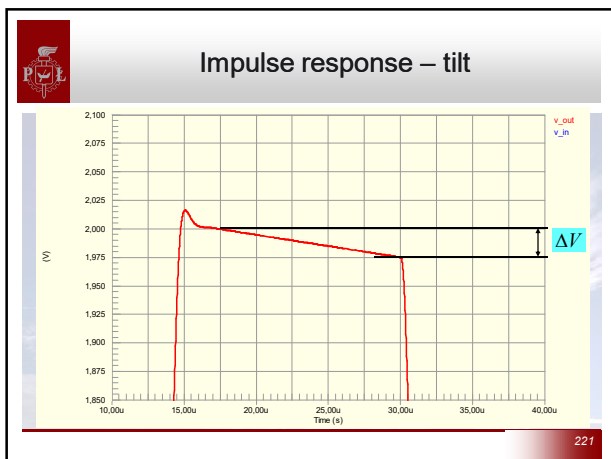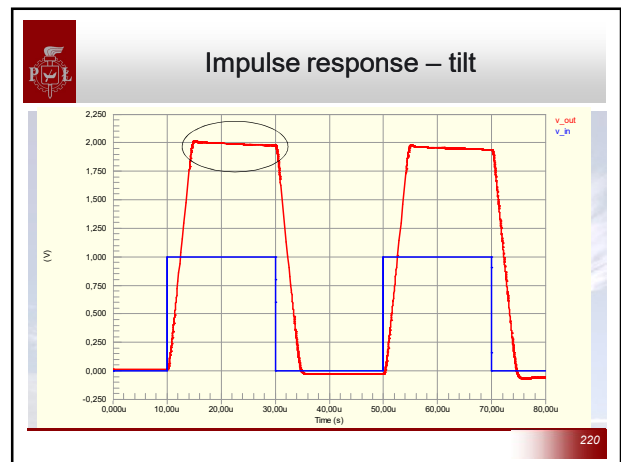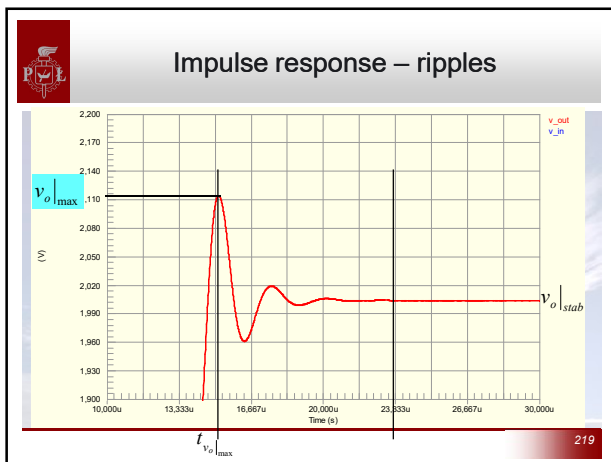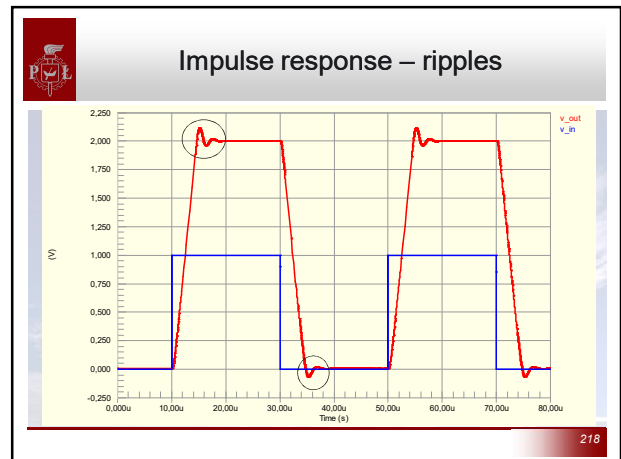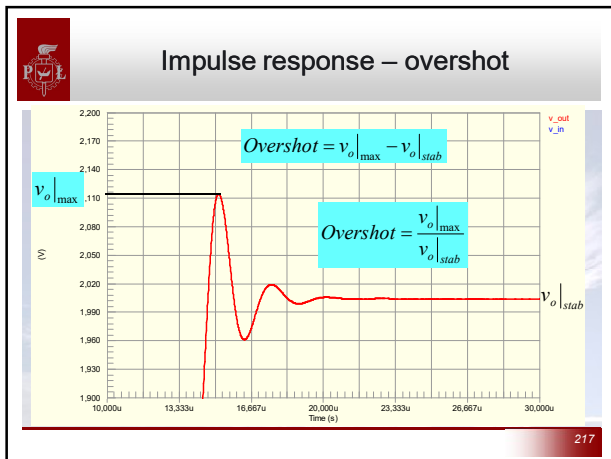

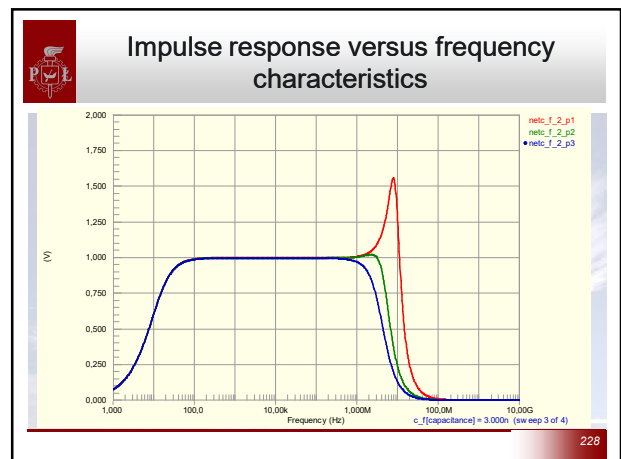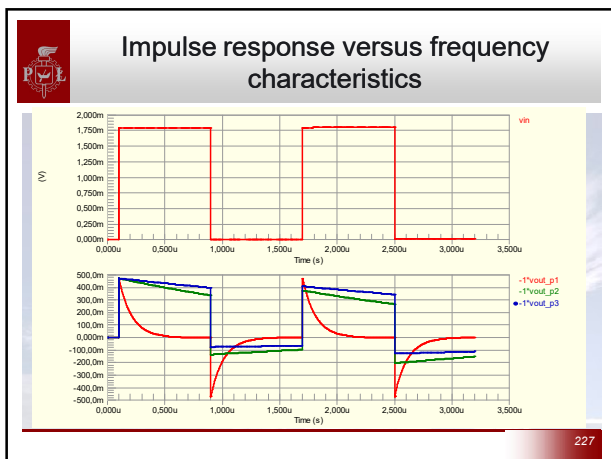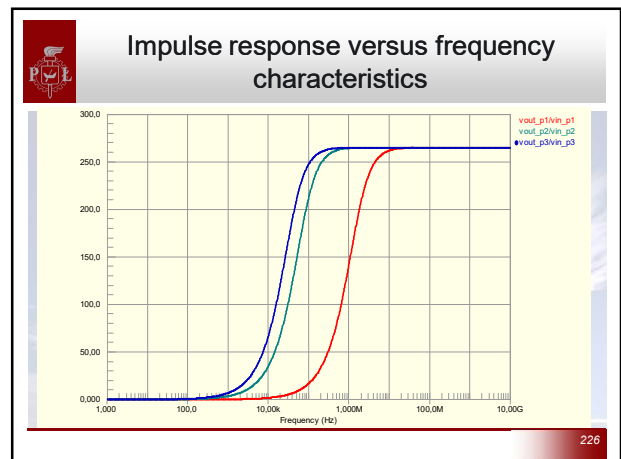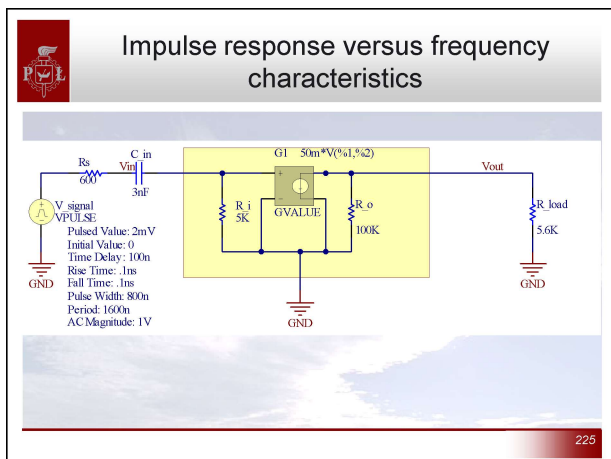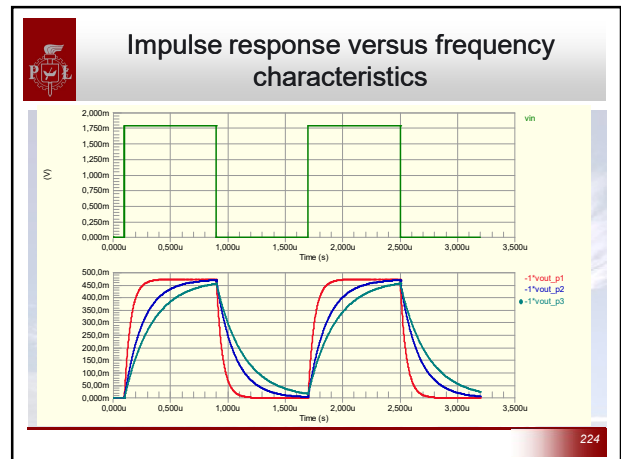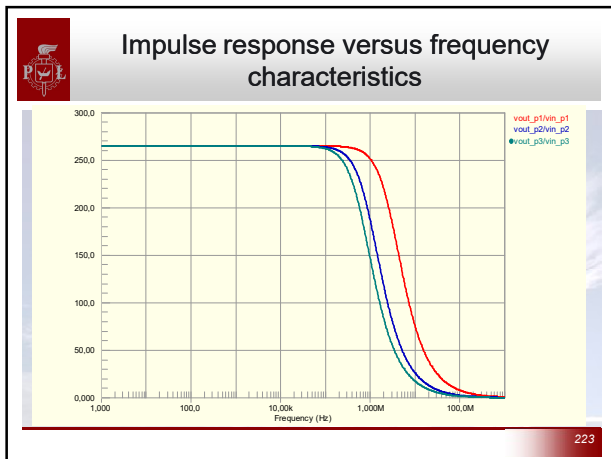

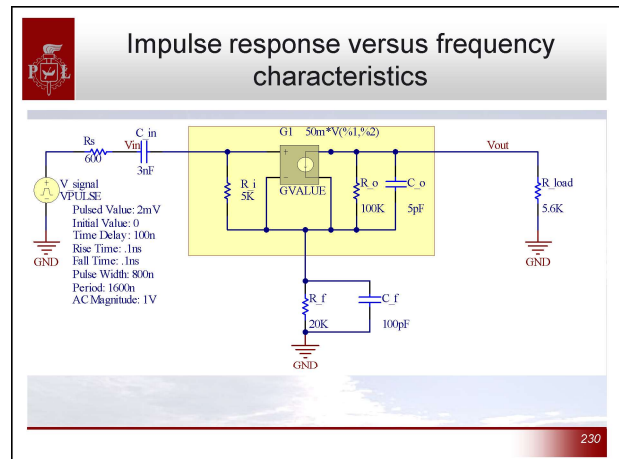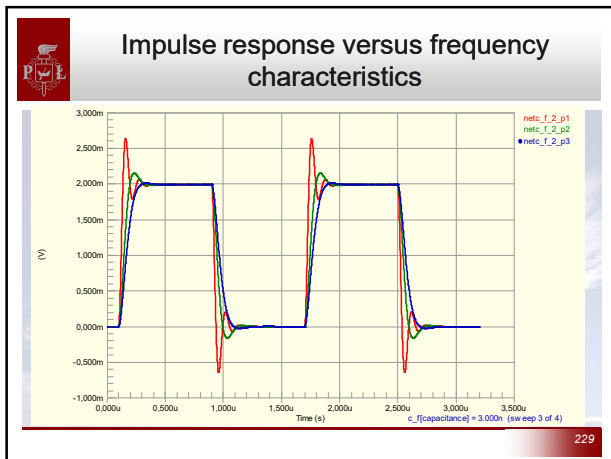

- ### Impulse response summary
- Impulse response determine dynamic behavior of an amplifier
 - There are 5 types of impulse response distortions:
 - delay
 - mild slope
 - overshoot
 - ripples
 - tilt
- 231

Relations between frequency characteristic and impulse response

$$h(t) = \mathcal{L}^{-1} \left[\frac{k(s)}{s} \right]$$
 Circuit response for unity excitation $1(t)$
 Where: $k(s)$ – circuit transfer function

$$\lim_{t \rightarrow \infty} h(t) = \lim_{\omega \rightarrow 0} k(j\omega)$$
 Circuit response for spine of the impulse is related to the shape of the frequency characteristics $k(j\omega)$ for the low frequencies

$$\lim_{t \rightarrow 0} h(t) = \lim_{\omega \rightarrow \infty} k(j\omega)$$
 Circuit response for edge of the impulse is related to the shape of the frequency characteristics $k(j\omega)$ for the high frequencies

232

Relations between frequency characteristic and impulse response

One pole low pass transfer function

$$k(s) = \frac{k_0}{1 + \frac{s}{\omega_h}} \quad h(t) = 1k_0 (1 - e^{-t\omega_h})$$

$$t_r = t_{90\%} - t_{10\%} \quad t_{90\%} = t|_{h(t)=0.9k_0} \quad t_{10\%} = t|_{h(t)=0.1k_0}$$

$$t_r = \frac{2,303}{\omega_h} - \frac{0,105}{\omega_h} = \frac{2,198}{\omega_h} = \frac{2,198}{2\pi f_h} \approx \frac{0,35}{f_h}$$

233







Relations between frequency characteristic and impulse response







One pole high pass transfer function







$$k(s) = \frac{k_0}{1 + \frac{\omega_l}{s}} \quad h(t) = 1k_0 e^{-t\omega_l}$$







$$\Delta V = \frac{h(0) - h(t)}{h(0)} = \frac{1k_0 - 1k_0 e^{-t\omega_l}}{1k_0} = 1 - e^{-t\omega_l} \approx t\omega_l \Big|_{t \ll \frac{1}{\omega_l}}$$

234

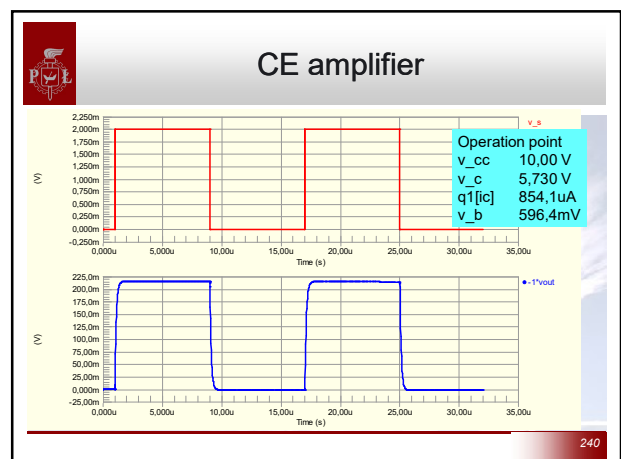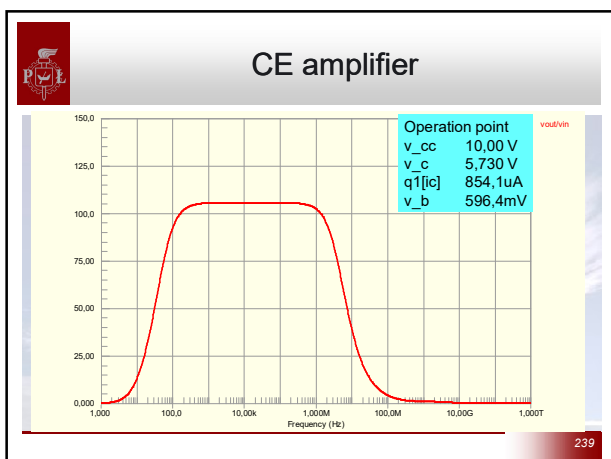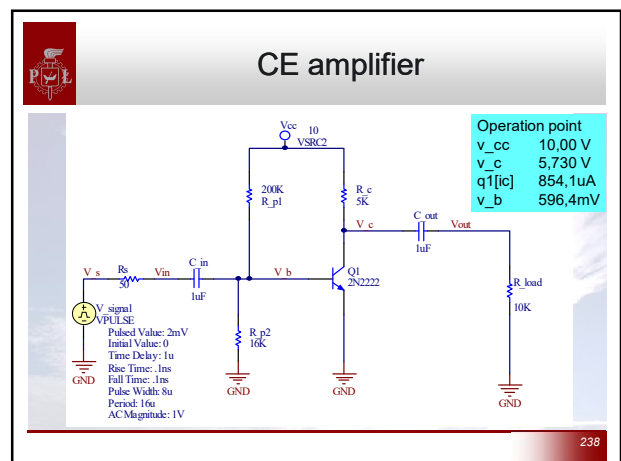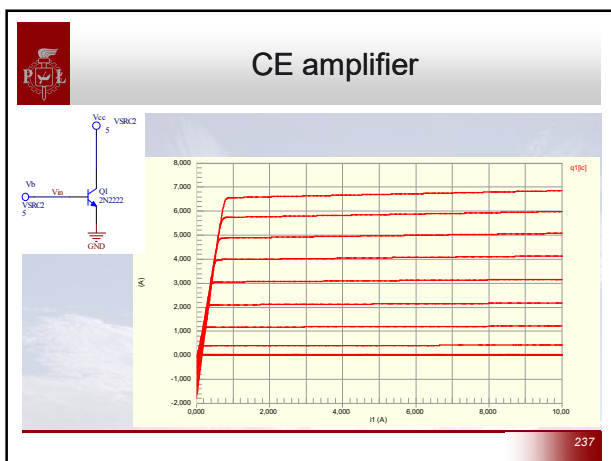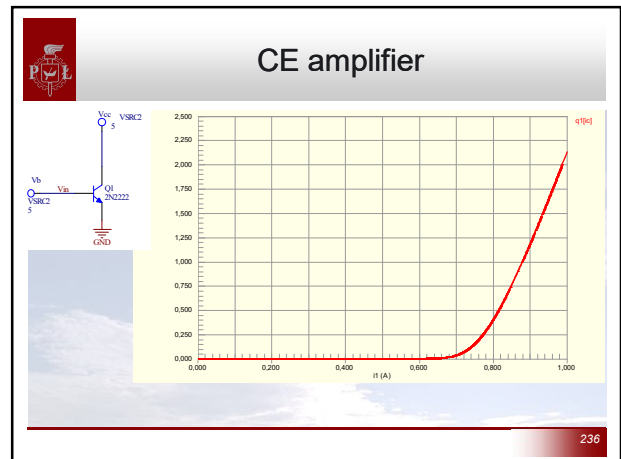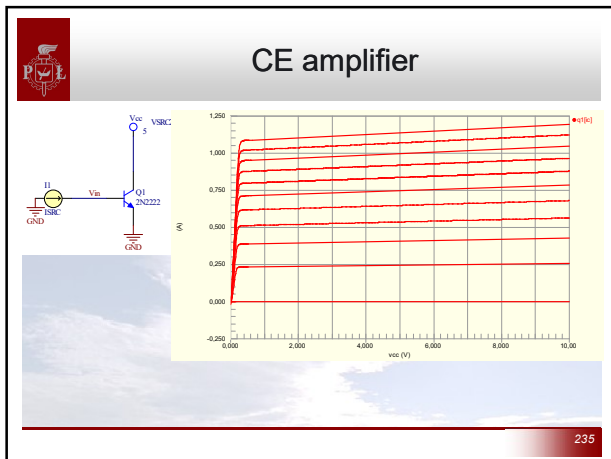

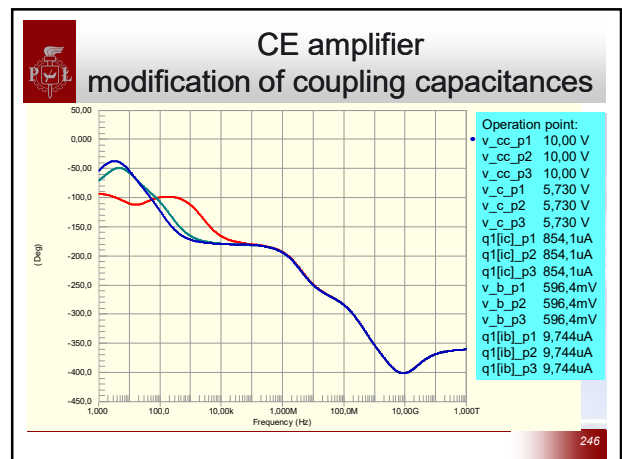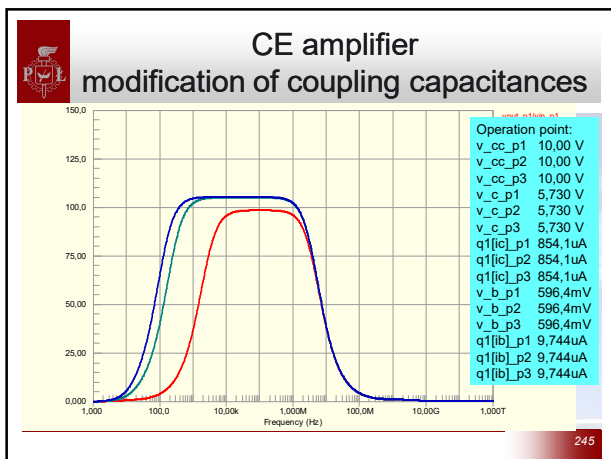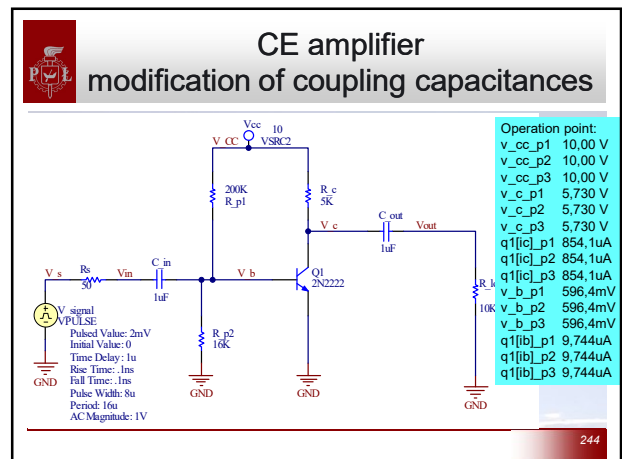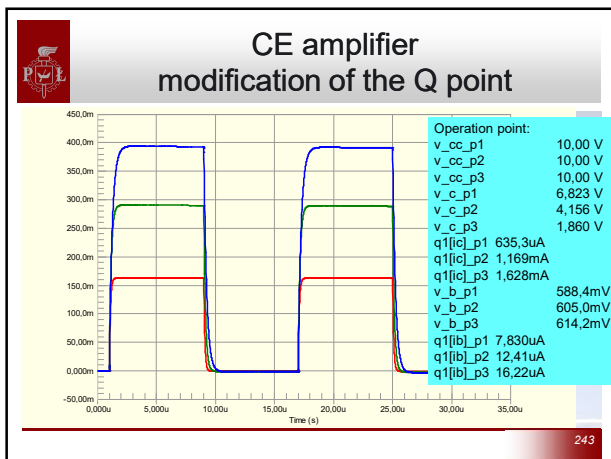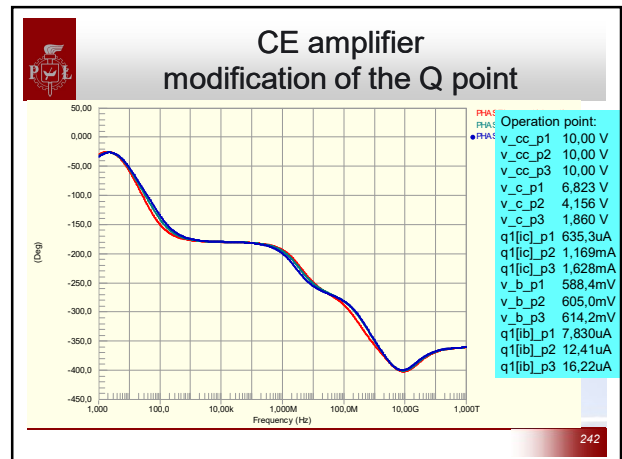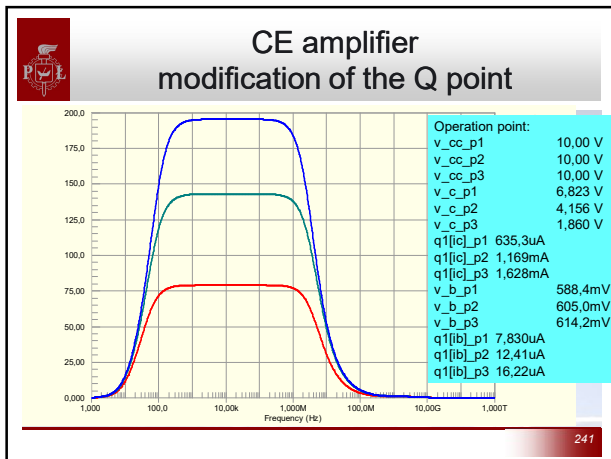


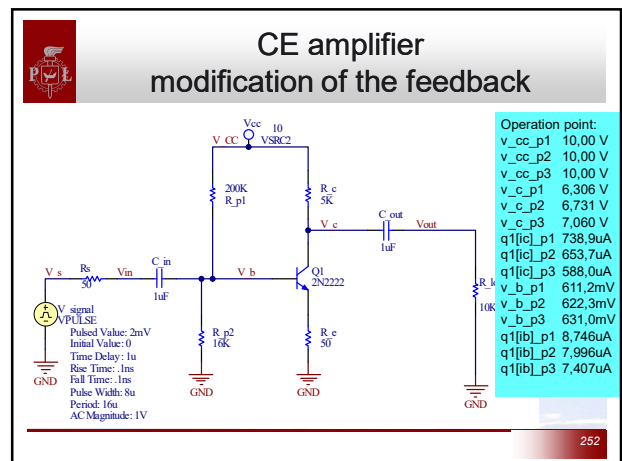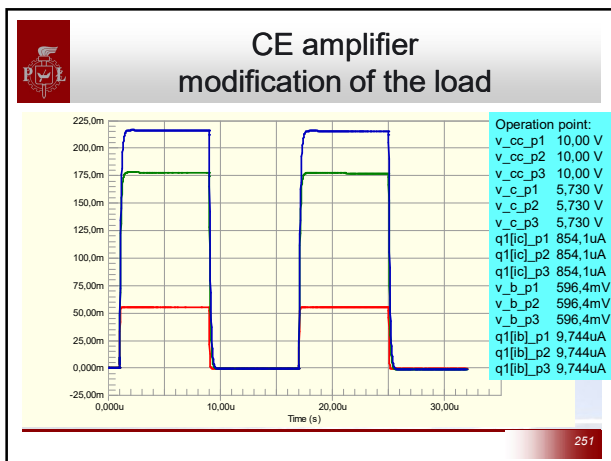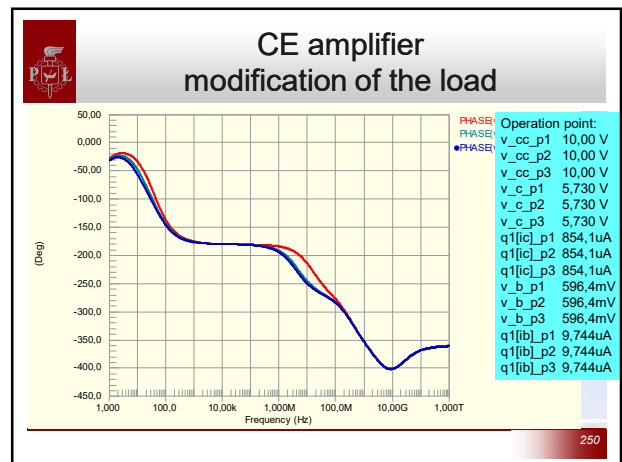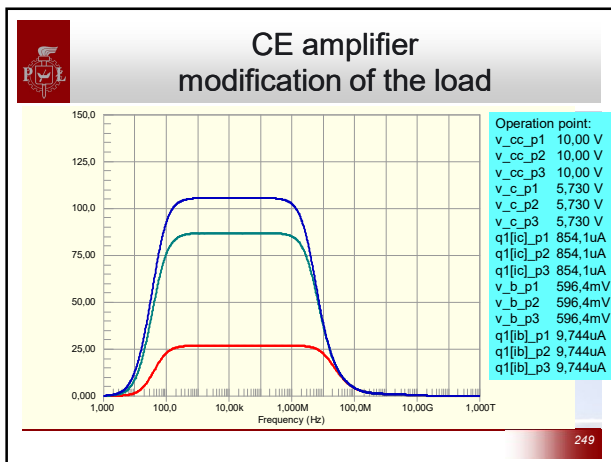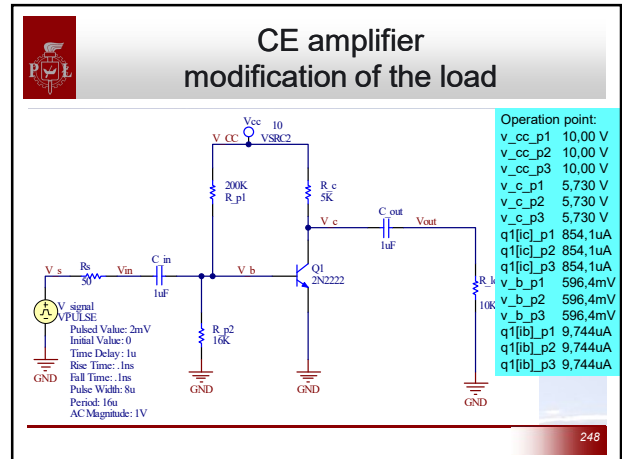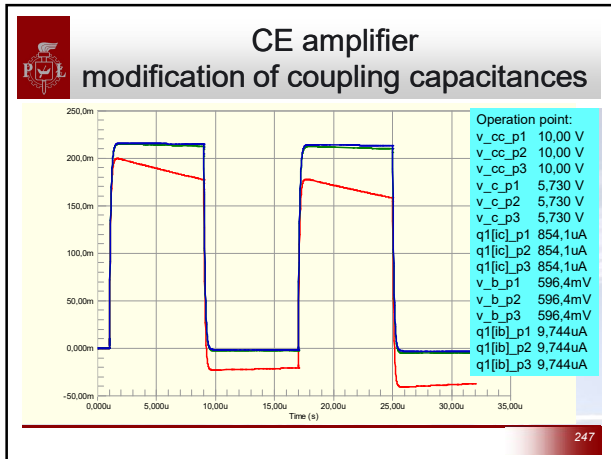

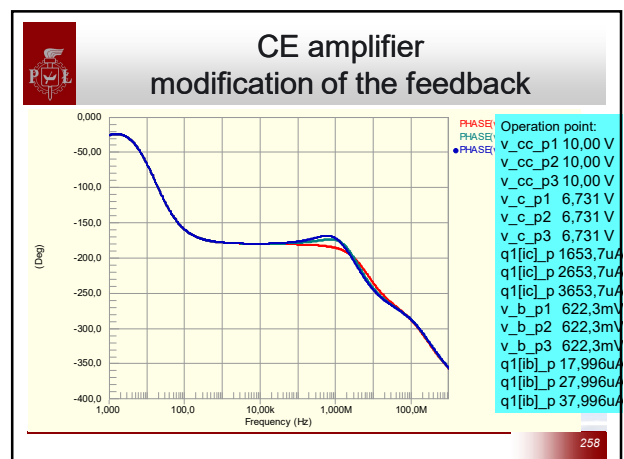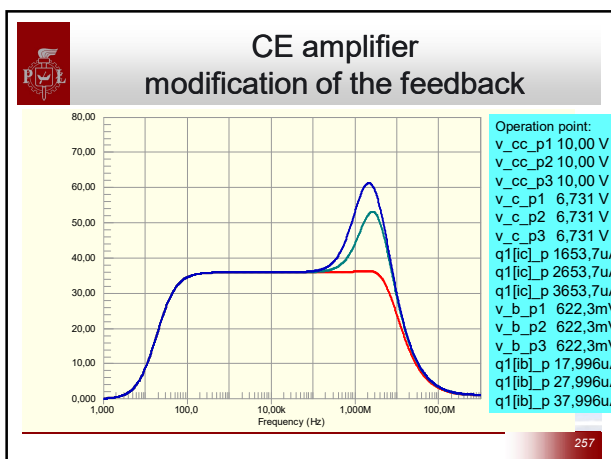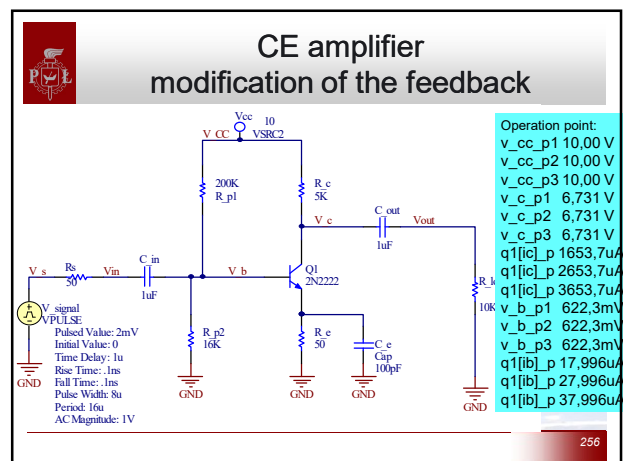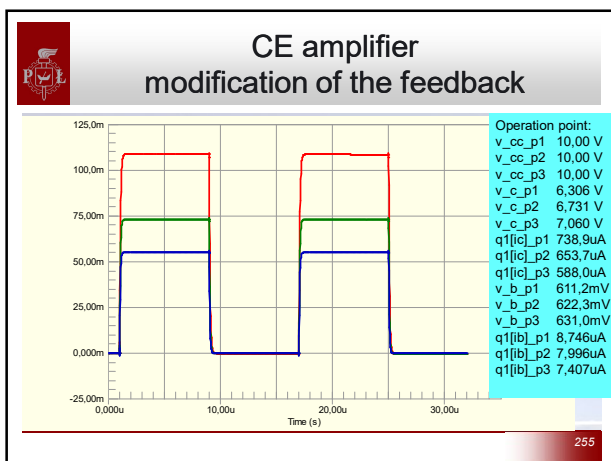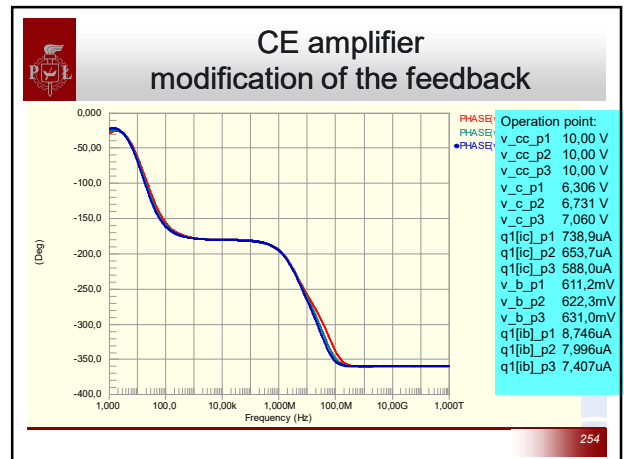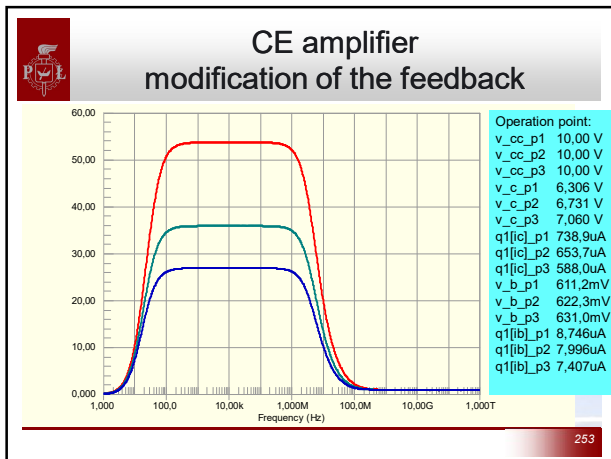



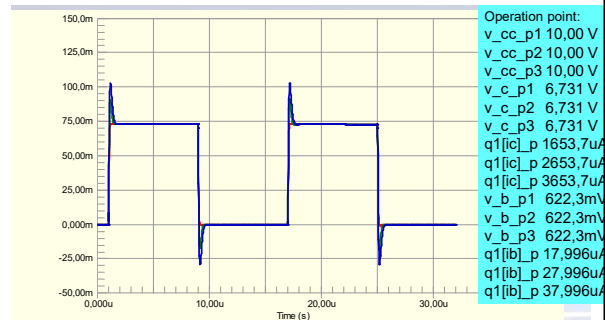CE amplifier modification of the feedback



259



Broad band and impulse amplifier integrated circuits

- LM2904, LM358/ LM358A, LM258/ LM258A Dual Operational Amplifier
- AD829 High Speed, Low Noise Video Op
- AD8597/AD8599 Single and Dual, Ultralow Distortion, Ultralow Noise Op Amps
- TL072 TL072A TL072B Low noise JFET dual operational amplifiers

260



Lecture Plan

1. Noise in active circuits
2. Power amplifiers integrated circuits.
3. Broadband and impulse amplifiers integrated circuits
4. **Active analog filters with continuous and discrete time**
5. Analog multipliers
6. Detectors of amplitude, frequency and phase
7. Phase-locked loop and its applications
8. Programmable analog circuits and their applications.
9. Application specific integrated circuits.
10. Digital integrated circuits.

261



Active analog filters with continuous and discrete time

Literature:

U. Tietze, Ch. Shenck, Electronics circuits, design and applications, Springer-Verlag, 2001

262



Active analog filters with continuous and discrete time

1. Passive filters
2. Filter types
3. Active filters of the continuous time
4. Switched capacitance filters
5. DSP filters
6. Examples of integrated circuits with analog filters







263



Filter

The piece of electric or electronic circuit responsible for passing or blocking signals with certain band or having specified harmonics

264

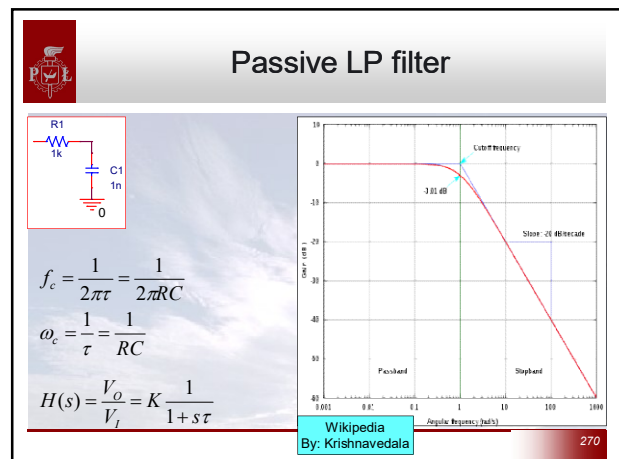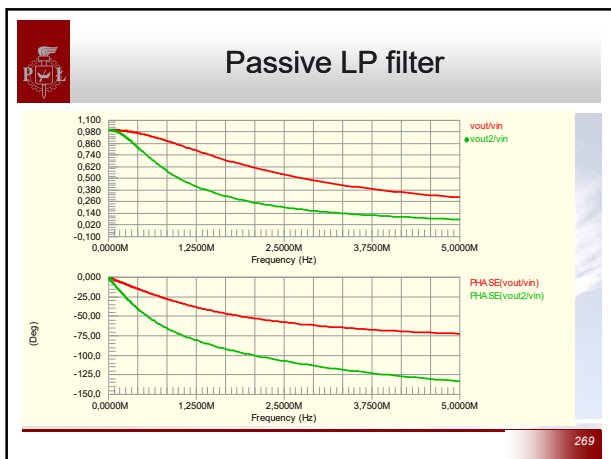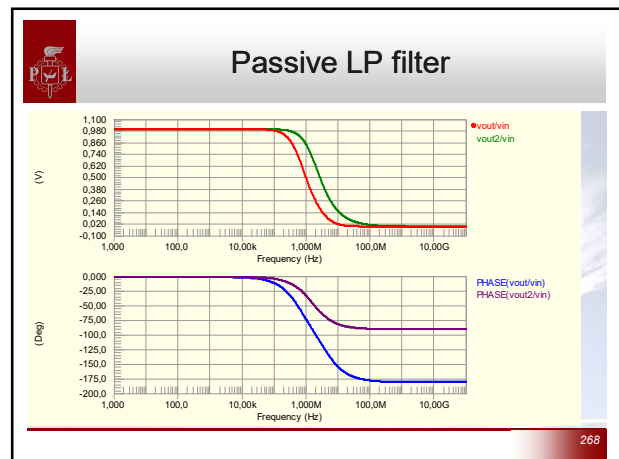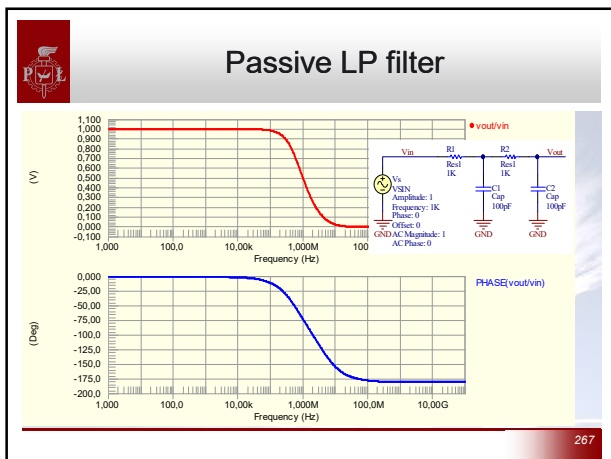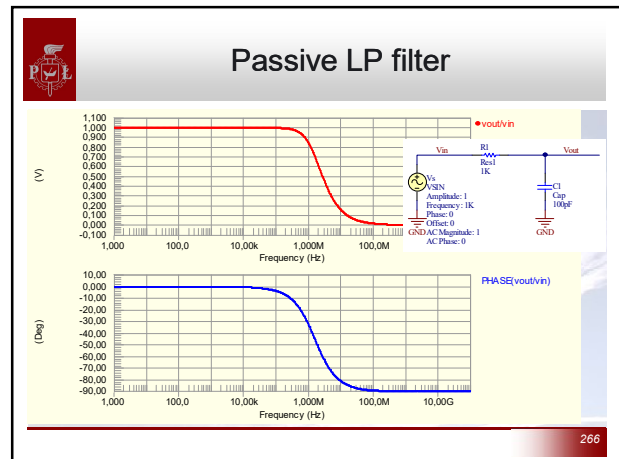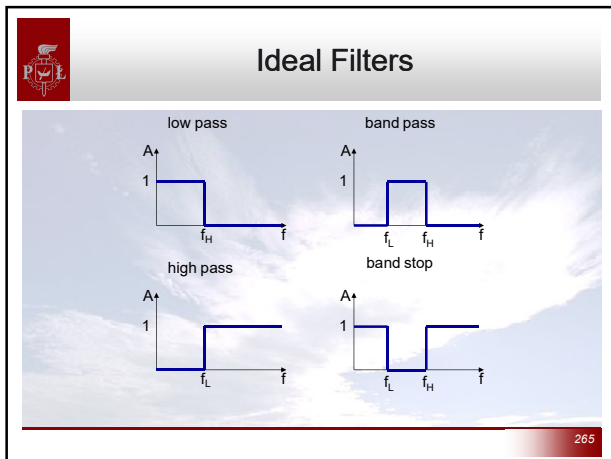




LP filter applications

- Separation of audio bands for bass, mid-range and tweeter loudspeaker
- Radio transmitters – blocking of harmonics emissions
- Telephonic filters for DSL
- Antialiasing filters for A/D converters
- Smoothing filters on outputs of D/A converters

271



Active LP filter

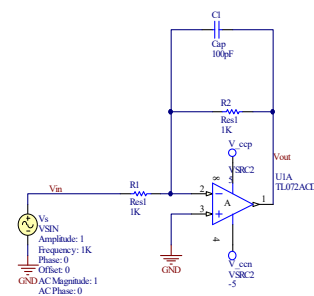

$$f_c = \frac{1}{2\pi\tau} = \frac{1}{2\pi R_2 C_1}$$


$$\omega_c = \frac{1}{\tau} = \frac{1}{R_2 C_1}$$

$$A_v = -\frac{R_2}{R_1}$$

272




Aktywny filtr LP

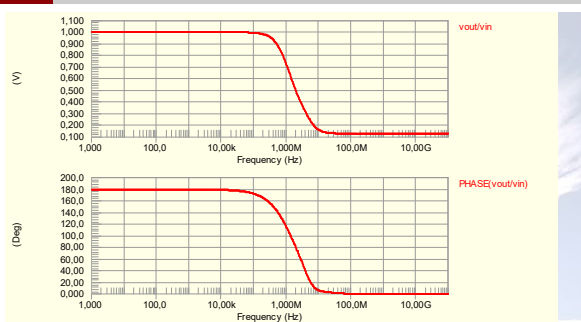

273



HP filter

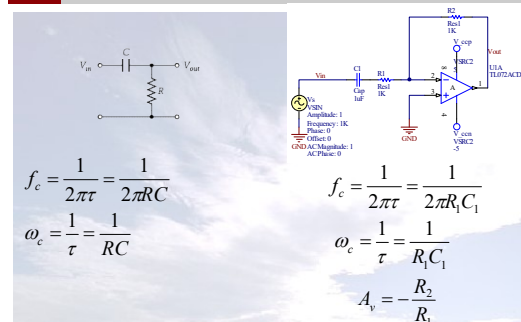

$$f_c = \frac{1}{2\pi\tau} = \frac{1}{2\pi RC}$$

$$\omega_c = \frac{1}{\tau} = \frac{1}{RC}$$

$$f_c = \frac{1}{2\pi\tau} = \frac{1}{2\pi R_1 C_1}$$


$$\omega_c = \frac{1}{\tau} = \frac{1}{R_1 C_1}$$

$$A_v = -\frac{R_2}{R_1}$$

274



HP filter?

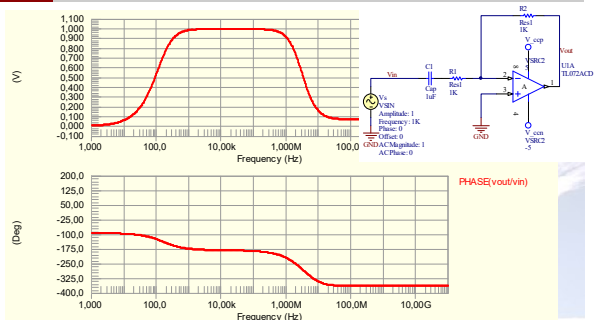

275



Other filters types

- Band pass
- Band stop
- Notch filter
- Comb filter
- all pass filter

276



Filter parameters

- Cutoff frequency usually given for specific attenuation e.g. 3dB.
- Roll-off
- Transition band,
- Ripple
- The order of a filter

277



Higher order active filters

Classification based on frequency response:


- Butterworth filter
- Chebyshev filter type I
- Chebyshev filter type II
- Bessel filter
- Elliptic filter
- Optimum "L" filter
- Gaussian filter
- Hourglass filter
- Raised-cosine filter

278



Butterworth filter

maximally flat magnitude filter

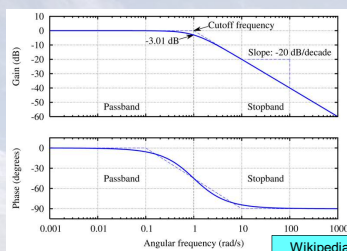


Wikipedia
by Omegatron

279



Filtr Butterworta (Butterworth filter)

$$G^2(\omega) = |H(j\omega)|^2 = \frac{G_0^2}{1 + \left(\frac{\omega}{\omega_c}\right)^{2n}}$$

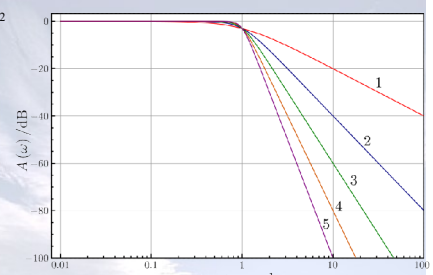

Wikipedia
by Inductiveload

280



Butterworth filter


$$C_2 = 1F$$

$$R_4 = 1\Omega$$

$$L_1 = \frac{3}{2}H$$

$$L_3 = \frac{1}{2}H$$

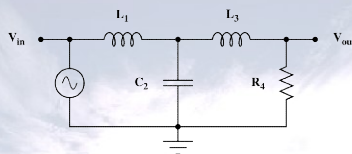
$$H(s) = \frac{V_o}{V_i} = \frac{1}{1 + 2s + 2s^2 + s^3}$$



281












Butterworth filter

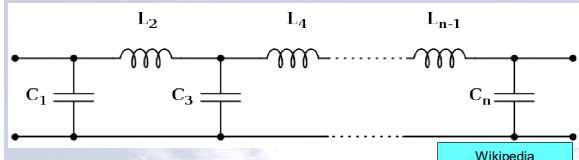

Wikipedia
by Alessio Damato

282

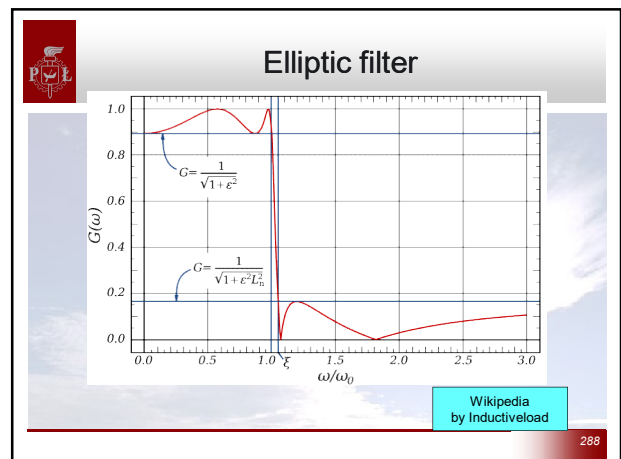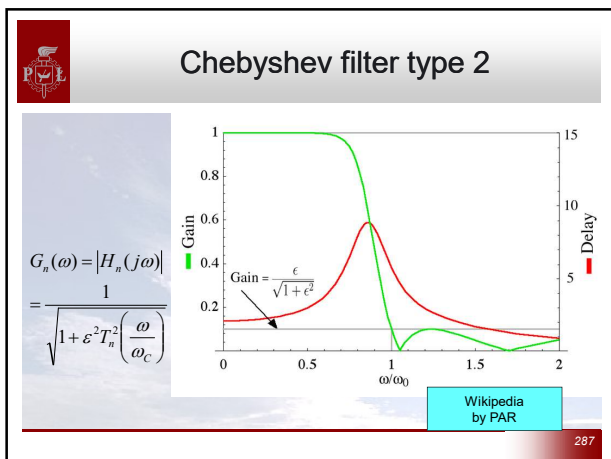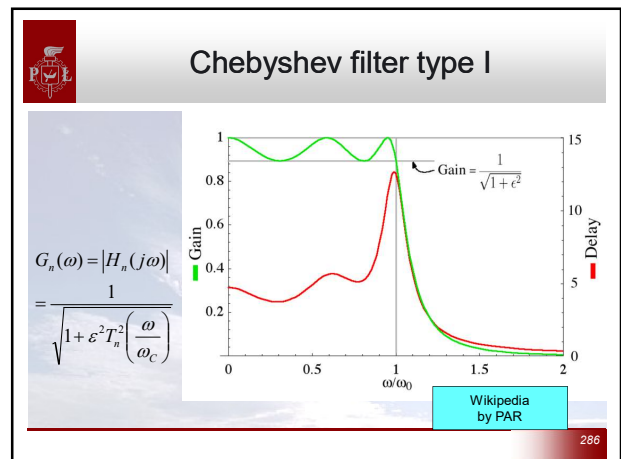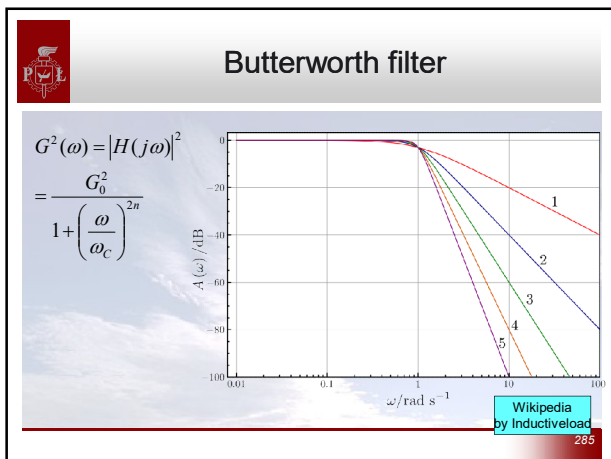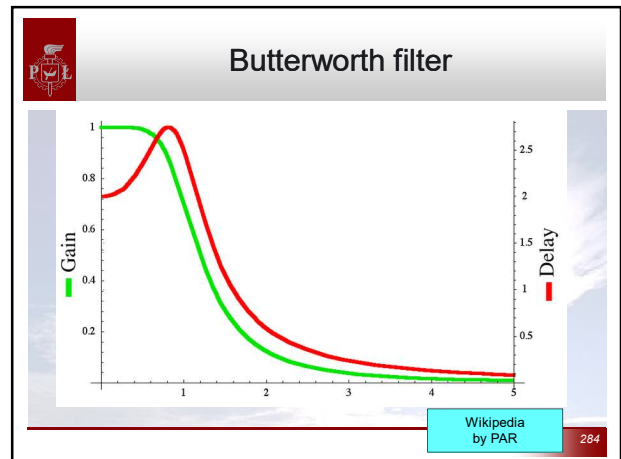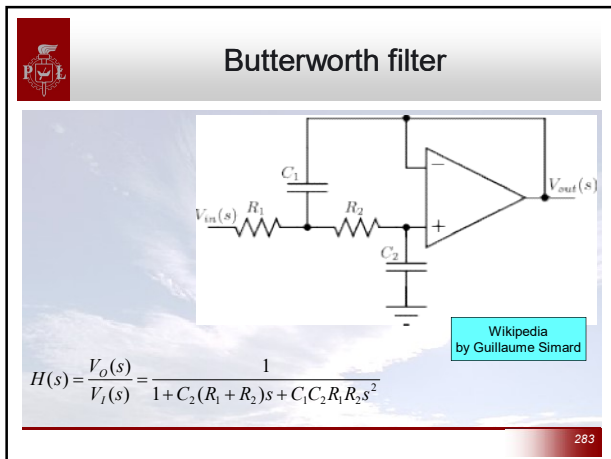

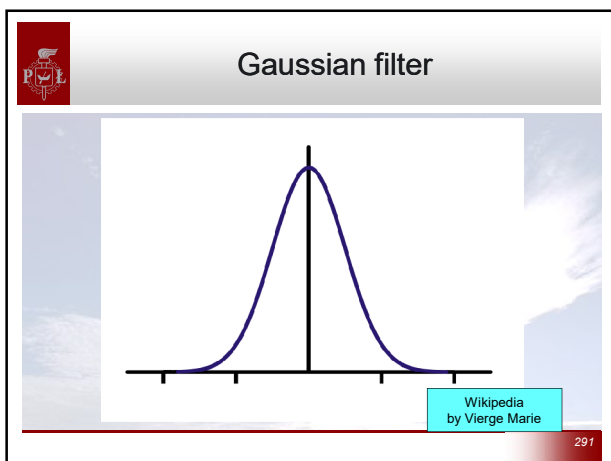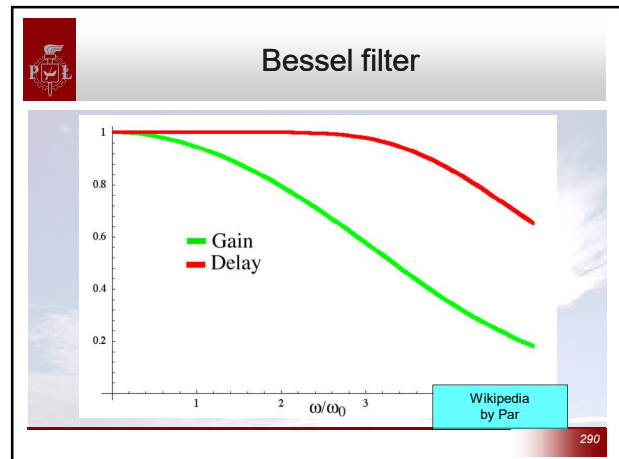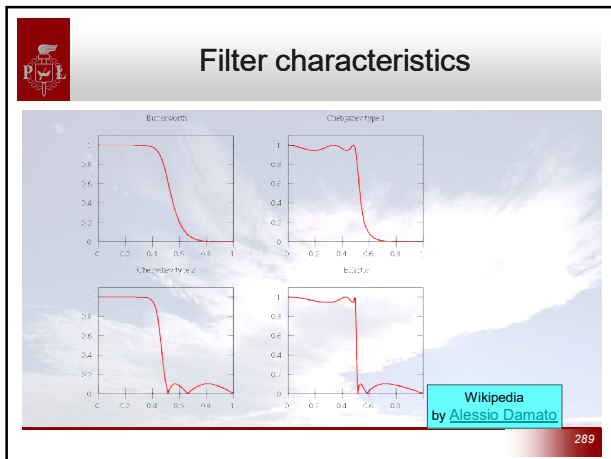

- ### Active filters of high orders
- Classification
- Butterworth filter – no gain ripple in pass band and stop band, slow cutoff
 - Chebyshev filter (Type I) – no gain ripple in stop band, moderate cutoff
 - Chebyshev filter (Type II) – no gain ripple in pass band, moderate cutoff
 - Elliptic filter – gain ripple in pass and stop band, fast cutoff
 - Bessel filter – no group delay ripple, no gain ripple in both bands, slow gain cutoff
 - Optimum "L" filter
 - Gaussian filter – no ripple in response to step function
 - Hourglass filter
 - Raised-cosine filter
- 292

- ### Discrete time filters
- Switched capacitor
 - DSP (Digital Signal Processor)
- 293

Switched capacitor

A switched capacitor is an electronic circuit element used for discrete time signal processing. It works by moving charges into and out of capacitors when switches are opened and closed. Usually, non-overlapping signals are used to control the switches, so that not all switches are closed simultaneously. Filters implemented with these elements are termed 'switched-capacitor filters'.

Unlike analog filters, which must be constructed with resistors, capacitors (and sometimes inductors) whose values are accurately known, switched capacitor filters depend only on the ratios between capacitances. This makes them much more suitable for use within integrated circuits, where accurately specified resistors and capacitors are not economical to construct.

294



Switched capacitor as a resistor

$$q = CV$$

$$q_{In} = C_S V_{In}$$

$$q_{Out} = C_S V_{Out}$$


$$q = q_{Out} - q_{In} = C_S (V_{Out} - V_{In})$$

$$I = qf$$

$$I = C_S (V_{Out} - V_{In}) f$$

$$V = V_{Out} - V_{In}$$


$$R = \frac{V}{I} = \frac{1}{C_S f}$$

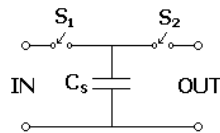

295




Switched capacitor as a resistor

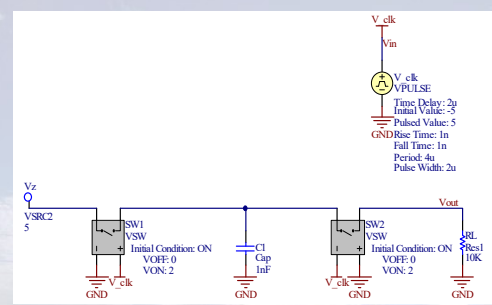

296




Switched capacitor as a resistor

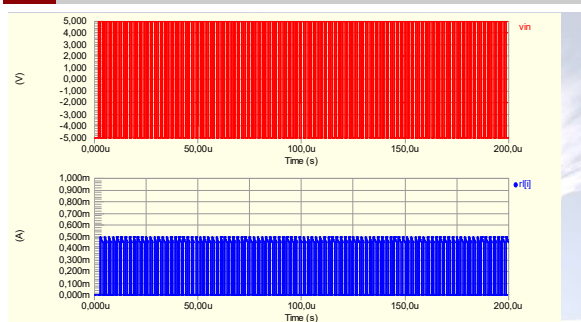

297




Switched capacitor as a resistor

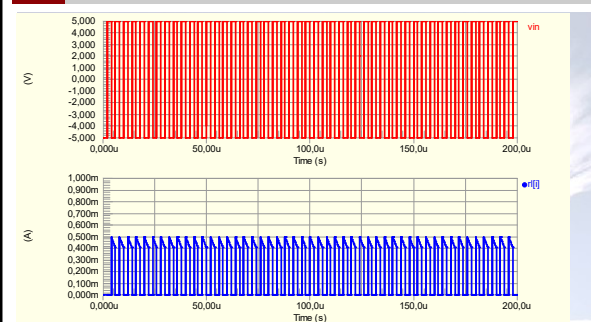

298




Switched capacitor as a resistor

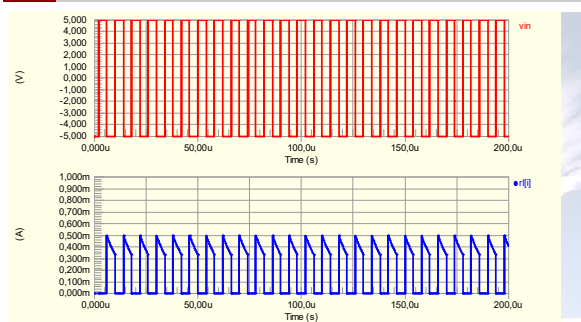

299




Switched capacitor as a resistor

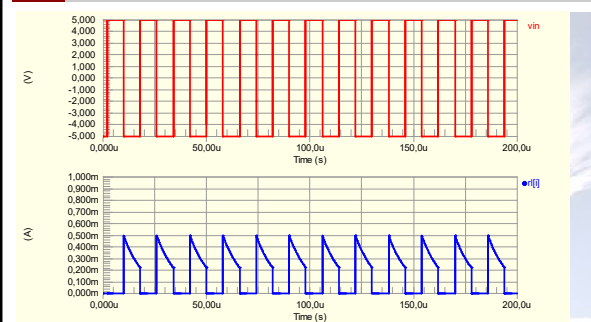

300




Switched capacitor as a resistor

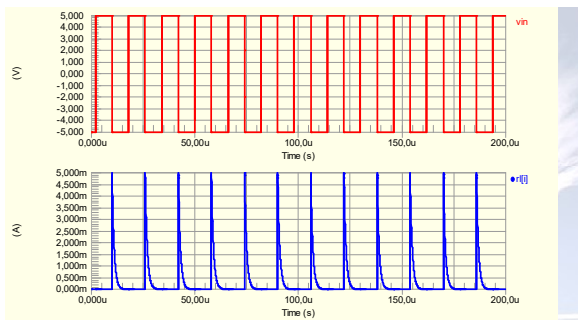

301




Switched capacitor as a resistor

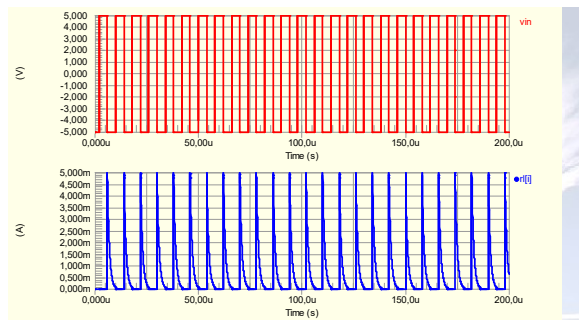

302




Switched capacitor as a resistor

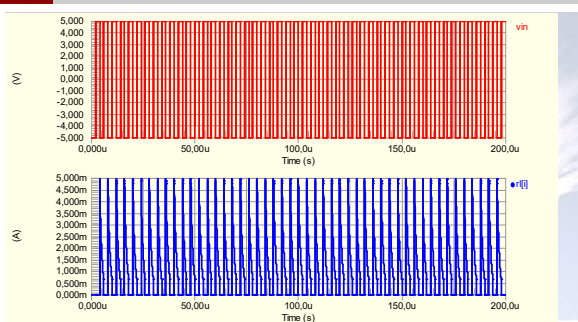

303




Switched capacitor as an integrator

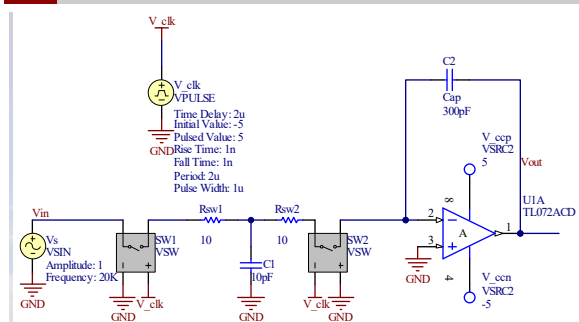

304




Switched capacitor as an integrator

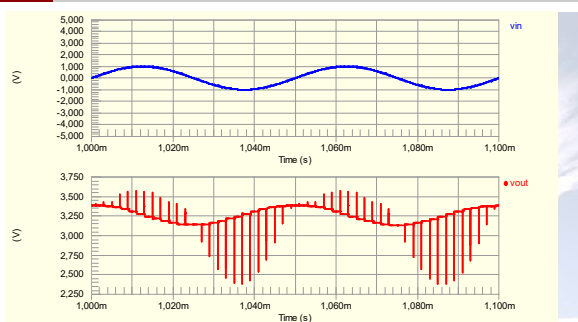

305




Switched capacitor as an integrator

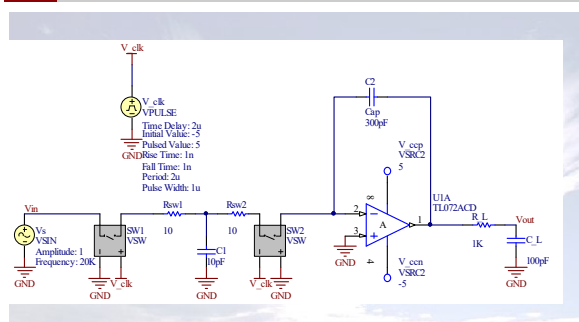

306



Switched capacitor as an integrator

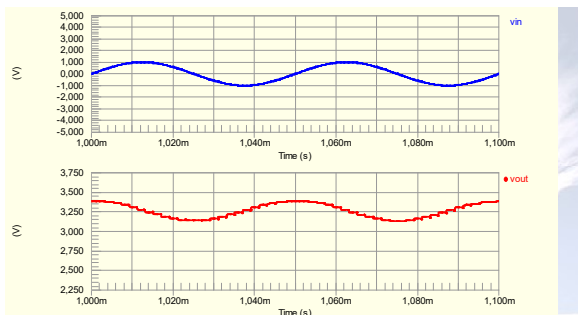

307



Analog filters IC

- LTC1062
- LTC1562
- LTC1569-7
- DF1704
- LTC1060
- MAX270
- MAX271
- MAX274
- MAX275
- MAX280
- MAX7480

308



Lecture Plan

1. Noise in active circuits
2. Power amplifiers integrated circuits.
3. Broadband and impulse amplifiers integrated circuits
4. Active analog filters with continuous and discrete time
5. **Analog multipliers**
6. Detectors of amplitude, frequency and phase
7. Phase-locked loop and its applications
8. Programmable analog circuits and their applications.
9. Application specific integrated circuits.
10. Digital integrated circuits.

309



Lecture Plan

1. Noise in active circuits
2. Power amplifiers integrated circuits.
3. Broadband and impulse amplifiers integrated circuits
4. Active analog filters with continuous and discrete time
5. Analog multipliers
6. **Detectors of amplitude, frequency and phase**
7. Phase-locked loop and its applications
8. Programmable analog circuits and their applications.
9. Application specific integrated circuits.
10. Digital integrated circuits.

310



Detectors of amplitude, frequency and phase

Literature:

U. Tietze, Ch. Shenck, Electronics circuits, design and applications, Springer-Verlag, 2001







311



Detectors of amplitude, frequency and phase.

- Modulation
- Radio receiver
- Amplitude detectors
- Frequency detectors
- Phase detectors
- IC implementations

312

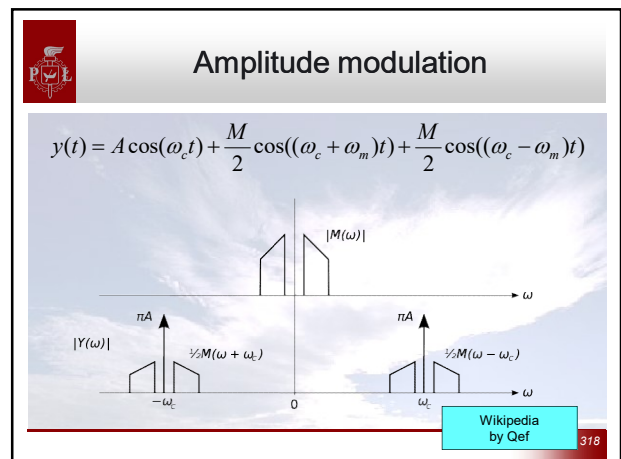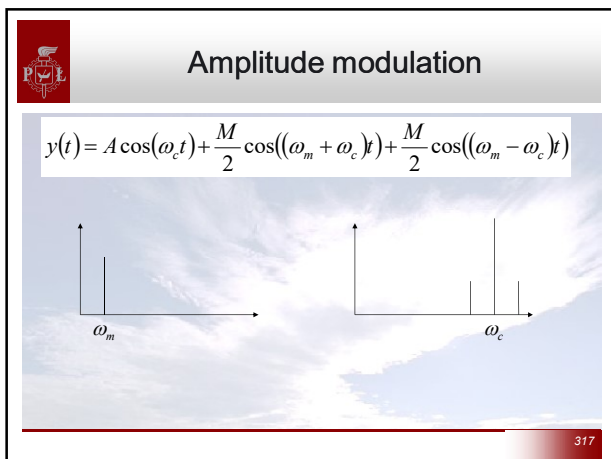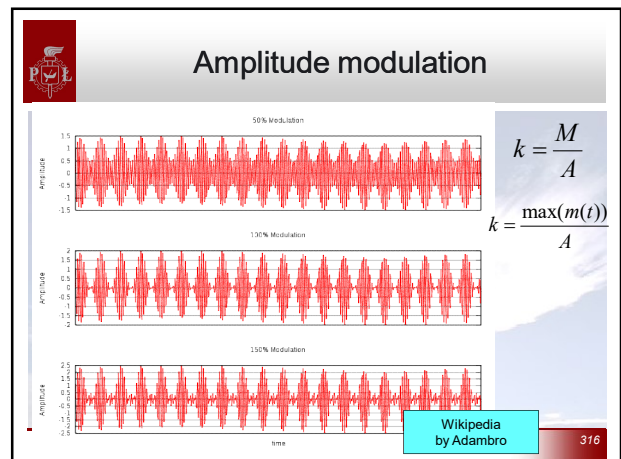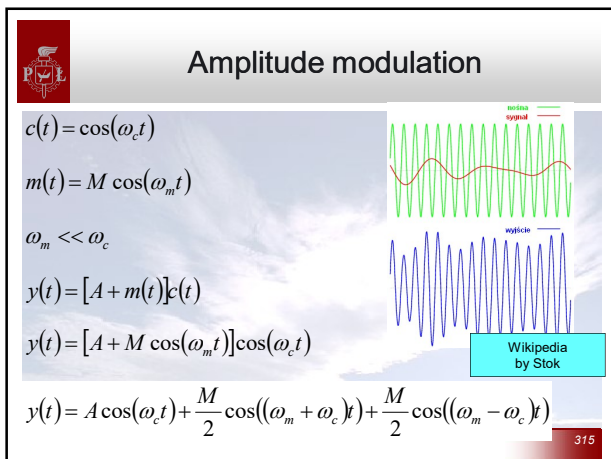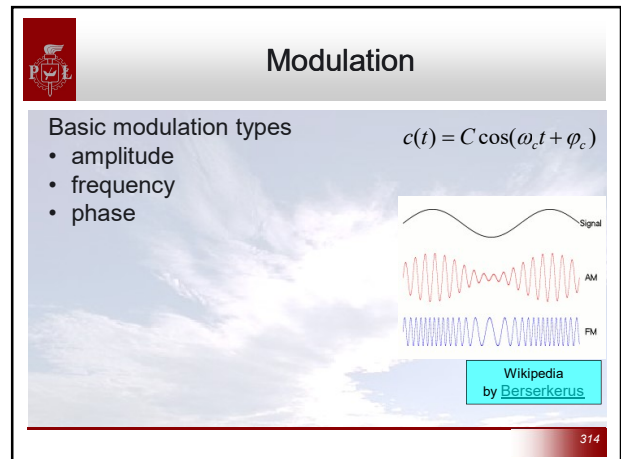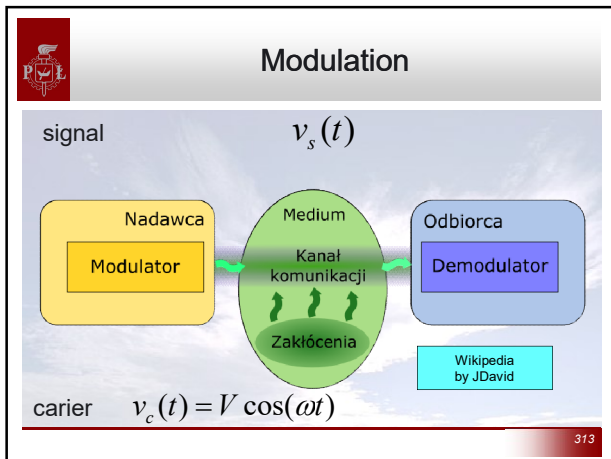



Amplitude modulation

$$y(t) = A \cos(\omega_c t) + \frac{M}{2} \cos((\omega_c + \omega_m)t) + \frac{M}{2} \cos((\omega_c - \omega_m)t)$$

Amplitude modulation


- DSB-LC (AM) Double-Sideband Large Carrier
- DSB-SC Double-Sideband Suppressed Carrier
- SSB Single-Sideband Modulation
- VSB Vestigial-Sideband Modulation

319



Amplitude modulation

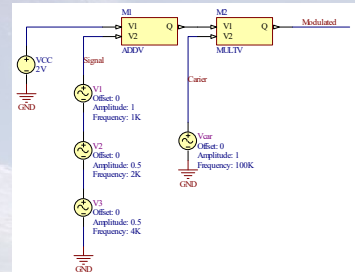
$$y(t) = [A + m(t)]c(t) = [A + M \cos(\omega_m t + \phi_m)]\cos(\omega_c t)$$



320




Amplitude modulation

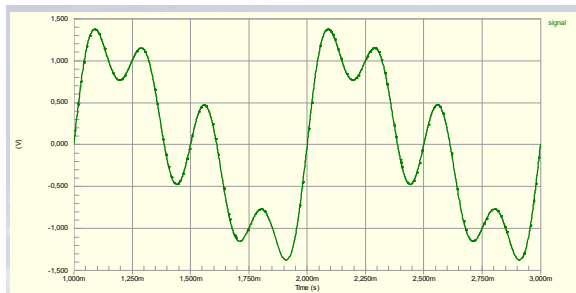

321




Amplitude modulation

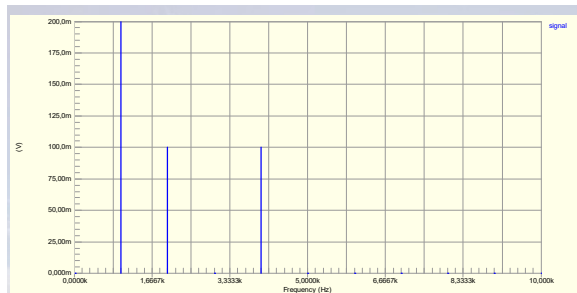

322




Amplitude modulation

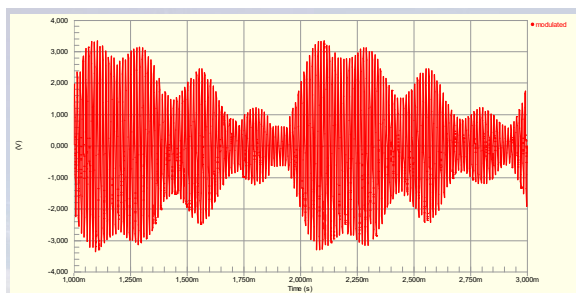







323









Amplitude modulation

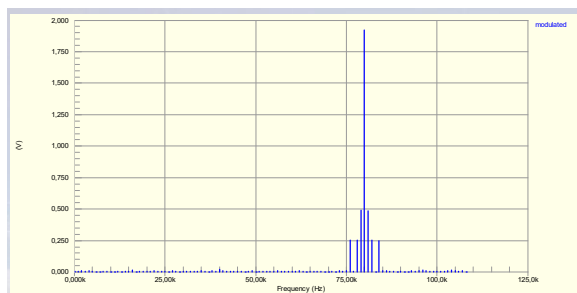


324

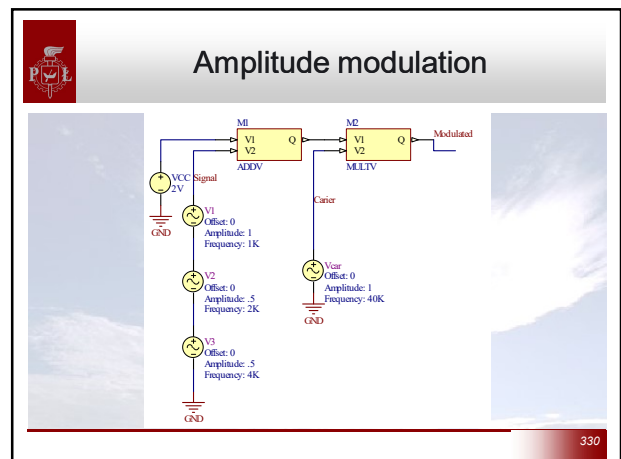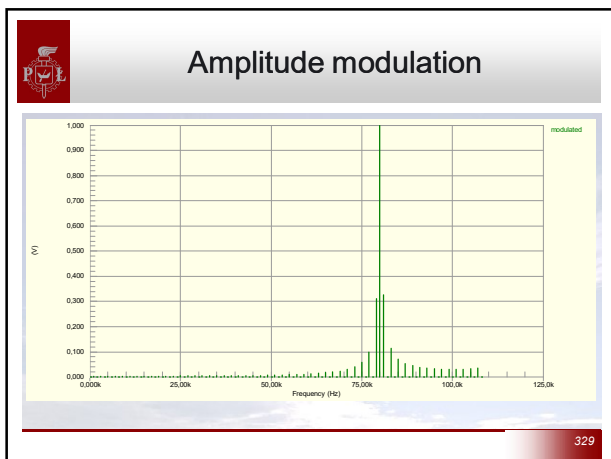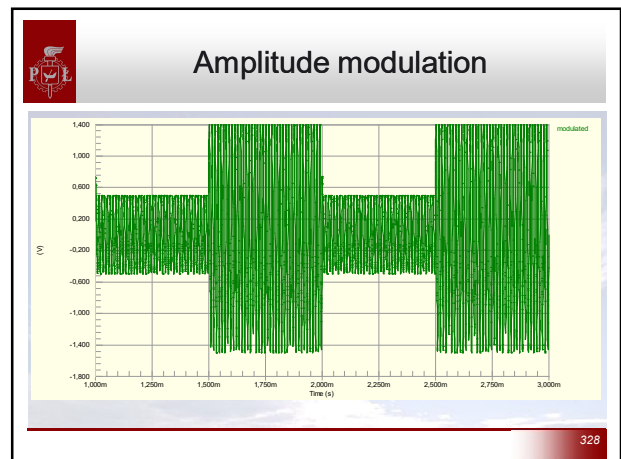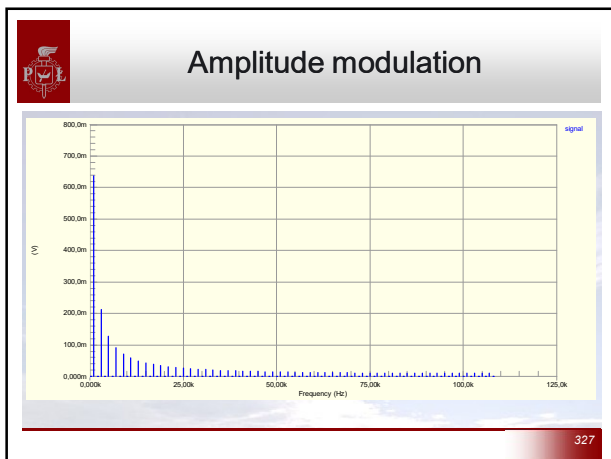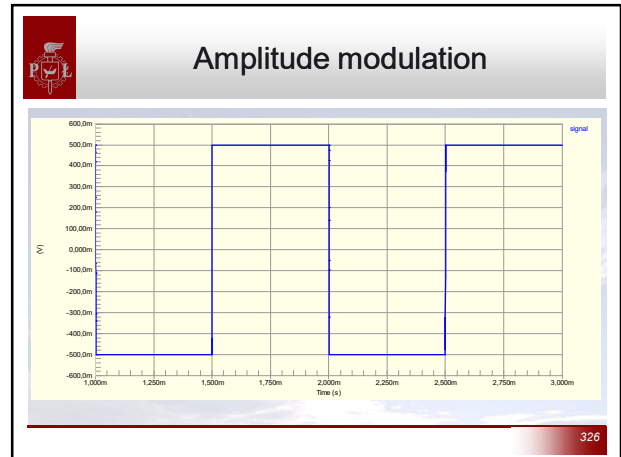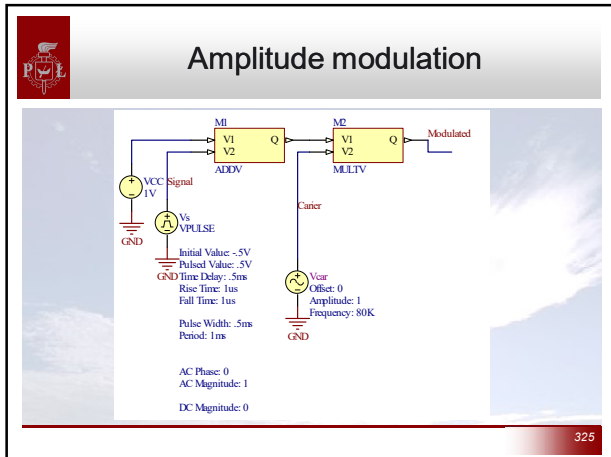

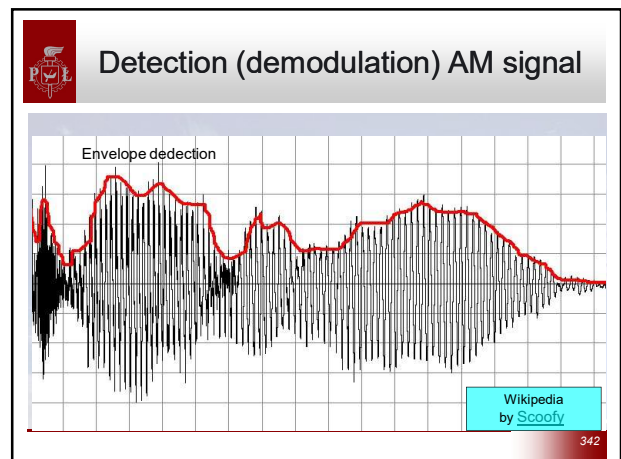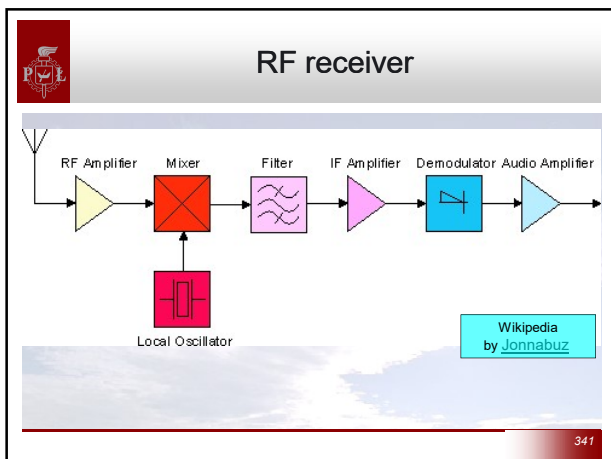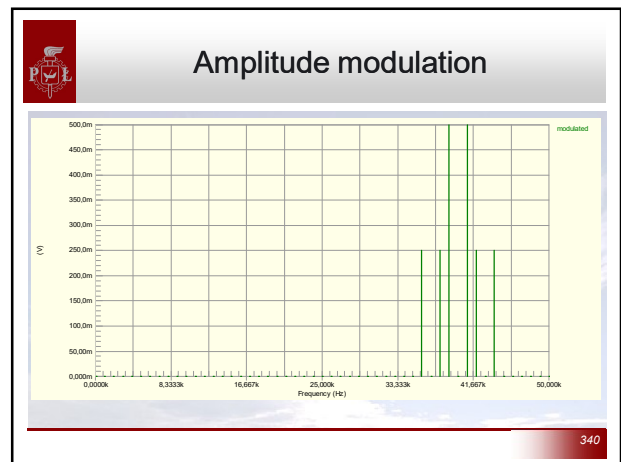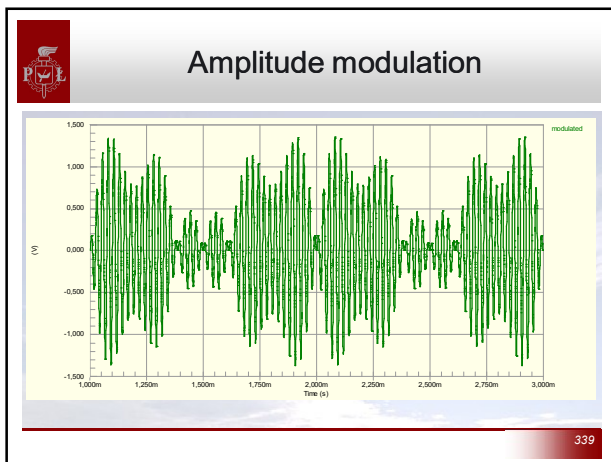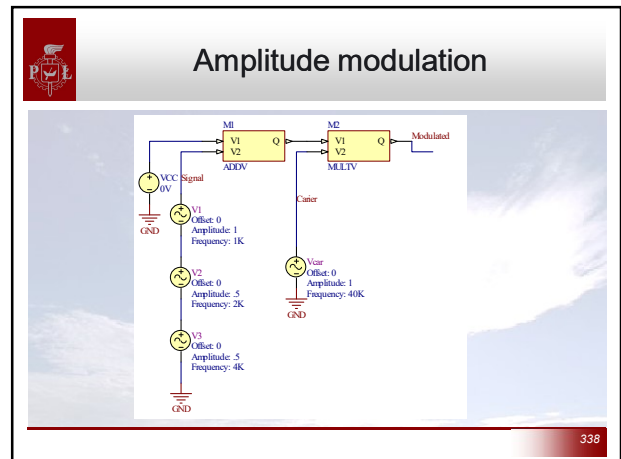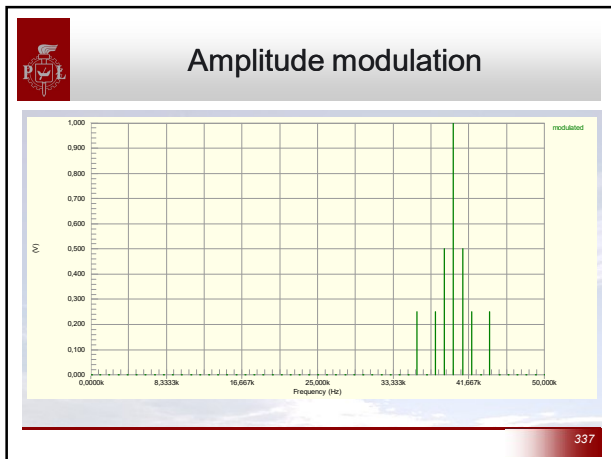




Detection (demodulation) AM signal

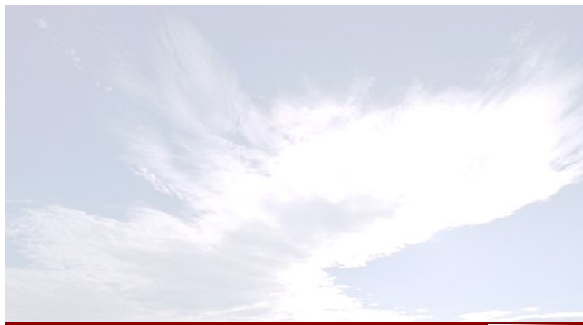

343




Detekcja (demodulacja) sygnału AM

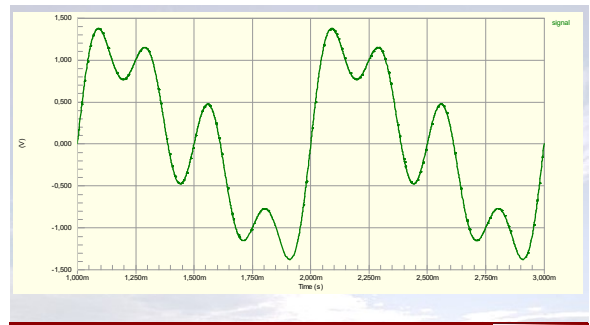

344




Detection (demodulation) AM signal

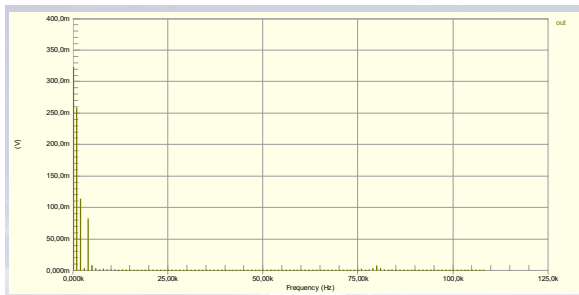

345




Detection (demodulation) AM signal

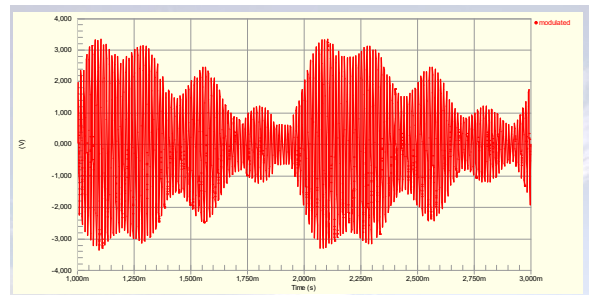

346




Detection (demodulation) AM signal

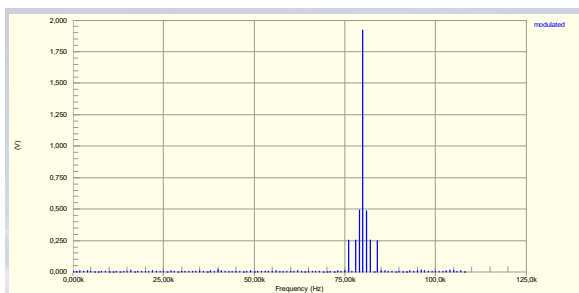







347



Detection (demodulation) AM signal

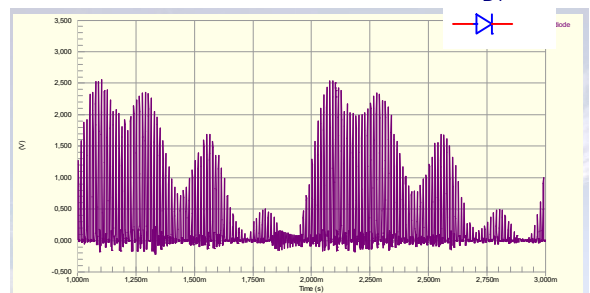


348

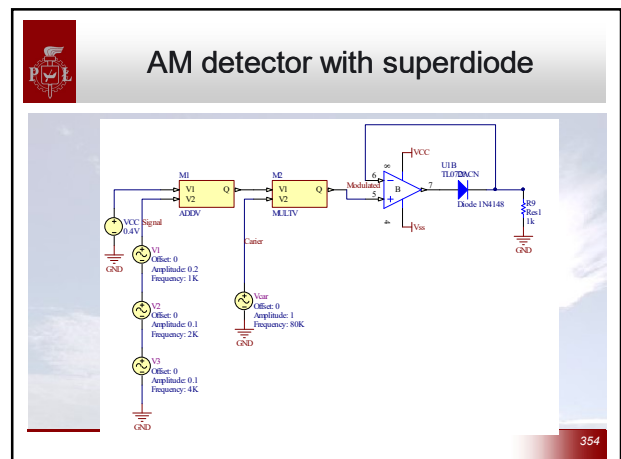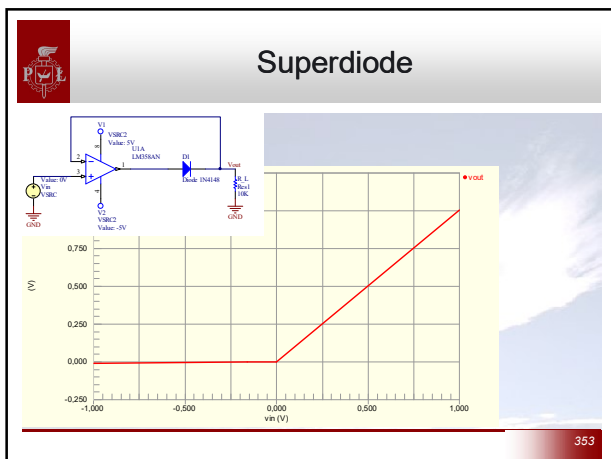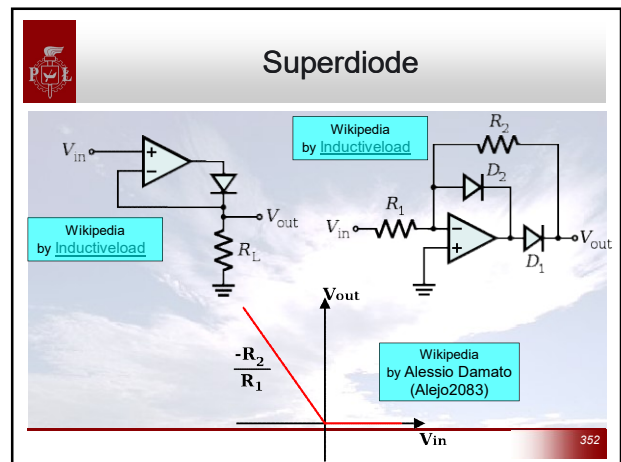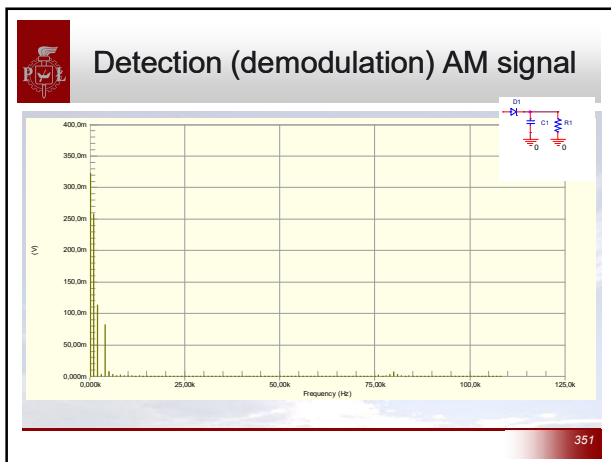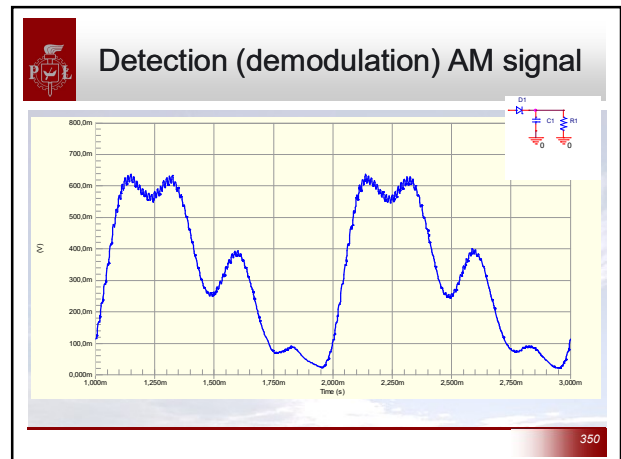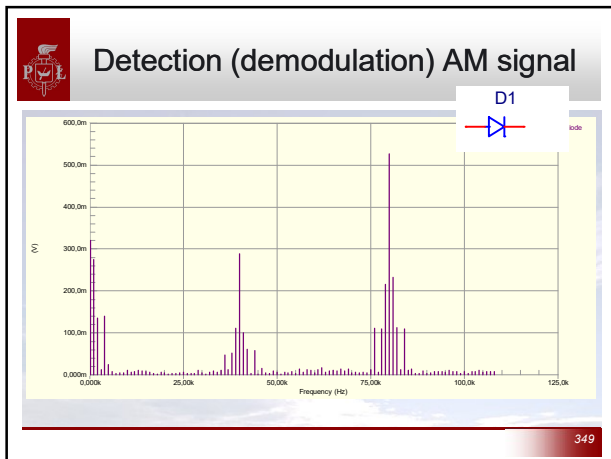




AM detector with superdiode

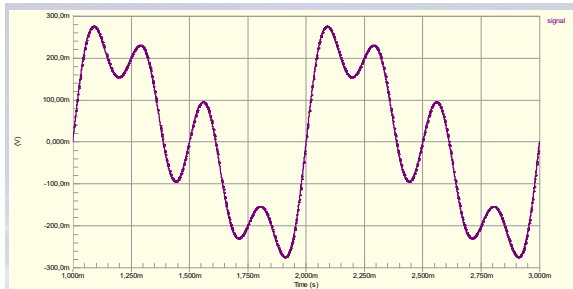

355




AM detector with superdiode

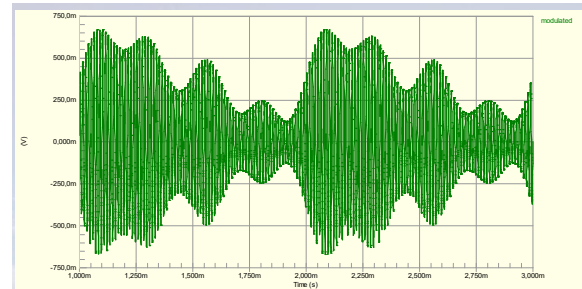

356




AM detector with superdiode

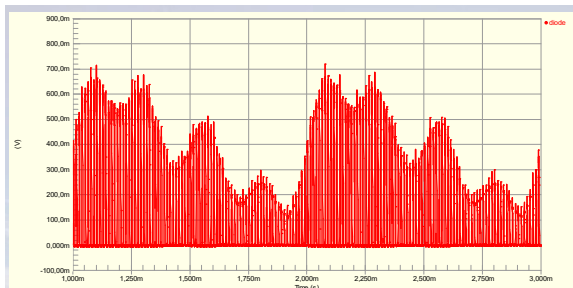

357




AM detector with superdiode

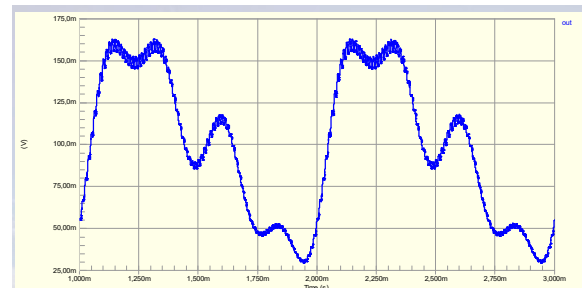

358




Transistor based demodulator

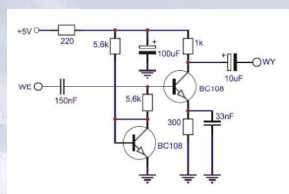

359




Detection (demodulation) AM signal

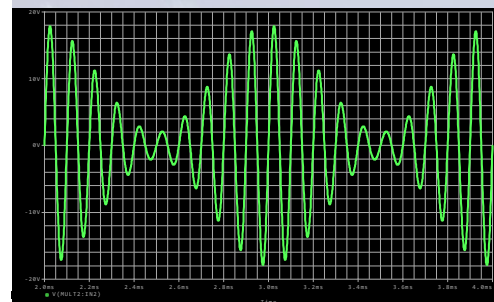

360




Detection (demodulation) AM signal

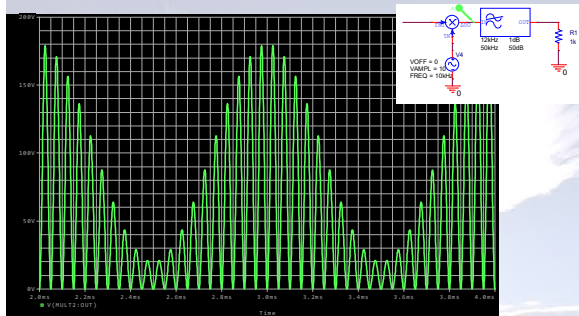

361




Detection (demodulation) AM signal

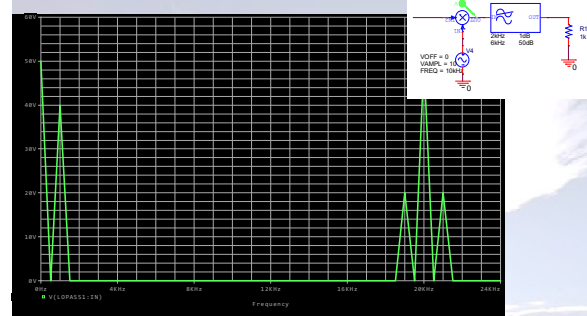

362




Detection (demodulation) AM signal

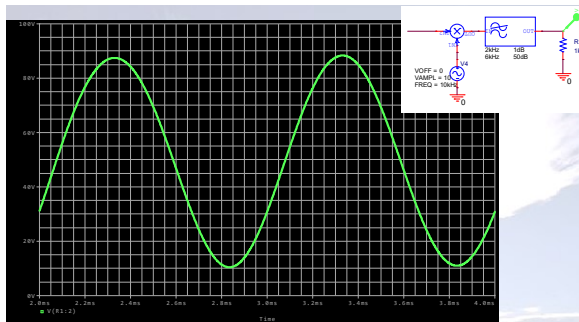

363




Detection (demodulation) AM signal

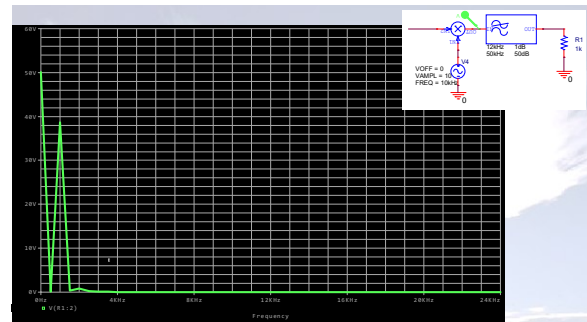

364




Detection (demodulation) AM signal

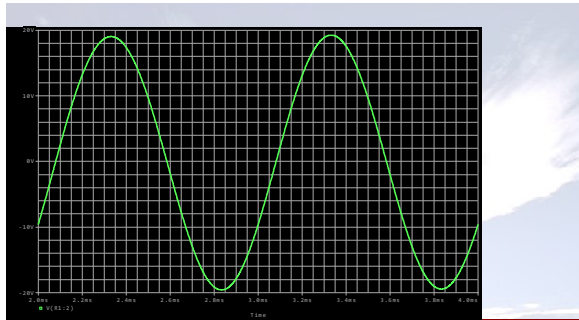







365















Detection (demodulation) AM signal






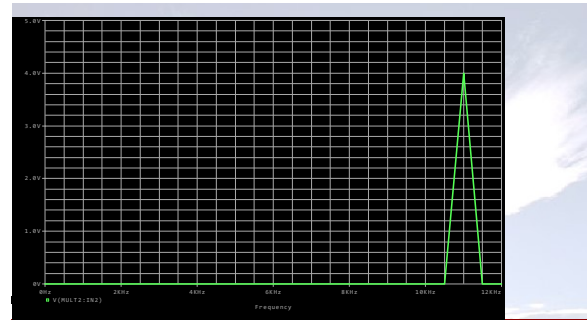


366

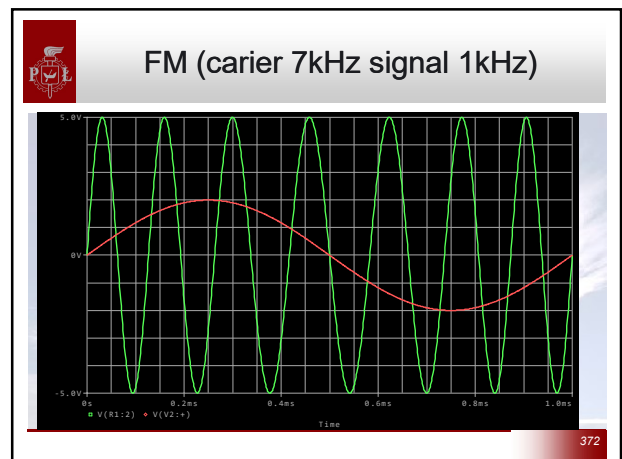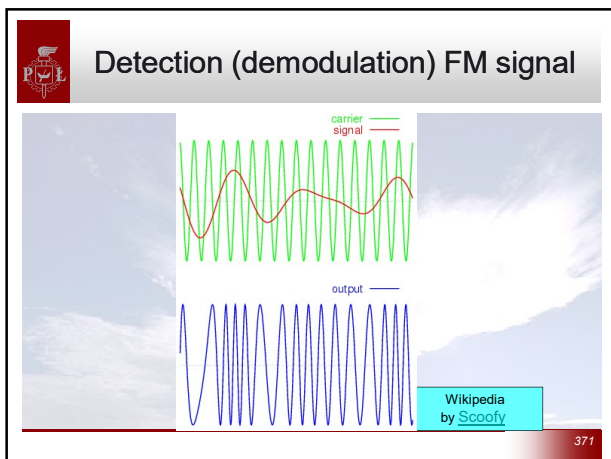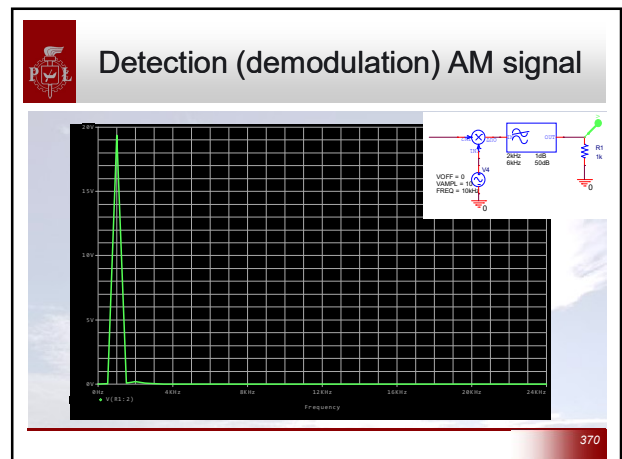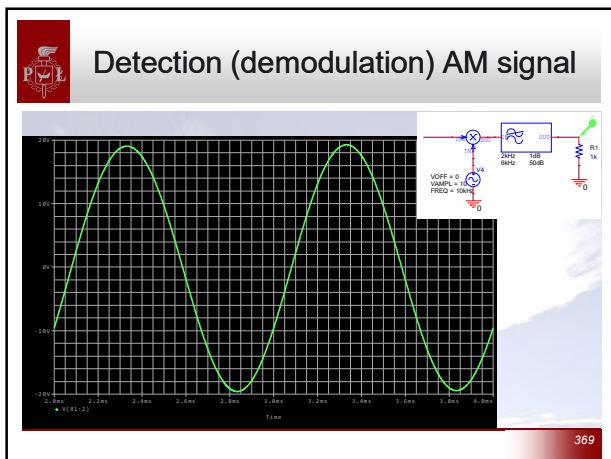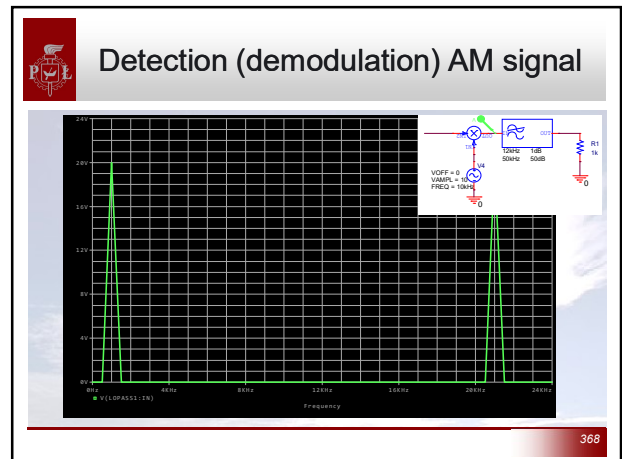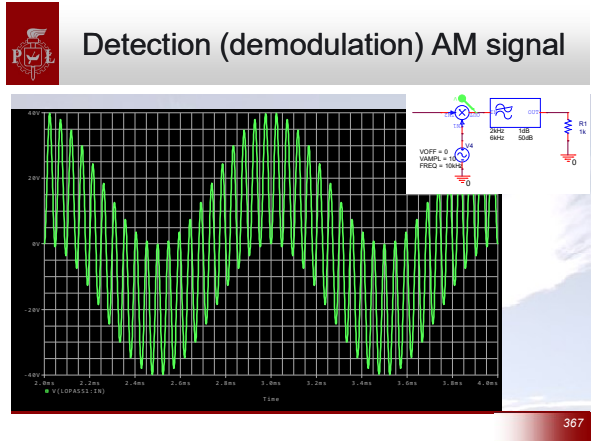

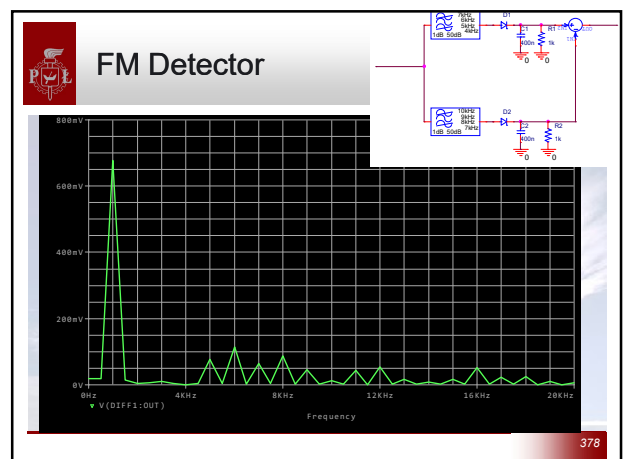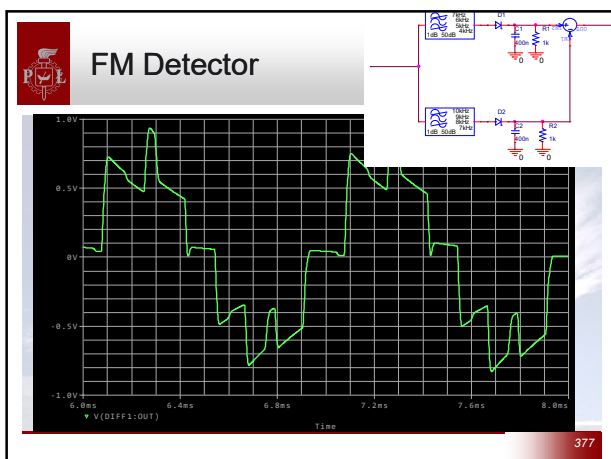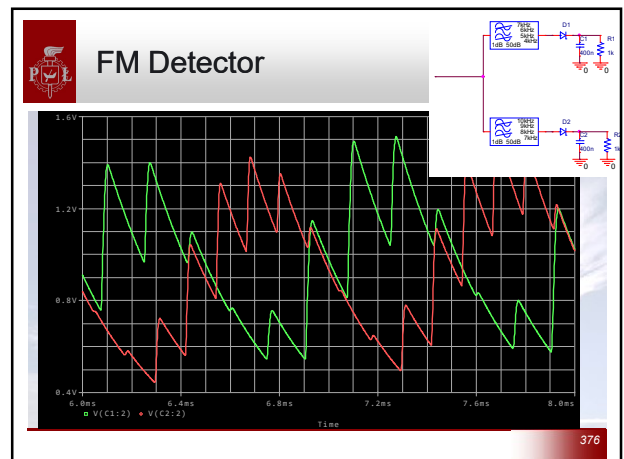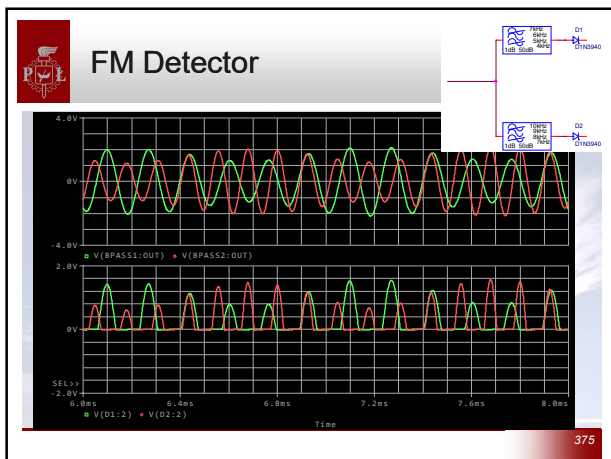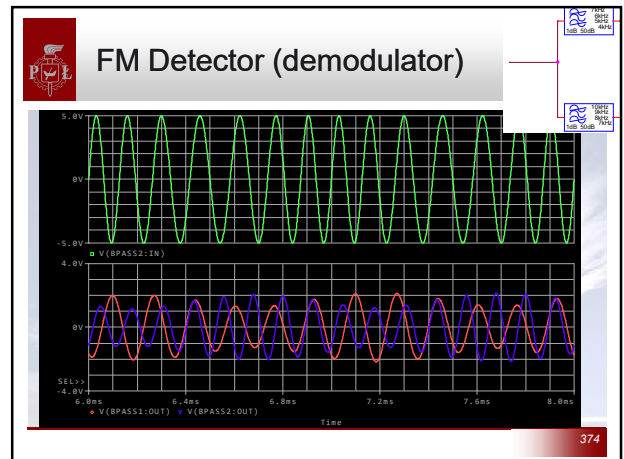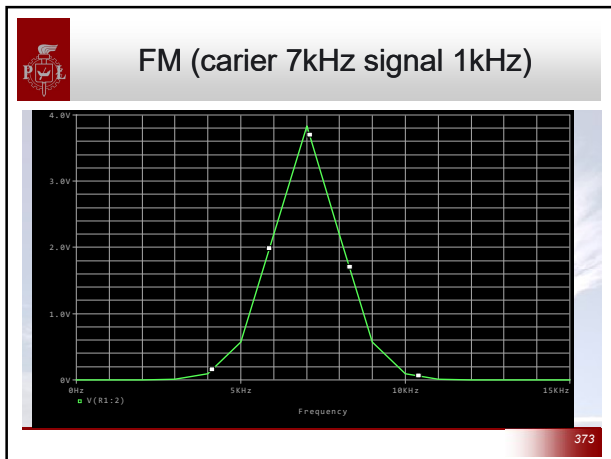

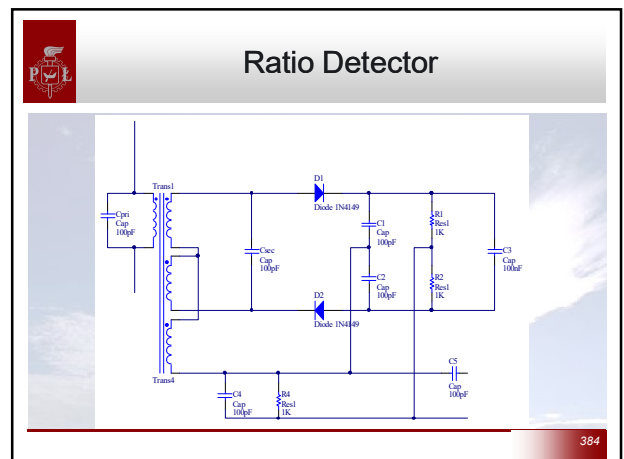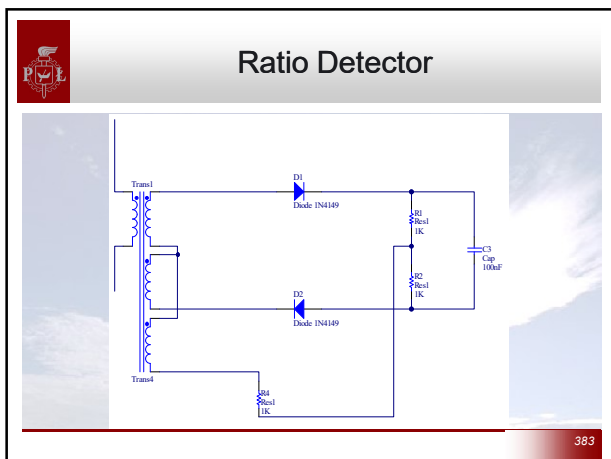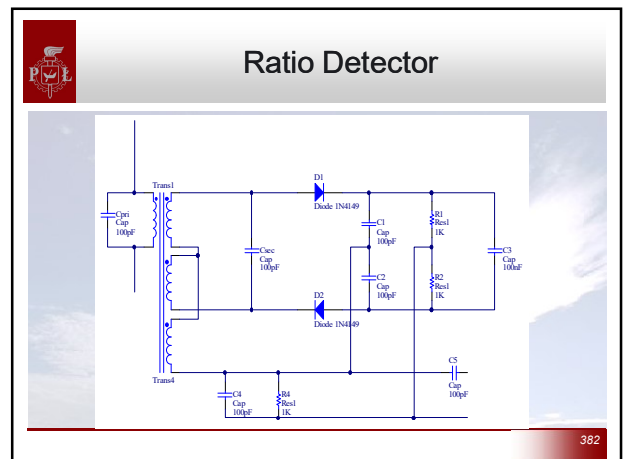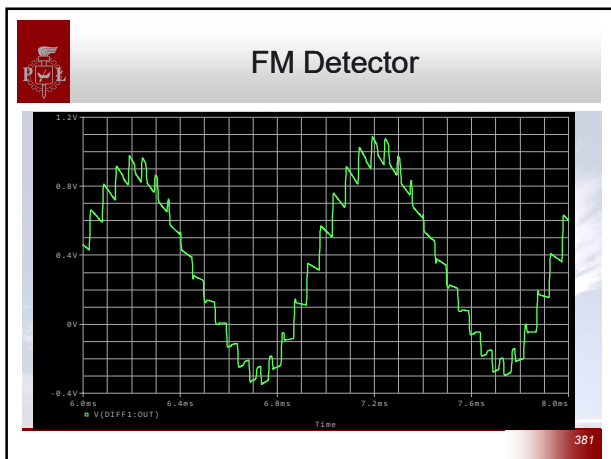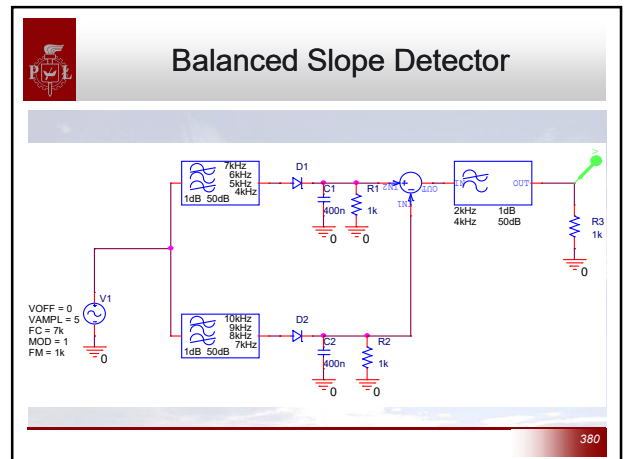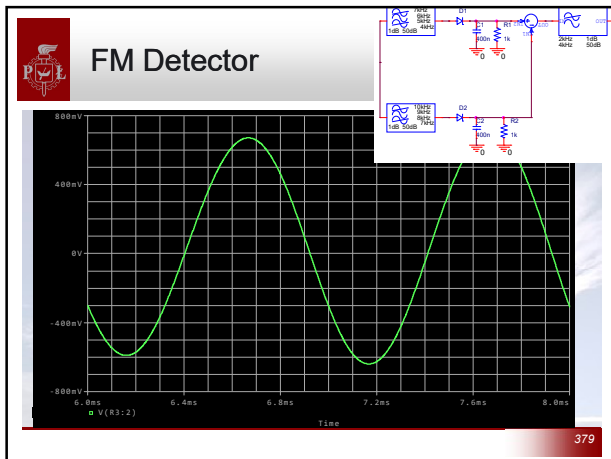

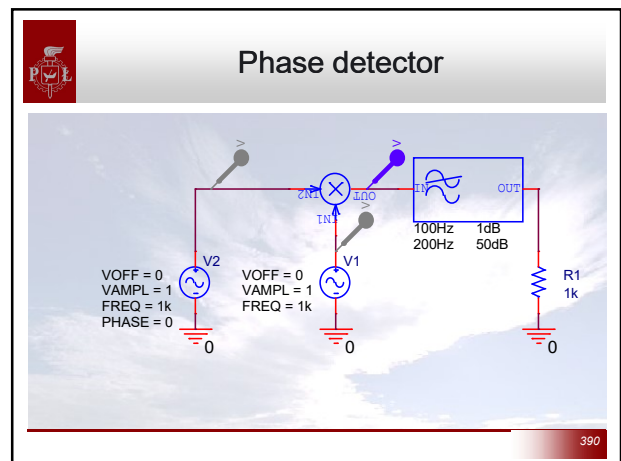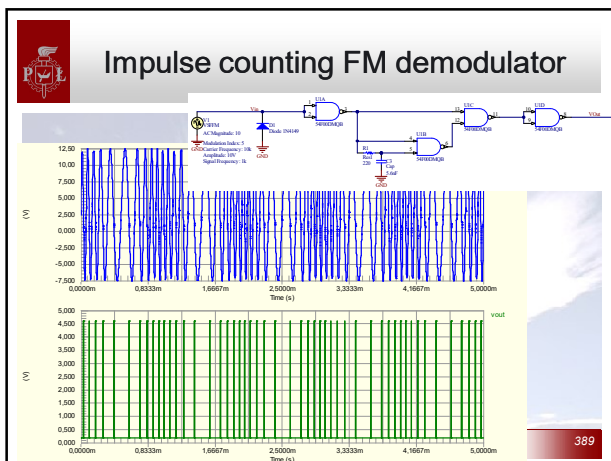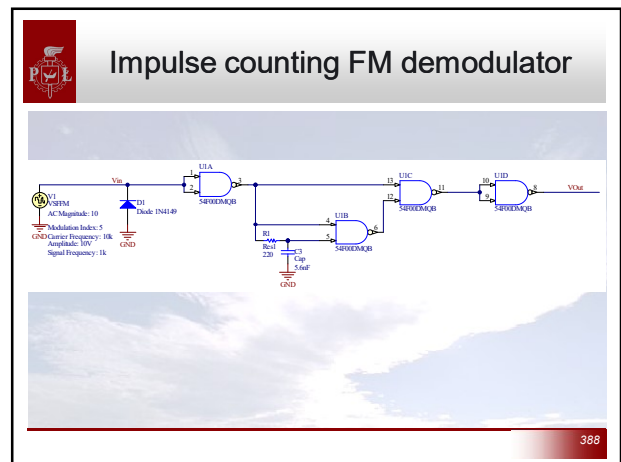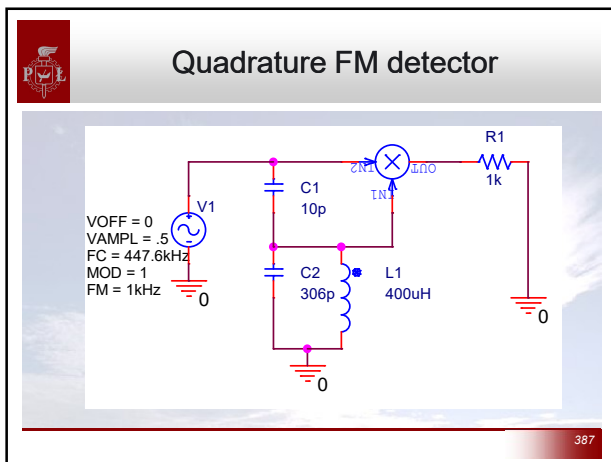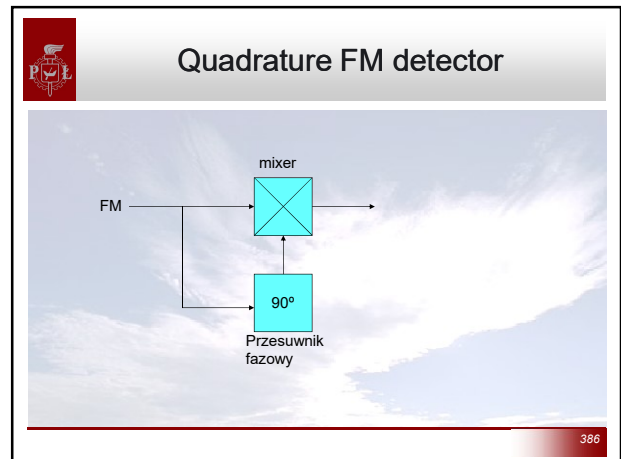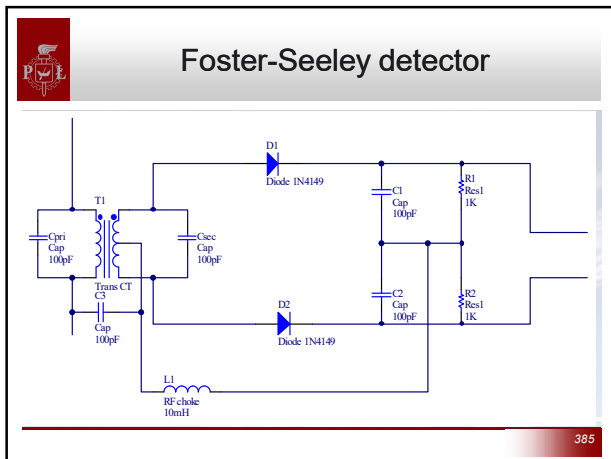



Multiplication of two sine waves

$$\begin{aligned} \sin(2\pi f_1 t + \phi_1) & \quad \sin(2\pi f_2 t + \phi_2) & \sin(\alpha)\sin(\beta) &= \frac{1}{2}\cos(\alpha - \beta) - \frac{1}{2}\cos(\alpha + \beta) \\ \sin(\omega_1 t + \phi_1) & \quad \sin(\omega_2 t + \phi_2) & \cos(\alpha) &= \sin(\alpha + 90^\circ) = \sin\left(\alpha + \frac{\pi}{2}\right) \\ & & -\sin(\alpha) &= \sin(\alpha + \pi) \end{aligned}$$


$$\begin{aligned} \sin(\omega_1 t + \phi_1)\sin(\omega_2 t + \phi_2) &= \\ &= \frac{1}{2}\cos(\omega_1 t - \omega_2 t + \phi_1 - \phi_2) - \frac{1}{2}\cos(\omega_1 t + \omega_2 t + \phi_1 + \phi_2) = \\ &= \frac{1}{2}\sin\left(\omega_1 t - \omega_2 t + \phi_1 - \phi_2 + \frac{\pi}{2}\right) - \frac{1}{2}\sin\left(\omega_1 t + \omega_2 t + \phi_1 + \phi_2 + \frac{\pi}{2}\right) = \\ &= \frac{1}{2}\sin\left(\omega_1 t - \omega_2 t + \phi_1 - \phi_2 + \frac{\pi}{2}\right) + \frac{1}{2}\sin\left(\omega_1 t + \omega_2 t + \phi_1 + \phi_2 - \frac{\pi}{2}\right) \end{aligned}$$

391



Phase detector
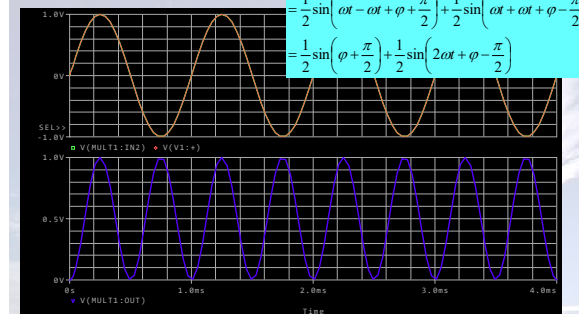
$$\begin{aligned} \sin(\omega t)\sin(\omega t + \phi) &= \\ &= \frac{1}{2}\sin\left(\omega t - \omega t + \phi + \frac{\pi}{2}\right) + \frac{1}{2}\sin\left(\omega t + \omega t + \phi - \frac{\pi}{2}\right) = \\ &= \frac{1}{2}\sin\left(\phi + \frac{\pi}{2}\right) + \frac{1}{2}\sin\left(2\omega t + \phi - \frac{\pi}{2}\right) \end{aligned}$$




392



Phase detector
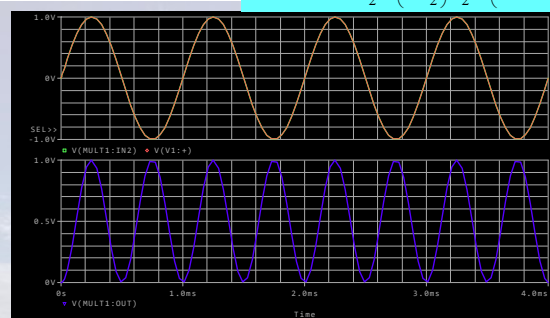
$$\sin(\omega t)\sin(\omega t + \phi) = \frac{1}{2}\sin\left(\phi + \frac{\pi}{2}\right) + \frac{1}{2}\sin\left(2\omega t + \phi - \frac{\pi}{2}\right)$$




393



Phase detector
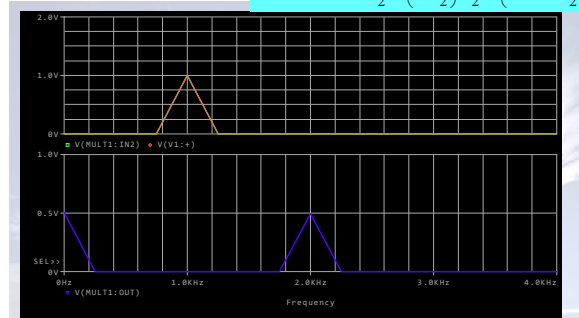
$$\sin(\omega t)\sin(\omega t + \phi) = \frac{1}{2}\sin\left(\phi + \frac{\pi}{2}\right) + \frac{1}{2}\sin\left(2\omega t + \phi - \frac{\pi}{2}\right)$$




394



Phase detector
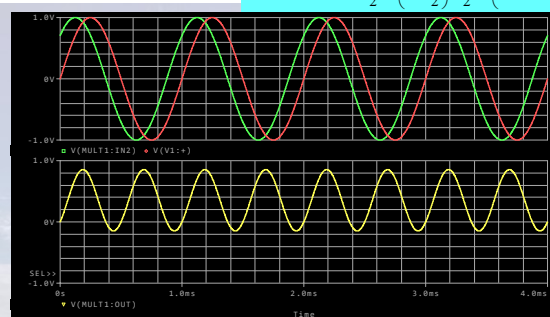
$$\sin(\omega t)\sin(\omega t + \phi) = \frac{1}{2}\sin\left(\phi + \frac{\pi}{2}\right) + \frac{1}{2}\sin\left(2\omega t + \phi - \frac{\pi}{2}\right)$$




395











Phase detector
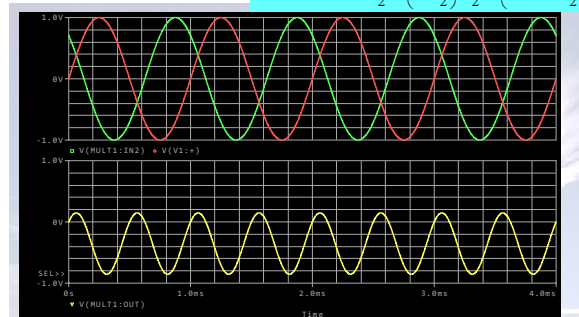
$$\sin(\omega t)\sin(\omega t + \phi) = \frac{1}{2}\sin\left(\phi + \frac{\pi}{2}\right) + \frac{1}{2}\sin\left(2\omega t + \phi - \frac{\pi}{2}\right)$$



396

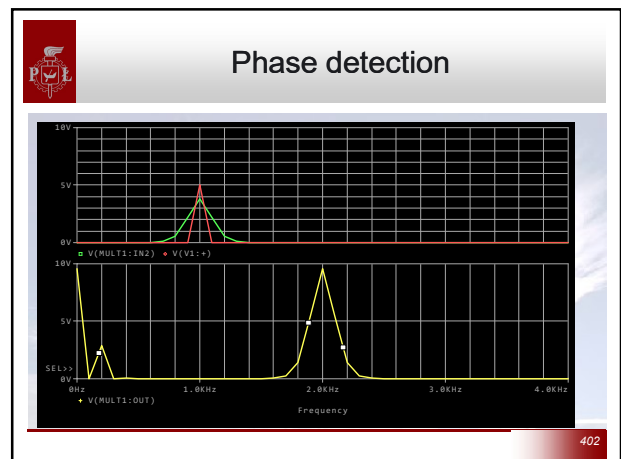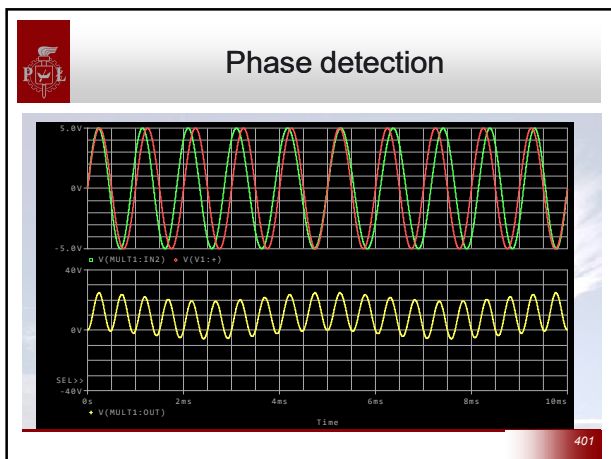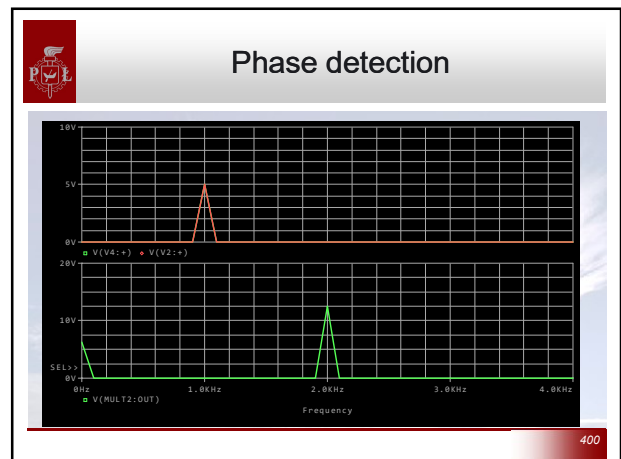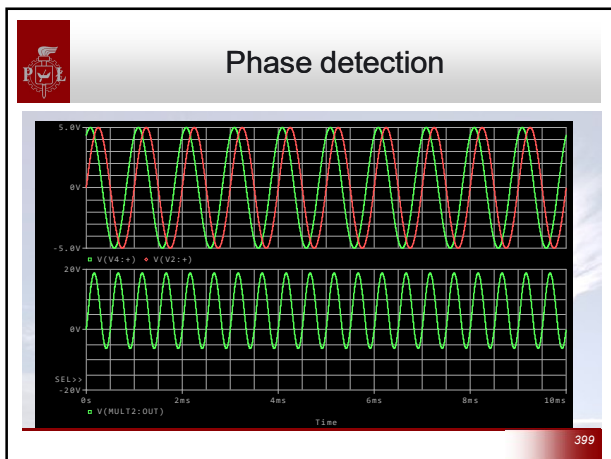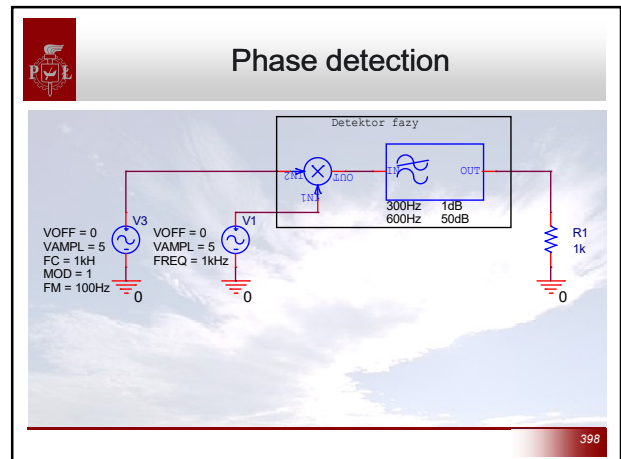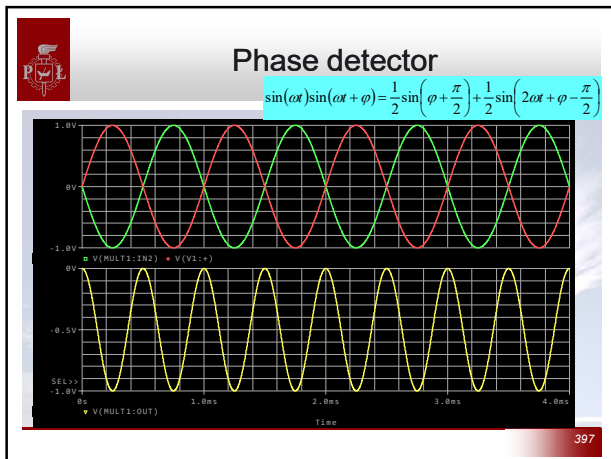

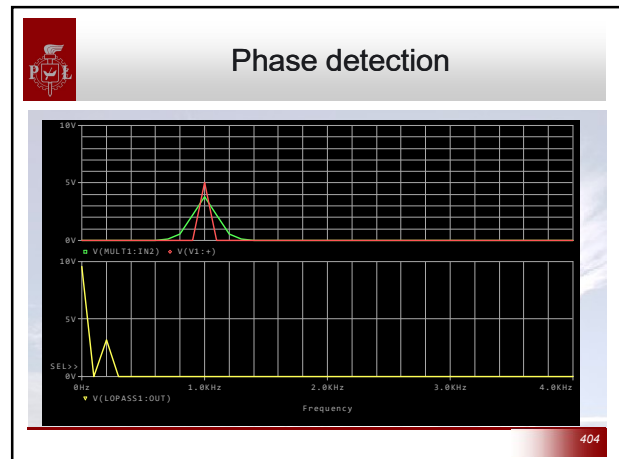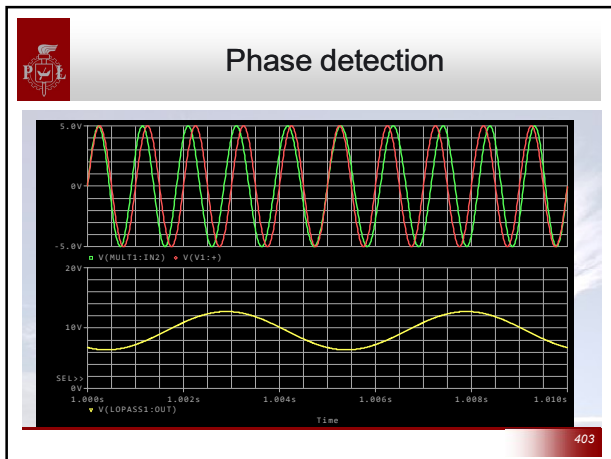

- ### Lecture Plan
1. Noise in active circuits
 2. Power amplifiers integrated circuits.
 3. Broadband and impulse amplifiers integrated circuits
 4. Active analog filters with continuous and discrete time
 5. Analog multipliers
 6. Detectors of amplitude, frequency and phase
 7. **Phase-locked loop and its applications**
 8. Programmable analog circuits and their applications.
 9. Application specific integrated circuits.
 10. Digital integrated circuits.
- 405

- ### Detectors of amplitude, frequency and phase
- Literature:
- U. Tietze, Ch. Shenck, Electronics circuits, design and applications, Springer-Verlag, 2001
- 406

Phase-locked loop (PLL)

PLL is a control system that generates a signal that has a fixed relation to the phase of a "reference" signal.

A PLL circuit responds to both the frequency and the phase of the input signals, automatically raising or lowering the frequency of a controlled oscillator until it is matched to the reference in both frequency and phase.

PLL is an example of a control system using negative feedback.

Wikipedia

407

Phase-locked loop (PLL)

Applications:

- radio, telecommunications,
- computers
- other electronic applications.

Wikipedia by Alessio Damato (Alejo2083)







Tasks:

- generation of stable frequencies,
- recovering signals from a noisy communication channel,
- distribution of clock timing pulses in digital logic designs such as microprocessors.

Since a single integrated circuit can provide a complete phase-locked-loop building block, the technique is widely used in modern electronic devices, with output frequencies from a fraction of a cycle per second up to many gigahertz.

Wikipedia

408

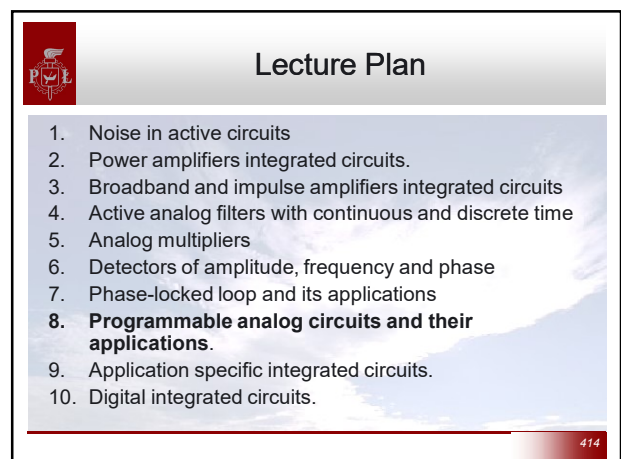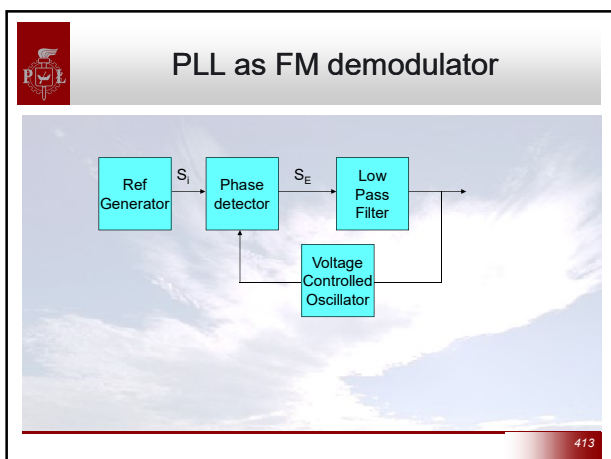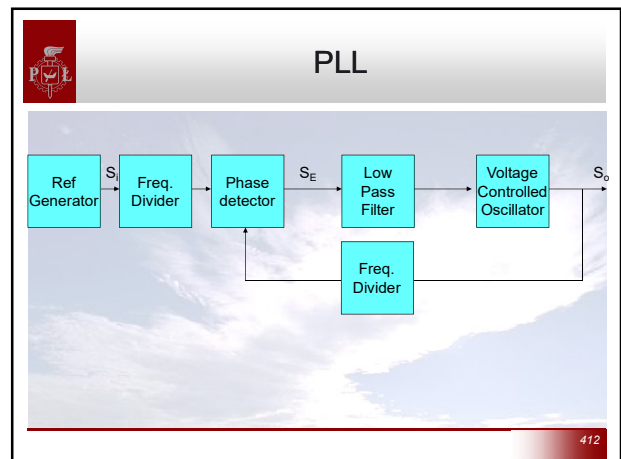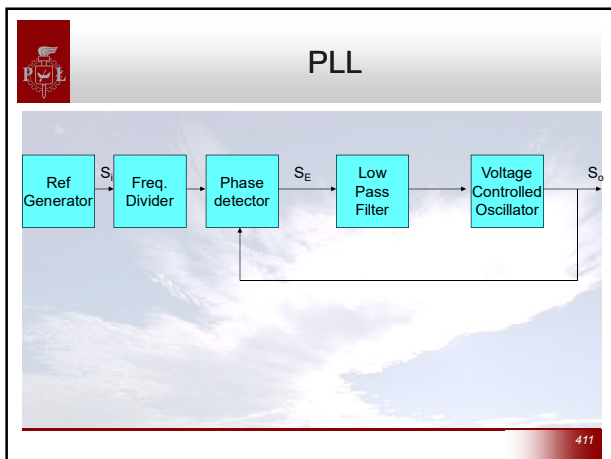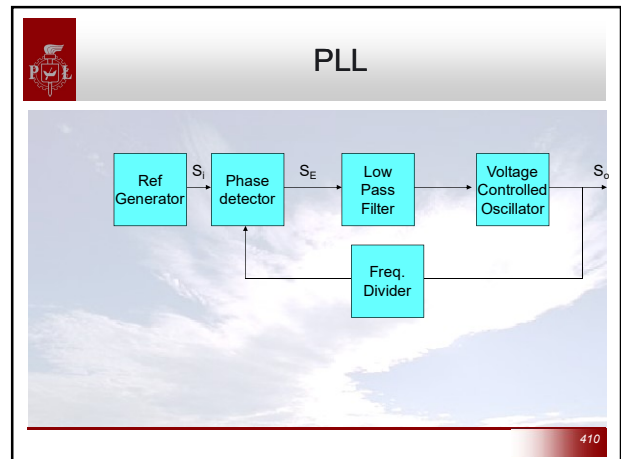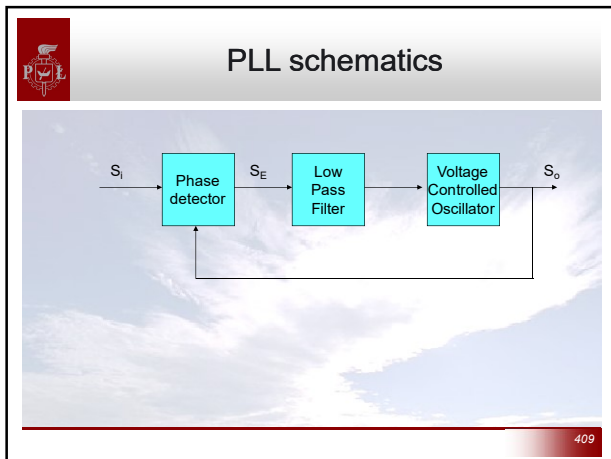



Programmable analog circuits and their applications

Literature:

U. Tietze, Ch. Shenck, Electronics circuits, design and applications, Springer-Verlag, 2001

415



Lecture Plan

1. Noise in active circuits
2. Power amplifiers integrated circuits.
3. Band pass amplifiers integrated circuits
4. Active analog filters with continuous and discrete time
5. Analog multipliers
6. Detectors of amplitude, frequency and phase
7. Phase-locked loop and its applications
8. Programmable analog circuits and their applications.
9. **Application specific integrated circuits.**
10. **Digital integrated circuits.**

416




Digital programmable ICs Application specific integrated circuits.

Literature:

417



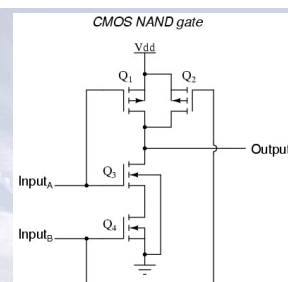
Digital programmable ICs Application specific integrated circuits.



418



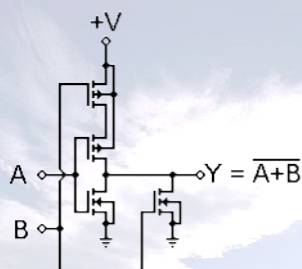
Digital programmable ICs Application specific integrated circuits.



419



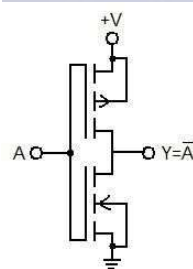Digital programmable ICs Application specific integrated circuits.



Scheme of not gate in CMOS technology with the use of two MOSFET transistors: one N-channel with its source grounded, and one P-channel with its source connected to +V.


420



Digital programmable ICs

Read only memory (ROM)

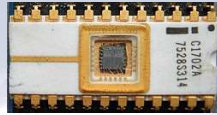- Programmable read-only memory (PROM)
- EPROM
- EEPROM
- Flash memory
- FeRAM
- MRAM
- PRAM



421



PROM as PLD

Address lines - inputs (m)

Data lines – outputs (n)

2^m values stored, 2^n functions available,

422



Digital programmable ICs

- Motorola XC157 (1969) 12 gates 30 I/O mask programmable
- General Electric Company (1971) UV PROM PLD.

423



Digital programmable ICs

- Programmable read-only memory (PROM)
- Programmable logic devices (PLD)
- Generic array logic (GAL)
- Complex programmable logic device (CPLD)
- Field-programmable gate array (FPGA)

424



Application-specific integrated circuit

5,000 to over 100 million gates.

Modern ASICs often include:

- 32-bit processors,
- memory blocks including ROM, RAM, EEPROM, Flash

Designers of digital ASICs use a hardware description language (HDL), such as Verilog or VHDL, to describe the functionality of ASICs.

425



Application-specific integrated circuit

- Standard cell design
- Gate array design
- Full-custom design
- Structured design
- Cell libraries, IP-based design, hard and soft macros

426



IDM ASIC suppliers

- Avago Technologies
- Elmos Semiconductor
- Cavium Networks
- Fujitsu
- Freescale
- HITACHI
- IBM
- Infineon Technologies
- LSI Corporation
- Marvell Semiconductors
- NEC
- NXP Semiconductors
- ON Semiconductor
- Renesas
- Samsung
- STMicroelectronics
- Texas Instruments
- Toshiba
- TSMC

427



Lecture Plan

1. Noise in active circuits
2. Power amplifiers integrated circuits
3. Band pass amplifiers integrated circuits
4. Active analog filters with continuous and discrete time
5. Analog multipliers
6. Phase-locked loop and its applications
7. Detectors of amplitude, frequency and phase
8. Programmable analog circuits and their applications
9. Application specific integrated circuits
10. Digital to analog and analog to digital converters

428




Analog and Discrete Signals

Analog signal - continuous function of time

Discrete signal - defined at discrete instants of time t_0, t_1, t_2, \dots such that $t_i - t_{i-1} = \Delta t$ where Δt is the sampling interval



Sampling of an analog signal

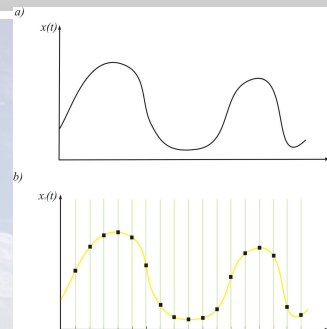

©D. Mlynarski



Discrete Signals

Shannon-Kotelnikov theorem:


An analog signal $x(t)$ can be perfectly reconstructed from its discrete version provided that:

1. $x(t)$ is band-limited, ie. $X(f)=0$, for $f \leq f_h$
2. the sampling frequency $f_s = 1/\Delta t$ is at least equal to $2f_h$





Discrete signal is still an analog signal, but it is not a continuous function of time.



Quantization of an discrete signal

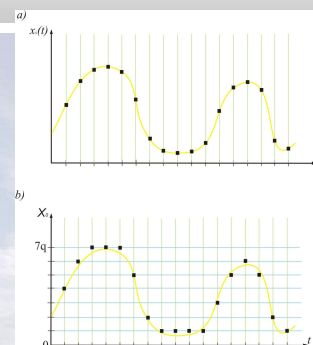

©D. Mlynarski

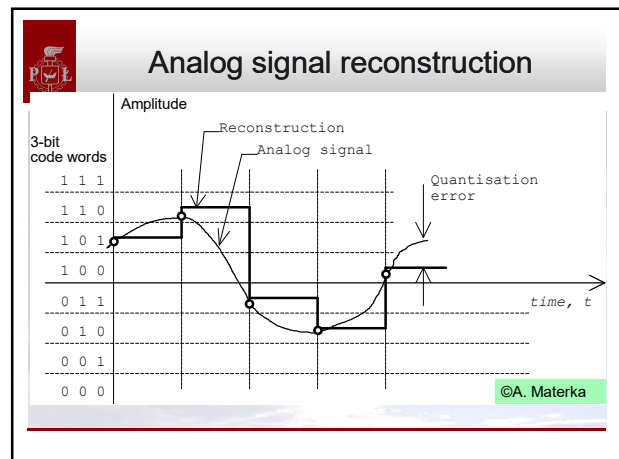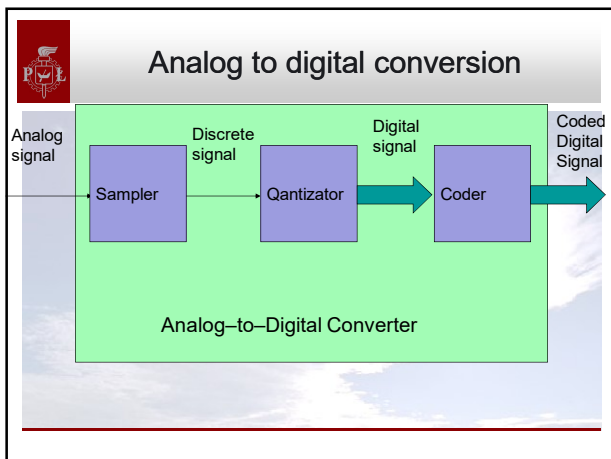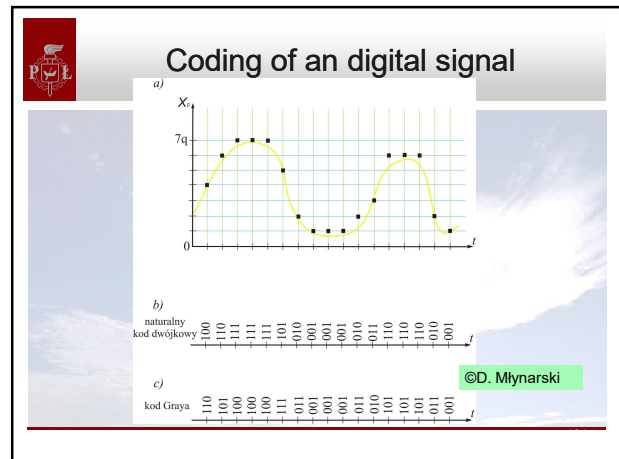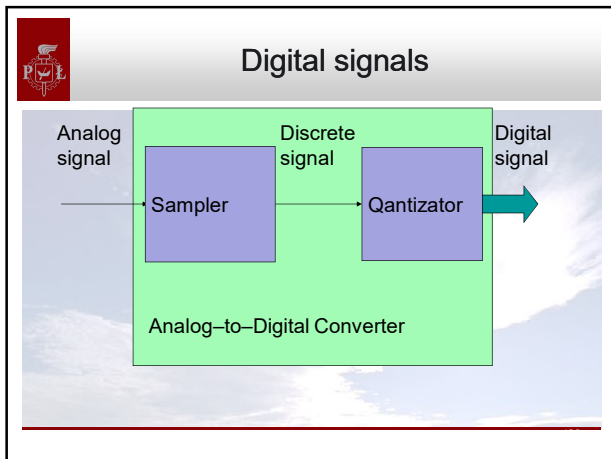

Digital signals

Number of amplitude zones (quantization levels)

$$N = 2^k$$

k=8 -> N = 256
 k=16 -> N = 65536
 k=24 -> N = 16 777 216

10-bit - instrumentation,
 16-bit - Compact Disc technology
 24-bit - color image processing (3 x 8 bit, or 8 bits per color)

- ### Advantages of digital signal processing
- coming through the use of digital electronics
- flexibility (digital circuits are programmable),
 - smaller tolerances on components,
 - lower sensitivity to external (eg. temperature) and internal (eg. ageing and drift) effects,
 - accuracy can be controlled by selecting the word length,
 - circuits are reproducible (no trimming or tuning during manufacture),
 - no accumulation of drift and noise -> unlimited number of successive operations,
 - easier to manufacture in IC technology (no large L or C).



Advantages of digital signal processing

related to limitations of analog electronics

- "ideal memory" to store signals for an infinite time
-> very low frequency signals can be processed with no need for large Cs and Ls
- linear phase filters - not available in analog electronics,
- circuits for exact compensation of two effects,
- adaptive systems,
- precise signal transforms,
- processing of 2D signals.



Main disadvantages of digital signal processing

- more supply power required (passive digital circuits do not yet exist),
- low-frequency applications,
- when used in analog environment, often complex AD and DA converters are required
- difficulties with AD and DA conversion of very weak and very strong signals -> analog pre- and post-amplifiers required,
- the same information (eg. music signal) requires larger bandwidth as a digital signal than it does as the analog one.




ADC

- <http://ww1.microchip.com/downloads/en/devicedoc/21841a.pdf>
- <http://www.maxim-ic.com/app-notes/index.mvp/id/641/CMP/ELK-11>
- <http://www.analog.com/library/analogDialogue/archives/39-06/architecture.html>
- <http://www.beis.de/Elektronik/DeltaSigma/DeltaSigma.html>
- http://en.wikipedia.org/wiki/Analog-to-digital_converter
- <http://www.maxim-ic.com/app-notes/index.mvp/id/1870>
- Data sheets: AD7714, MCP3008, MAX104

441




Bridge sensor e.g. load cell

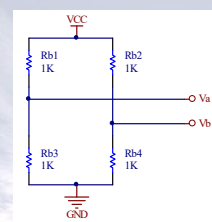

442




Amplifiers

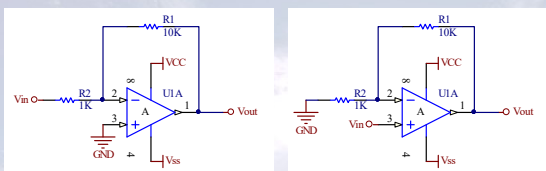

443




Differential amplifier

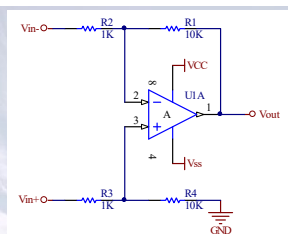

444




Buffered differential amplifier

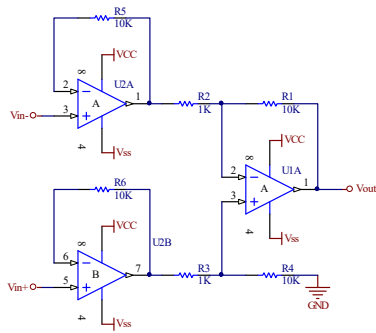

445




Buffered differential amplifier

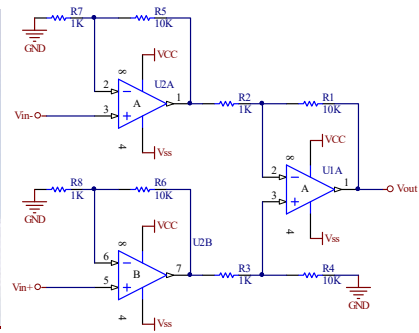

446




Buffered differential amplifier

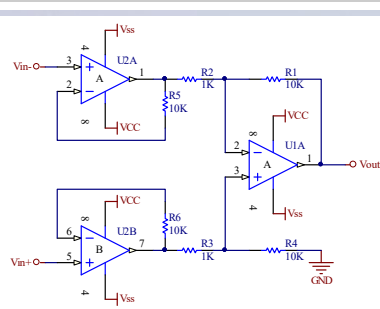

447



Instrumentation amplifier

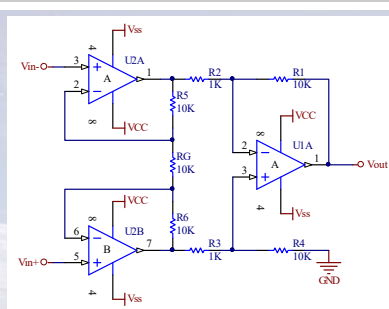

448



Instrumentation amplifier

- INA114
- INA128
- AD8422
- LT1167

449